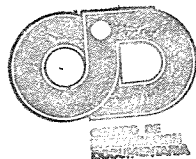


No. 1133  
\$9.95

~ 6 JUN 1980



JUL 1 1980

# THE ACTIVE FILTER HANDBOOK

**TAB BOOKS**  

---

BLUE RIDGE SUMMIT, PA. 17214

# Contents

<b>1</b>	<b>Filter Fundamentals .....</b>	<b>11</b>
	Definitions and Concepts—Transformed Impedance—Transfer Function—Bode Diagrams—Pole and Zero Values for the Transfer Function—Plotting Approximate Amplitude Response—Frequency and Impedance Scaling or Normalizing—Second Order Transfer Function Amplitude and Phase Response—Third Order Transfer Function Amplitude and Phase Response	
<b>2</b>	<b>Operational Amplifier Characteristics and Circuits .....</b>	<b>42</b>
	Frequency Response and Gain—Op Amp Specifications—Which Op Amp to Use—Inverting Op Amp—Noninverting Amplifier—Voltage Follower—Summing Amplifier—Difference Amplifier—Differentiator—Integrator—Voltage Comparator—Op Amp Circuits Employed in Active Filters	
<b>3</b>	<b>Butterworth and Chebyshev Transfer Functions .....</b>	<b>61</b>
	Butterworth Low-Pass Filter—Butterworth Transfer Functions—Chebyshev or Equal Ripple Low-Pass Filter—Comparing the Butterworth and Chebyshev Responses—Chebyshev Filter Transfer Functions—The Inverse Chebyshev Filter—Frequency Transformation—Low-Pass to High-Pass Transformation—Low-Pass to Band-Pass Transformation	
<b>4</b>	<b>Putting Together an Active Filter Circuit .....</b>	<b>80</b>
	Infinite Gain Multiple Feedback Filters—Voltage Controlled Voltage Source (VCVS) Filters—Biquad Active Filter Circuit—Higher Order Active Filters	
<b>5</b>	<b>Low-Pass Active Filter Design .....</b>	<b>104</b>
	Infinite Gain Multiple Feedback Low-Pass Filters—Voltage Controlled Voltage Source (VCVS) or Sallen and Key Low-Pass Filters—Higher Order Low-Pass Filter Circuits—Frequency Response	

<b>6</b>	<b>High-Pass Active Filter Design</b> .....	<b>130</b>
	Infinite Gain Multiple Feedback High-Pass Filters—Voltage Controlled Voltage Source (VCVS) or Sallen and Key High-Pass Filters—Higher Order High-Pass Filter Circuits—Frequency Response	
<b>7</b>	<b>Band-Pass Active Filter Design</b> .....	<b>159</b>
	Infinite Gain Multiple Feedback Band-Pass Filters—Voltage Controlled Voltage Source (VCVS) or Sallen and Key Band-Pass Filters—Positive Feedback Second Order Band-Pass Active Filters—Higher Order Band-Pass Active Filters—State Variable Band-Pass Active Filter—Biquad Band-Pass Active Filter	
<b>8</b>	<b>Other Types of Active Filters</b> .....	<b>191</b>
	The Band-Reject or Notch Active Filter—A VCVS Notch or Band-Reject Active Filter Circuit—An Infinite Gain MFB Notch or Band-Reject Active Filter—All-Pass or Phase Shift Active Filter	
<b>9</b>	<b>Applications of Active Filters</b> .....	<b>206</b>
	Scratch, Rumble, and Speech Filters—Octave Equalizer—Pink Noise Generator—Room Equalizing Instrument—Biamplication—Active Crossover Networks—Electronic Music—Speech Therapy—Modems	
<b>10</b>	<b>Active Filter Potpourri</b> .....	<b>227</b>
	Deliyannis Band-Pass Active Filter Circuit—Testing the Deliyannis Circuit—Jump Resonance in Band-Pass Active Filter Circuits—Voltage Controlled State Variable Filter—Transconductance Controlled Low-Pass, High-Pass, or All-Pass Filters	
<b>Appendices</b>		
	<b>The Q of a State Variable Filter</b> .....	<b>255</b>
	<b>The General Transconductance Controlled Network</b> .....	<b>259</b>
	<b>LM108/LM208 Operational Amplifiers</b> .....	<b>261</b>
	<b>MC1741/MC1741C Operational Amplifiers</b> .....	<b>266</b>
	<b>Additional Reading</b> .....	<b>277</b>
	<b>Index</b> .....	<b>279</b>