

621.38
L 254
H

ELECTRONIC DESIGNERS' HANDBOOK

ROBERT W. LANDEE

*Assistant Director of Research and Development
Western Division
Collins Radio Company, Burbank, California*

DONOVAN C. DAVIS

*Assistant Director of Engineering
Gilfillan Bros. Inc., Los Angeles, California*

ALBERT P. ALBRECHT

*General Manager
Space Electronics Corporation*

McGraw-Hill Book Company, Inc.
New York Toronto London
1957



Instituto Nacional
de Tecnología Industrial
Extensión y Desarrollo
División Biblioteca

INTI

132346

Contents

Preface	v
SECTION 1 GENERAL DESIGN DATA	1-1
Tables	1-2
Figures	1-17
SECTION 2 VACUUM TUBES AND TRANSISTORS	2-1
2.1 Electron Motion	2-2
2.2 Electron Emission	2-6
2.3 Diodes	2-12
2.4 Triode Tubes	2-17
2.5 Tetrode Tubes	2-29
2.6 Pentode Tubes	2-35
2.7 Cathode-ray Tubes	2-39
2.8 Gas Tubes	2-49
2.9 Transistors	2-57
SECTION 3 VOLTAGE AMPLIFIERS	3-1
3.1 Classes of Operation and Types of Coupling	3-2
3.2 Amplifier Equivalent Circuits	3-3
3.3 Graphical Analysis of Triode Amplifiers	3-8
3.4 Graphical Analysis of Tetrode or Pentode Amplifiers	3-14
3.5 Gain and Bandwidth. Resistance-coupled Amplifiers	3-17
3.6 Gain and Bandwidth. Impedance-coupled Amplifiers	3-21
3.7 Gain and Bandwidth. Transformer-coupled Amplifiers	3-24
3.8 Grid-input Impedance of an Amplifier	3-27
3.9 Gain-bandwidth Product, Pulse Rise Time, and Tube Selection for Wideband Amplifiers	3-31
3.10 Effect of Bypassed Cathode and Bypassed Screen-grid Resistors on the Frequency Response	3-34
3.11 High-frequency Compensation	3-39
3.12 Low-frequency Compensation	3-47
3.13 Gain and Phase Characteristics of Multiple-stage Amplifiers	3-50
3.14 Cathode Followers	3-52
3.15 Grounded-grid Amplifiers	3-57
3.16 Cathode-coupled Amplifiers	3-58
3.17 Differential Amplifiers	3-61

3.18 Phase Inverters	3-64
3.19 D-C Amplifiers	3-69
SECTION 4 POWER AMPLIFIERS	4-1
4.1 Class A1 Single-ended Transformer-coupled Power Amplifiers	4-2
4.2 Classes A, AB, and B Push-pull Transformer-coupled Power Amplifiers	4-8
4.3 Class B Radio-frequency Power Amplifiers	4-20
4.4 Class C Radio-frequency Power Amplifiers	4-22
SECTION 5 MODULATION	5-1
5.1 Introduction	5-2
5.2 Amplitude Modulation	5-2
5.3 Methods of Amplitude Modulation	5-6
5.4 Suppressed Carrier Modulation and Single-sideband Generation	5-22
5.5 Angle Modulation	5-27
5.6 Methods of Angle Modulation	5-33
5.7 Pulse Modulation	5-39
SECTION 6 OSCILLATORS	6-1
6.1 General Considerations in Oscillator Design	6-2
6.2 Four-terminal <i>LC</i> Oscillators	6-4
6.3 Two-terminal <i>LC</i> Oscillators	6-12
6.4 Crystal Oscillators	6-14
6.5 UHF Oscillators	6-24
6.6 Microwave Oscillators	6-31
6.7 <i>RC</i> Oscillators	6-39
SECTION 7 RECEIVERS	7-1
7.1 Classification of Receivers	7-2
7.2 Noise	7-2
7.3 Superheterodyne Receivers	7-21
7.4 R-F and I-F Amplifiers	7-22
7.5 Mixers	7-60
7.6 Local Oscillators	7-83
7.7 AM Detectors	7-93
7.8 Tuned Radio Frequency Receivers	7-115
7.9 Crystal Video Receivers	7-116
7.10 Superregenerative Receivers	7-119
7.11 Frequency-modulation Receivers	7-125
7.12 Receiver Measurements	7-126
7.13 Practical Considerations in the Design of a Receiver	7-130
SECTION 8 MULTIVIBRATORS	8-1
8.1 Introduction	8-2
8.2 Bistable Multivibrators	8-2
8.3 Plate-coupled Monostable Multivibrators	8-7
8.4 Cathode-coupled Monostable Multivibrators	8-16
8.5 Astable Multivibrators	8-20
8.6 Effects of Tube and Stray Capacitances in Multivibrator Circuits	8-24
8.7 Triggering	8-25
8.8 Synchronization	8-27

SECTION 9 VARIABLE DELAY CIRCUITS	9-1
9.1 Introduction	9-2
9.2 The Screen-coupled Phantastron	9-2
9.3 Cathode-coupled Phantastron	9-8
9.4 The Sanatron	9-11
9.5 The Sanaphant	9-12
9.6 Cathode-coupled Monostable Multivibrator	9-12
SECTION 10 TRIGGER CIRCUITS	10-1
10.1 Introduction	10-2
10.2 RC Differentiation	10-2
10.3 RLC Peaking	10-3
10.4 Blocking Oscillators	10-7
10.5 Thyatron Pulse Generators	10-14
SECTION 11 SAWTOOTH GENERATORS	11-1
11.1 Sawtooth Generators	11-2
11.2 Basic Considerations for Beam Deflection in Electromagnetic Cathode-ray Tubes	11-10
11.3 Basic Considerations for Beam Deflection in Electrostatic Cathode-ray Tubes	11-11
SECTION 12 CLIPPERS, LIMITERS, AND CLAMPS	12-1
12.1 Clippers	12-2
12.2 Limiters	12-5
12.3 Clamps	12-12
SECTION 13 INDUCTIVELY COUPLED CIRCUITS	13-1
13.1 Fundamentals of Inductively Coupled Circuits	13-2
13.2 Undercoupling	13-6
13.3 Critical Coupling	13-7
13.4 Transitional Coupling	13-11
13.5 Overcoupled Circuits	13-14
SECTION 14 TRANSFORMERS AND CHOKES	14-1
14.1 Fundamentals of Magnetic Circuits	14-2
14.2 Fundamentals of Iron-core Transformers	14-8
14.3 Power Transformers	14-21
14.4 Iron-core Chokes	14-30
14.5 Audio Transformers	14-34
14.6 Special Magnetic-circuit Components	14-43
14.7 Pulse Transformers	14-47
SECTION 15 POWER SUPPLIES	15-1
15.1 Characteristics of Ideal Rectifiers with Infinite Inductance Choke-input Filters	15-2
15.2 Critical Inductance of the Input Choke to a Filter	15-2
15.3 Power Supplies Having Choke-input Filters	15-5
15.4 Power Supplies Having Capacitor-input Filters	15-8
15.5 Power Supply LC and RC Low-pass Filters	15-7
15.6 Cancellation and Resonant Filters	15-20

15.7	Gas-tube Voltage Regulators	15-23
15.8	Vacuum-tube Voltage Regulators	15-27
15.9	Zener Diodes as Voltage Regulator Elements	15-47
SECTION 16 FILTERS		16-1
16.1	Constant- k and m -derived Filters	16-2
16.2	Bridged-T and Parallel-T Networks	16-20
16.3	Special Applications of Bridged-T and Parallel-T Networks	16-26
SECTION 17 ATTENUATORS AND EQUALIZERS		17-1
17.1	Fixed Attenuators	17-2
17.2	Amplitude Equalizers	17-4
17.3	Phase Equalizers	17-14
SECTION 18 PRINCIPLES OF FEEDBACK		18-1
18.1	Introduction	18-2
18.2	System Characteristics Affected by Feedback	18-2
18.3	Transfer Functions	18-6
18.4	Methods of Analyzing Stability and Transient Response	18-9
18.5	Minimum-phase-shift Equalizing Networks	18-21
SECTION 19 COMPUTER AND SERVOMECHANISM TECHNIQUES		19-1
19.1	Analog Computers	19-2
19.2	Operational Amplifiers	19-6
19.3	Mathematical Operations	19-7
19.4	Servomechanism Design Principles	19-24
19.5	Servomechanism Elements	19-35
19.6	Stability and Methods of Analysis	19-42
19.7	Error Coefficients and Stabilization Networks	19-53
SECTION 20 TRANSMISSION LINES		20-1
20.1	Fundamentals of Transmission Lines	20-2
20.2	Open-wire Transmission Lines	20-18
20.3	Coaxial Transmission Lines	20-21
20.4	Coaxial Circuit Elements	20-29
20.5	Waveguide Transmission Lines	20-36
20.6	Waveguide Circuit Elements	20-44
20.7	Waveguide Cavities and Filters	20-55
20.8	Delay Lines	20-59
20.9	Ferrite Elements	20-61
SECTION 21 ANTENNAS		21-1
21.1	Fundamentals of Antennas	21-2
21.2	Basic Antennas	21-12
21.3	Systems of Antennas—Antenna Arrays	21-25
21.4	Microwave Radiators	21-38
21.5	Reflector Systems and Lenses	21-43
SECTION 22 WAVEFORM ANALYSIS		22-1
22.1	Peak, Root-mean-square, and Average Values of Recurrent Waveforms	22-2
22.2	Effect of a Superimposed D-C Component	22-2
22.3	Effect of Superposition of Waveforms	22-3

CONTENTS

xi

22.4	Fourier Series	22-6
22.5	Graphical Analysis	22-8
22.6	Spectra of Periodic and Nonperiodic Signals	22-10
22.7	Spectra of Sampled Signals	22-17
SECTION 23 NETWORK ANALYSIS		23-1
23.1	Network Geometry	23-2
23.2	Passive Elements Including Mutual Inductance	23-4
23.3	Active Elements	23-9
23.4	Loop Equations	23-10
23.5	Nodal Equations	23-13
23.6	Solution of Network Equations	23-16
23.7	Thévenin's Theorem	23-31
23.8	Norton's Theorem	23-31
23.9	Superposition Theorem	23-32
23.10	Reciprocity Theorem	23-33
23.11	Compensation Theorem	23-34
23.12	Driving Point and Transfer Impedances and Admittances	23-34
23.13	Dual and Inverse Networks	23-38
23.14	Two-terminal-pair Networks	23-40
23.15	Matrix Methods	23-44
23.16	Network Transformations	23-50
23.17	Dimensional Analysis	23-53
23.18	Buckingham π Theorem	23-54
23.19	Network Algebra	23-55
23.20	Fundamentals of Probability and Statistics	23-58

Index follows Section 23.