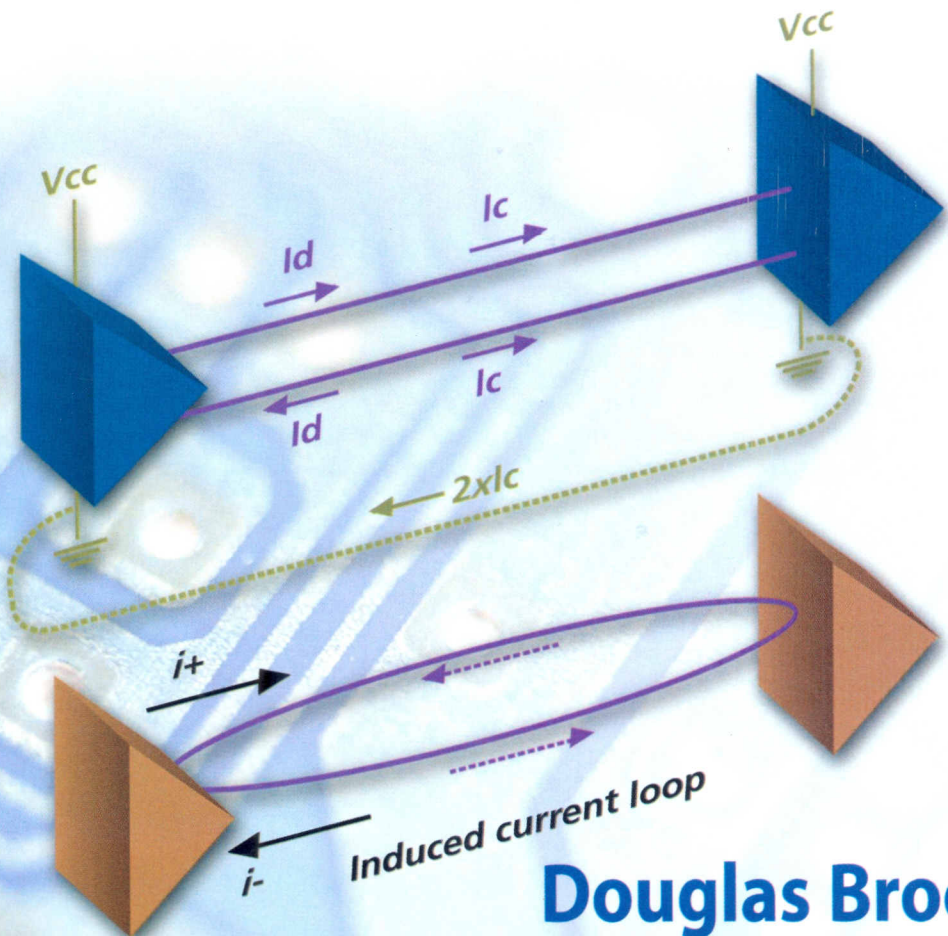


**SIGNAL**

# Integrity Issues and Printed Circuit Board Design



**Douglas Brooks**

# TABLE OF CONTENTS

<b>PREFACE</b> .....	<b>xvii</b>
<b>Part 1 BASIC CONCEPTS</b> .....	<b>1</b>
<b>1 Electronic Concepts</b> .....	<b>3</b>
Current .....	3
Charge .....	5
Voltage .....	6
Direct and Alternating Voltage and Current .....	8
Harmonics .....	11
Measurement of AC Voltage or Current .....	12
Frequency, Rise/Fall Times, and Period .....	13
Frequency Measurement .....	16
Complex Waveforms (Fourier Analyses).....	18
Chapter Endnotes .....	23
Direction of Current Flow .....	23
Some Standard Symbols Used in Electronics .....	24
Some Fundamental Definitions.....	25
Important Names in Electronics.....	26
<b>2 Propagation Times</b> .....	<b>27</b>
Propagation Speed.....	27
Propagation Times .....	28
Trace Configurations and Signal Propagation.....	29
Circuit Timing Issues .....	32
Wavelength .....	35

<b>3</b>	<b>Electrical Components .....</b>	<b>37</b>
	The Three Basics .....	37
	Resistance .....	38
	Ohm's Law .....	39
	Capacitance .....	43
	Charge Storage .....	47
	Formula for Capacitance .....	48
	Capacitance Functions and Effects .....	49
	Inductance .....	50
	Formulas for Inductance .....	55
	Charge and Discharge Currents .....	56
	Resonance .....	60
<b>4</b>	<b>Voltage and Current Changes and Time Constants.....</b>	<b>63</b>
	Voltage and Current Changes Through Resistors .....	63
	Voltage and Current Changes Through Capacitors .....	64
	Voltage and Current Changes Through Inductors .....	66
	Some Interesting Inductive Circuit Dynamics .....	69
	Time Constants .....	71
	A Note on Charge and Discharge Equations .....	76
<b>5</b>	<b>Resistance .....</b>	<b>77</b>
	Kirchhoff's Laws .....	77
	Series Resistors .....	79
	Parallel Resistors .....	81
	Voltage Dividers .....	83
	Amplifier Feedback and Gain .....	85
	Power .....	86
	Equivalent Circuits .....	88
	Power Curve .....	91
	Power Sources .....	93
	Conductance .....	94
<b>6</b>	<b>Reactance .....</b>	<b>97</b>
	Capacitive Reactance .....	98
	Inductive Reactance .....	99
	Ohm's Law for Reactance .....	101
	Series LC Combinations .....	104
	Parallel LC Circuits .....	107
	Resonance .....	111
	Poles and Zeros .....	115

Susceptance.....	119
<b>7 Impedance and Phase Shift.....</b>	<b>121</b>
Impedance .....	121
Effect of Frequency.....	128
Another RC Example .....	129
Classic RC Filter .....	131
Combining Impedances.....	133
Resonance and Q.....	134
Series RLC Circuits.....	137
Series RLC at Resonance .....	140
Admittance.....	142
Chapter Endnotes .....	144
Detailed Calculations for Figure 7-8.....	144
RLC Simulation .....	145
Imaginary Numbers.....	146
<b>Part 2 SIGNAL INTEGRITY ISSUES.....</b>	<b>147</b>
<b>8 Signal Integrity Overview.....</b>	<b>149</b>
<b>9 Electromagnetic Interference (EMI) .....</b>	<b>155</b>
Background.....	155
Fields and Cancellations .....	156
Some Basic Truths .....	158
Signal Coupling.....	159
Loop Area .....	161
Slots in Planes 1 .....	162
Return Pathways .....	163
Power Plane Returns.....	164
Changing Trace Layers .....	165
Unrelated Planes .....	166
Stripline.....	167
Stubs.....	168
Common Mode .....	169
The 20-H Rule.....	173
Picket Fences (Faraday Shields).....	174

<b>10 Reflections and Transmission Lines .....</b>	<b>175</b>
Communications Model .....	175
Transmission Lines .....	178
Critical Length .....	181
Reflection Coefficients.....	183
Visualizing Reflections .....	184
Determining Trace Impedance .....	185
Termination Techniques.....	190
Parallel .....	192
Thevenin .....	192
AC Termination .....	194
Series.....	194
Diode.....	195
Some Design Issues.....	196
Changing Trace Layers 1 .....	196
Power Planes.....	197
Changing Trace Layers 2 .....	197
Slots in Planes 2 .....	199
Stubs.....	200
Absolute vs. Relative Value of $Z_0$ .....	201
Chapter Endnote.....	203
On Formulas.....	203
<b>11 Some Transmission Line Simulations.....</b>	<b>207</b>
Basic Simulation .....	207
Series Termination .....	215
Placement Issues .....	217
Branches, or Ys .....	219
<b>12 Crosstalk.....</b>	<b>221</b>
Forward versus Backward Crosstalk.....	221
Backward Crosstalk .....	223
Forward Crosstalk .....	225
In Summary.....	226
Estimating Crosstalk .....	226
Calculations.....	226
Coupling.....	227
Distance .....	227
Terminations .....	229
UltraCAD Calculator .....	230
HyperLynx Simulation Tool .....	231
Design Considerations .....	232

Slots in Planes 3 .....	232
Guard Bands.....	233
<b>13 Crosstalk Simulations .....</b>	<b>235</b>
Basic Model .....	235
Add an Uncoupled Region .....	239
Effect of Length .....	240
Stripline.....	242
Stripline With Terminations.....	242
More Realistic Example.....	244
Summary .....	247
<b>14 Differential Traces and Impedance.....</b>	<b>249</b>
Background .....	249
Advantages.....	249
Key Assumptions.....	251
Design Rules .....	255
Design Rule 1 (Equal Length).....	255
Common Mode Implications .....	255
Differential Signals and Loop Areas.....	256
Design Rule 2 (Close Together).....	257
Rule 2 Consequence.....	258
Design Rule 3 (Differential Impedance) .....	260
Differential Mode Impedance .....	260
Common Mode Impedance.....	261
Design Rule 4 (Constant Separation).....	262
Differential Simulations .....	262
Calculating Differential Impedance .....	265
Edge Coupled.....	266
Broadside Coupled.....	268
<b>15 Bypass Caps and Decoupling Systems .....</b>	<b>269</b>
Traditional Approach .....	269
Size and Quantity.....	273
Placement.....	275
Connection .....	276
Power System Impedance Approach.....	277
Ideal Response .....	277
Capacitor Response.....	278
Inductance Effects.....	278
Multiple Capacitors.....	280
Additional Capacitor Value.....	281

Planar Capacitance.....	282
Equivalent Series Resistance (ESR).....	285
Self Resonant Frequencies.....	287
Effects of Multiple Capacitors.....	288
Parallel Capacitors.....	288
Resonance.....	290
Impedance at Self-Resonant Frequency.....	291
Impedance at Anti-Resonance.....	292
General Case Analysis.....	293
Consequences.....	294
Summary.....	296
<b>16 Power Systems.....</b>	<b>297</b>
Power Supply Voltages.....	297
Need For Power Planes.....	300
Strategies For Designing With Plane.....	300
Some Design Rules.....	303
Connecting Reference Planes Together.....	303
Overlapping Planes.....	304
Decoupling to Wrong Plane.....	305
Signals Crossing Separations.....	305
Stack-Ups.....	307
Conclusion.....	308
<b>17 Lossy Lines and Eye Diagrams.....</b>	<b>311</b>
Lossy Lines.....	311
Skin Effect.....	312
Dielectric Absorption.....	314
Lossy Line Model.....	314
Eye Diagrams.....	316
Equalization.....	318
Passive Equalization.....	319
Active Equalization.....	319
Summary.....	320
<b>Part 3 Appendices, Glossary, and Index.....</b>	<b>323</b>
<b>Appendices.....</b>	<b>325</b>
A UltraCAD's Square Wave Simulator.....	325
B Why Inductors Induct.....	329
C Logarithms.....	345

D Phase Shift Simulation .....351  
 E Complex Algebra .....357  
 F Transmission Line Simulation.....367  
 G Echo Illustration .....369  
 H UltraCAD Freeware Calculators .....371  
 I TDRs and VNAs .....375  
 J Right Angle Corners.....383

**Glossary** .....387

**Index** .....397

**About the Author**.....401