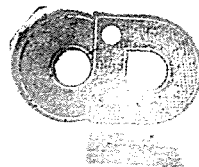


Handbook of Practical Electronic Tests and Measurements

John D. Lenk

Consulting Technical Writer



PRENTICE-HALL, INC.
Englewood Cliffs, N.J.

Contents

SAFETY PRECAUTIONS 1

1 VOLTAGE MEASUREMENTS 3

- 1-1. Kirchhoff's voltage law, 3
- 1-2. Basic voltmeter measurements, 5
- 1-3. Checking voltmeter accuracy, 7
- 1-4. Extending voltmeter ranges, 9
- 1-5. Suppressed-zero voltage measurements, 11
- 1-6. Measuring voltages with oscilloscopes, 12
- 1-7. Measuring peak-to-peak voltages with an oscilloscope, 13
- 1-8. Measuring instantaneous voltage with an oscilloscope, 15
- 1-9. Voltage measurements with a variable calibrating source, 18
- 1-10. Measuring composite and pulsating voltage with an oscilloscope, 21
- 1-11. Measuring complex voltages with a meter, 24
- 1-12. Measuring radio frequency voltages, 26
- 1-13. Measuring 3-phase circuit voltages, 30
- 1-14. Measuring voltage-sensitive circuits, 31

2 CURRENT MEASUREMENTS 34

- 2-1. Kirchhoff's current law, 34
- 2-2. Ohm's law for direct current, 34

- 2-3. Ohm's law for alternating current circuits, 36
- 2-4. Basic ammeter (current) measurements, 37
- 2-5. Checking ammeter accuracy, 38
- 2-6. Extending ammeter ranges, 39
- 2-7. In-circuit current measurements, 42
- 2-8. Current measurement with a current probe, 44
- 2-9. Measuring 3-phase circuit currents, 45

3 RESISTANCE MEASUREMENTS 46

- 3-1. Basic resistance equations, 46
- 3-2. Resistor color codes, 46
- 3-3. Solving resistance network problems, 48
- 3-4. Basic ohmmeter (resistance) measurements, 50
- 3-5. Checking ohmmeter accuracy, 51
- 3-6. Extending ohmmeter ranges, 51
- 3-7. Resistance bridges, 54
- 3-8. Testing potentiometers and variable resistors, 56
- 3-9. Measuring thermal or ballast resistances, 58
- 3-10. Measuring internal resistance of circuits, 59

4 CAPACITANCE MEASUREMENTS 62

- 4-1. Basic capacitance equations, 62
- 4-2. Capacitor color codes, 62
- 4-3. Capacitance bridges, 66
- 4-4. Testing capacitors with a meter, 67
- 4-5. Measuring capacitance with a dip circuit, 75
- 4-6. Measuring capacitance with a resonant circuit, 78

5 INDUCTANCE MEASUREMENTS 80

- 5-1. Basic inductance equations, 80
- 5-2. Inductance bridges, 84
- 5-3. Measuring inductance with a dip circuit, 87
- 5-4. Measuring self-resonance and distributed capacitance of inductors, 89
- 5-5. Coupling dip circuits to inductors, 90
- 5-6. Dynamic distributed capacitance measurements, 91
- 5-7. Measuring inductance with a resonant circuit, 93

6 IMPEDANCE MEASUREMENTS 96

- 6-1. Basic impedance equations, 96
- 6-2. Effects of frequency on impedance, 99

- 6-3. Matching impedances, 100
- 6-4. Measuring impedance in power circuits, 101
- 6-5. Measuring impedance with pulses, 103
- 6-6. Measuring impedances with sweep frequencies, 106

7 DECIBEL MEASUREMENTS 118

- 7-1. Power ratio units, 118
- 7-2. Decibel conversion chart, 120
- 7-3. Practical decibel measurements, 121
- 7-4. Effect of blocking capacitor on decibel readings, 125

8 TIME, FREQUENCY, AND PHASE MEASUREMENT 128

- 8-1. Relationship of wavelength, frequency, period, and velocity, 128
- 8-2. Time-duration measurements, 130
- 8-3. Frequency measurements with an oscilloscope (internal sweep), 134
- 8-4. Frequency measurements with Lissajous figures, 134
- 8-5. Frequency measurements with modulated ring patterns, 137
- 8-6. Frequency measurements with broken ring patterns, 139
- 8-7. Frequency measurements with broken line patterns, 141
- 8-8. Zero-beat frequency measurement, 143
- 8-9. Measuring resonant frequency with dip adapters, 148
- 8-10. Measuring resonant frequency of LC circuits with a meter, 150
- 8-11. Sweep frequency technique for measuring resonant frequency of tuning devices, 151
- 8-12. Measuring frequency response, 152
- 8-13. Frequency bridges, 156
- 8-14. Phase angle relationships, 158
- 8-15. Phase measurement, 164

9 SOLID STATE MEASUREMENTS 174

- 9-1. Basic diode tests, 174
- 9-2. Diode continuity tests, 174
- 9-3. Diode reverse leakage and forward voltage drop tests, 176
- 9-4. Dynamic diode tests, 177
- 9-5. Diode switching tests, 180
- 9-6. Zener diode tests, 182
- 9-7. Tunnel diode tests, 185
- 9-8. Basic transistor testing, 189
- 9-9. Transistor tests (ohmmeter method), 190
- 9-10. Transistor leakage tests, 191
- 9-11. Transistor breakdown tests, 193
- 9-12. Transistor gain tests, 193
- 9-13. Transistor switching tests, 199

- 9-14. Testing unijunction transistors, 203
- 9-15. Testing field effect transistors, 205
- 9-16. Controlled rectifier tests, 212
- 9-17. Integrated circuit tests, 219

10 MICROWAVE MEASUREMENTS 221

- 10-1. Microwave power measurement, 221
- 10-2. Microwave measurement devices, 226
- 10-3. Fixed-frequency versus swept-frequency measurements, 229
- 10-4. Microwave impedance measurements, 229
- 10-5. Microwave attenuation measurements, 232
- 10-6. Microwave frequency measurements, 233

11 ANTENNA AND TRANSMISSION LINE MEASUREMENTS 237

- 11-1. Antenna length and resonance measurements, 237
- 11-2. Antenna impedance and radiated power, 241
- 11-3. Antenna gain, 245
- 11-4. Transmission line measurements, 246
- 11-5. Standing-wave ratio measurements, 251

12 MISCELLANEOUS CIRCUIT AND COMPONENT TESTS 255

- 12-1. Photocell tests, 255
- 12-2. Relay tests, 256
- 12-3. Vibrator tests, 256
- 12-4. Chopper tests, 259
- 12-5. Magnetic component tests, 259
- 12-6. Ferroelectric component tests, 261
- 12-7. Microphone tests, 262
- 12-8. Transformer tests, 263
- 12-9. Battery tests, 268
- 12-10. Quartz crystal tests, 270
- 12-11. L and T pad tests, 270
- 12-12. Resonance and Q measurements, 273
- 12-13. Distortion measurements, 276
- 12-14. Noise measurements, 282
- 12-15. Modulation measurements, 286
- 12-16. Delay measurements, 289
- 12-17. Strain, acceleration, and pressure measurements, 290
- 12-18. Vibration measurements, 293
- 12-19. Speed measurements, 293