

621.39  
L 248  
H

# RADIOTRON DESIGNER'S HANDBOOK

Edited By  
**F. LANGFORD-SMITH**  
*B.Sc., B.E. (1st class honours)*  
*Senior Member I.R.E. (U.S.A.)*  
*A.M.I.E. (Aust.)*

FOURTH EDITION

Published by the Wireless Press  
for  
AMALGAMATED WIRELESS VALVE COMPANY PTY. LTD.  
47 YORK STREET, SYDNEY, AUSTRALIA  
1952

Reproduced and Distributed  
by  
RCA Victor Division  
RADIO CORPORATION OF AMERICA  
HARRISON, N. J.

# CHAPTER HEADINGS

## PART 1: THE RADIO VALVE

CHAPTER	PAGE
1 INTRODUCTION TO THE RADIO VALVE ... ..	1
2 VALVE CHARACTERISTICS ... ..	13
3 THE TESTING OF OXIDE-COATED CATHODE HIGH-VACUUM RECEIVING VALVES	68

## PART 2: GENERAL THEORY AND COMPONENTS

4 THEORY OF NETWORKS ... ..	128
5 TRANSFORMERS AND IRON-CORED INDUCTORS ... ..	199
6 MATHEMATICS ... ..	254
7 NEGATIVE FEEDBACK ... ..	306
8 WAVE MOTION AND THE THEORY OF MODULATION ... ..	403
9 TUNED CIRCUITS ... ..	407
10 CALCULATION OF INDUCTANCE ... ..	429
11 DESIGN OF RADIO FREQUENCY INDUCTORS ... ..	450

## PART 3: AUDIO FREQUENCIES

12 AUDIO FREQUENCY VOLTAGE AMPLIFIERS ... ..	481
13 AUDIO FREQUENCY POWER AMPLIFIERS ... ..	544
14 FIDELITY AND DISTORTION ... ..	603
15 TONE COMPENSATION AND TONE CONTROL ... ..	635
16 VOLUME EXPANSION, COMPRESSION AND LIMITING ... ..	679
17 REPRODUCTION FROM RECORDS... ..	701
18 MICROPHONES, PRE-AMPLIFIERS, ATTENUATORS AND MIXERS... ..	775
19 UNITS FOR THE MEASUREMENT OF GAIN AND NOISE ... ..	806
20 LOUDSPEAKERS ... ..	831
21 THE NETWORK BETWEEN THE POWER OUTPUT STAGE AND THE LOUDSPEAKER	880

## PART 4: RADIO FREQUENCIES

22 AERIALS AND TRANSMISSION LINES ... ..	890
23 RADIO FREQUENCY AMPLIFIERS ... ..	912
24 OSCILLATORS ... ..	947
25 FREQUENCY CONVERSION AND TRACKING ... ..	962
26 INTERMEDIATE FREQUENCY AMPLIFIERS ... ..	1020
27 DETECTION AND AUTOMATIC VOLUME CONTROL ... ..	1072
28 REFLEX AMPLIFIERS ... ..	1140
29 LIMITERS AND AUTOMATIC FREQUENCY CONTROL ... ..	1147

## PART 5: RECTIFICATION, REGULATION, FILTERING AND HUM

30 RECTIFICATION ... ..	1161
31 FILTERING AND HUM ... ..	1192
32 VIBRATOR POWER SUPPLIES ... ..	1202
33 CURRENT AND VOLTAGE REGULATORS ... ..	1213

## PART 6: COMPLETE RECEIVERS

34 TYPES OF A-M RECEIVERS ... ..	1223
35 DESIGN OF SUPERHETERODYNE A-M RECEIVERS ... ..	1228
36 DESIGN OF F-M RECEIVERS ... ..	1287
37 RECEIVER AND AMPLIFIER TESTS AND MEASUREMENTS ... ..	1297

## PART 7: SUNDRY DATA

38 TABLES, CHARTS AND SUNDRY DATA ... ..	1328
--	------

See next page for detailed List of Contents.

SUPPLEMENT ... ..	1475
-------------------	------

# CONTENTS

## PART 1: THE RADIO VALVE

### CHAPTER 1. INTRODUCTION TO THE RADIO VALVE

SECTION	PAGE
1. ELECTRICITY AND EMISSION ... ..	1
2. THE COMPONENT PARTS OF RADIO VALVES ... ..	4
(i) Filaments, cathodes and heaters ... ..	4
(ii) Grids ... ..	5
(iii) Plates ... ..	5
(iv) Bulbs ... ..	5
(v) Voltages with valve operation ... ..	5
3. TYPES OF RADIO VALVES ... ..	6
(i) Diodes ... ..	6
(ii) Triodes ... ..	7
(iii) Tetrodes ... ..	7
(iv) Pentodes ... ..	7
(v) Pentode power amplifiers ... ..	8
(vi) Combined valves ... ..	8
(vii) Pentagrid converters ... ..	8
4. MAXIMUM RATINGS AND TOLERANCES ... ..	9
(i) Maximum ratings and their interpretation ... ..	9
(ii) Tolerances ... ..	9
5. FILAMENT AND HEATER VOLTAGE/CURRENT CHARACTERISTICS ... ..	10
6. VALVE NUMBERING SYSTEMS ... ..	10
7. REFERENCES ... ..	12

### CHAPTER 2. VALVE CHARACTERISTICS

1. VALVE COEFFICIENTS ... ..	13
2. CHARACTERISTIC CURVES ... ..	15
(i) Plate characteristics ... ..	15
(ii) Mutual characteristics ... ..	17
(iii) Grid current characteristics ... ..	18
(iv) Suppressor characteristics ... ..	21
(v) Constant current curves ... ..	22
(vi) "G" curves ... ..	23
(vii) Drift of characteristics during life ... ..	23
(viii) Effect of heater-voltage variation ... ..	24
3. RESISTANCE-LOADED AMPLIFIERS ... ..	24
(i) Triodes ... ..	24
(ii) Pentodes ... ..	26
4. TRANSFORMER-COUPLED AMPLIFIERS ... ..	27
(i) With resistive load ... ..	27
(ii) Effect of primary resistance ... ..	28
(iii) With i-f voltage amplifiers ... ..	28
(iv) R-F amplifiers with sliding screen ... ..	28

## CONTENTS

SECTION	PAGE
(v) Cathode loadlines ... .. .	29
(vi) With reactive loads ... .. .	30
5. TRIODE OPERATION OF PENTODES ... .. .	34
(i) Triode operation of pentodes ... .. .	34
(ii) Examples of transconductance calculation ... .. .	34
(iii) Triode amplification factor ... .. .	35
(iv) Plate resistance ... .. .	36
(v) Connection of suppressor grid ... .. .	36
6. CONVERSION FACTORS, AND THE CALCULATION OF CHARACTERISTICS OTHER THAN THOSE PUBLISHED ... .. .	36
(i) The basis of valve conversion factors ... .. .	36
(ii) The use of valve conversion factors ... .. .	37
(iii) The calculation of valve characteristics other than those published ... .. .	40
(iv) The effect of changes in operating conditions ... .. .	42
7. VALVE EQUIVALENT CIRCUITS AND VECTORS ... .. .	45
(i) Constant voltage equivalent circuit ... .. .	45
(ii) Constant current equivalent circuit ... .. .	46
(iii) Valve vectors ... .. .	47
8. VALVE ADMITTANCES ... .. .	49
(i) Grid input impedance and admittance ... .. .	49
(ii) Admittance coefficients ... .. .	50
(iii) The components of grid admittance—input resistance—input capacitance—grid input admittance ... .. .	51
(iv) Typical values of short-circuit input conductance ... .. .	55
(v) Change of short-circuit-input capacitance with transconductance ... .. .	55
(vi) Grid-cathode capacitance ... .. .	56
(vii) Input capacitances of pentodes (published values) ... .. .	56
(viii) Grid-plate capacitance ... .. .	57
9. MATHEMATICAL RELATIONSHIPS ... .. .	57
(i) General ... .. .	57
(ii) Resistance load ... .. .	58
(iii) Power and efficiency ... .. .	59
(iv) Series expansion; resistance load ... .. .	61
(v) Series expansion; general case ... .. .	63
(vi) The equivalent plate circuit theorem ... .. .	63
(vii) Dynamic load line—general case ... .. .	64
(viii) Valve networks—general case ... .. .	64
(ix) Valve coefficients as partial differentials ... .. .	64
(x) Valve characteristics at low plate currents ... .. .	65
10. REFERENCES ... .. .	66
<b>CHAPTER 3. THE TESTING OF OXIDE-COATED CATHODE HIGH-VACUUM RECEIVING VALVES</b>	
1. BASIS OF TESTING PRACTICE ... .. .	68
(i) Fundamental physical properties ... .. .	69
(ii) Basic functional characteristics ... .. .	70
(iii) Fundamental characteristic tests ... .. .	73
(iv) Valve ratings and their limiting effect on operation ... .. .	75
(A) Limiting ratings ... .. .	75
(B) Characteristics usually rated ... .. .	75
(C) Rating systems ... .. .	77
(D) Interpretation of maximum ratings ... .. .	77
(E) Operating conditions ... .. .	80
(v) Recommended practice and operation ... .. .	80
(a) Mounting ... .. .	80
(b) Ventilation ... .. .	81

# CONTENTS

SECTION	PAGE
(c) Heater-cathode insulation ... ..	81
(d) Control grid circuit resistance ... ..	82
(e) Operation at low screen voltages ... ..	84
(f) Microphony ... ..	84
(g) Hum ... ..	84
(h) Stand-by operation ... ..	84
2. CONTROL OF CHARACTERISTICS DURING MANUFACTURE ... ..	85
(i) Importance of control over characteristics ... ..	85
(ii) Basic manufacturing test specification ... ..	85
(iii) Systematic testing ... ..	86
(iv) Tolerances on characteristics ... ..	88
3. METHODS OF TESTING CHARACTERISTICS ... ..	89
(i) General conventions ... ..	90
(ii) General characteristics ... ..	91
(a) Physical dimensions ... ..	91
(b) Shorts and continuity ... ..	91
(c) Heater (or filament) current ... ..	93
(d) Heater to cathode leakage ... ..	94
(e) Inter-electrode insulation ... ..	94
(f) Emission ... ..	94
(g) Direct inter-electrode capacitances ... ..	95
(iii) Specific diode characteristics ... ..	99
(a) Rectification test ... ..	99
(b) Sputter and arcing ... ..	100
(c) Back emission ... ..	100
(d) Zero signal or standing diode current ... ..	101
(iv) Specific triode, pentode and beam tetrode characteristics... ..	101
(A) Reverse grid current ... ..	101
(B) Grid current commencement voltage ... ..	102
(C) Positive grid current ... ..	102
(D) Positive voltage electrode currents ... ..	103
(E) Transconductance or mutual conductance... ..	103
(F) Amplification factor ... ..	104
(G) Plate resistance ... ..	104
(H) A.C. amplification ... ..	105
(I) Power output ... ..	105
(J) Distortion ... ..	106
(K) Microphony ... ..	107
(L) Audio frequency noise ... ..	107
(M) Radio frequency noise ... ..	107
(N) Blocking ... ..	107
(O) Stage gain testing ... ..	108
(P) Electrode dissipation ... ..	108
(v) Specific converter characteristics ... ..	108
(A) Methods of operation including oscillator excitation ... ..	108
(1) Oscillator self-excited ... ..	108
(2) Oscillator driven ... ..	109
(3) Static operation ... ..	109
(B) Specific characteristics ... ..	109
(a) Reverse signal grid current ... ..	109
(b) Signal-grid current commencement ... ..	109
(c) Mixer positive voltage electrode currents ... ..	109
(d) Mixer conversion transconductance ... ..	109
(e) Mixer plate resistance ... ..	111
(f) Mixer transconductance ... ..	111
(g) Oscillator grid current ... ..	111

	PAGE
(h) Oscillator plate current ... ..	113
(i) Oscillator transconductance ... ..	113
(j) Oscillator amplification factor ... ..	113
(k) Oscillator plate resistance ... ..	113
(l) Signal-grid blocking... ..	113
(m) Microphony ... ..	113
(n) R-F noise ... ..	113
(vi) Tests for special characteristics ... ..	113
(A) Short-circuit input admittance ... ..	113
(B) Short-circuit feedback admittance ... ..	117
(C) Short-circuit output admittance ... ..	117
(D) Short-circuit forward admittance ... ..	117
(E) Perveance ... ..	117
(vii) Characteristics by pulse methods—point by point ... ..	118
(viii) Characteristics by curve tracer methods ... ..	119
4. ACCEPTANCE TESTING ... ..	120
(i) Relevant characteristics ... ..	120
(ii) Valve specifications ... ..	120
(iii) Testing procedure ... ..	120
5. SERVICE TESTING AND SERVICE TESTER PRACTICE ... ..	121
(i) Purpose and scope of service testing and discussion of as- sociated problems ... ..	121
(ii) Fundamental characteristics which should be tested ... ..	122
(iii) Types of commercial testers ... ..	122
(iv) Methods of testing characteristics in commercial service testers	123
(a) Shorts testing ... ..	123
(b) Continuity testing ... ..	123
(c) Heater to cathode leakage ... ..	123
(d) Emission testing ... ..	123
(e) Mutual conductance testing ... ..	123
(f) Plate conductance testing ... ..	124
(g) Reverse grid current testing ... ..	124
(h) Power output testing ... ..	124
(i) Conversion conductance testing ... ..	124
(j) Oscillator mutual conductance testing ... ..	124
(k) Noise testing ... ..	124
(l) A.C. amplification testing ... ..	124
(v) A.C. versus d.c. electrode voltages in testers ... ..	124
(vi) Pre-heating ... ..	125
(vii) Testing procedure ... ..	125
6. REFERENCES ... ..	125

## PART 2: GENERAL THEORY AND COMPONENTS

### CHAPTER 4. THEORY OF NETWORKS

1. CURRENT AND VOLTAGE ... ..	128
(i) Direct current ... ..	128
(ii) Alternating current ... ..	129
(iii) Indications of polarity and current flow ... ..	130
2. RESISTANCE ... ..	130
(i) Ohm's Law for d.c. ... ..	130
(ii) Ohm's Law for a.c. ... ..	131
(iii) Resistances in series ... ..	131
(iv) Resistances in parallel ... ..	132
(v) Conductance in resistive circuits ... ..	133

# CONTENTS

SECTION	PAGE
3. POWER ... ..	133
(i) Power in d.c. circuits ... ..	133
(ii) Power in resistive a.c. circuits... ..	133
4. CAPACITANCE ... ..	134
(i) Introduction to capacitance ... ..	134
(ii) Condensers in parallel and series ... ..	135
(iii) Calculation of capacitance ... ..	135
(iv) Condensers in d.c. circuits ... ..	136
(v) Condensers in a.c. circuits ... ..	137
5. INDUCTANCE ... ..	140
(i) Introduction to inductance ... ..	140
(ii) Inductances in d.c. circuits ... ..	141
(iii) Inductances in series and parallel ... ..	141
(iv) Mutual inductance ... ..	142
(v) Inductances in a.c. circuits ... ..	142
(vi) Power in inductive circuits ... ..	143
6. IMPEDANCE AND ADMITTANCE ... ..	144
(i) Impedance, a complex quantity ... ..	144
(ii) Series circuits with L, C and R ... ..	144
(iii) Parallel combinations of L, C and R ... ..	147
(iv) Series-parallel combinations of L, C and R... ..	149
(v) Conductance, susceptance and admittance ... ..	153
(vi) Conversion from series to parallel impedance ... ..	157
7. NETWORKS ... ..	158
(i) Introduction to networks ... ..	158
(ii) Kirchhoff's Laws ... ..	160
(iii) Potential dividers ... ..	161
(iv) Thevenin's Theorem ... ..	164
(v) Norton's Theorem ... ..	165
(vi) Maximum Power Transfer Theorem ... ..	165
(vii) Reciprocity Theorem ... ..	165
(viii) Superposition Theorem... ..	165
(ix) Compensation Theorem... ..	166
(x) Four-terminal networks... ..	166
(xi) Multi-mesh networks ... ..	167
(xii) Non-linear components in networks ... ..	170
(xiii) Phase shift networks ... ..	170
(xiv) Transients in networks ... ..	171
(xv) References to networks ... ..	171
8. FILTERS ... ..	172
(i) Introduction to filters ... ..	172
(ii) Resistance-capacitance filters, high-pass and low-pass ... ..	172
(iii) Special types of resistance-capacitance filters ... ..	176
(iv) Iterative impedances of four terminal networks ... ..	176
(v) Image impedances and image transfer constant of four terminal networks ... ..	177
(vi) Symmetrical networks ... ..	179
(vii) "Constant k" filters ... ..	179
(viii) M-derived filters ... ..	182
(ix) Practical filters ... ..	184
(x) Frequency dividing networks ... ..	184
(xi) References to filters ... ..	185

## CONTENTS

SECTION	PAGE
9. PRACTICAL RESISTORS, CONDENSERS AND INDUCTORS ... ..	186
(i) Practical resistors ... ..	186
(ii) Practical condensers ... ..	191
(iii) Combination units ... ..	197
(iv) Practical inductors ... ..	197
(v) References to practical resistors and condensers ... ..	198
<b>CHAPTER 5. TRANSFORMERS AND IRON-CORED INDUCTORS</b>	
1. IDEAL TRANSFORMERS ... ..	199
(i) Definitions ... ..	199
(ii) Impedance calculations—single load ... ..	200
(iii) Impedance calculations—multiple loads ... ..	201
2. PRACTICAL TRANSFORMERS ... ..	204
(i) General considerations ... ..	204
(ii) Effects of losses ... ..	205
3. AUDIO-FREQUENCY TRANSFORMERS ... ..	206
(i) General considerations ... ..	206
(ii) Core materials ... ..	207
(iii) Frequency response and distortion	
(a) Interstage transformers ... ..	209
(b) Low level transformers ... ..	210
(c) Output transformers ... ..	211
(iv) Designing for low leakage inductance ... ..	217
(v) Winding capacitance ... ..	219
(vi) Tests on output transformers ... ..	227
(vii) Specifications for a-f transformers ... ..	228
4. MAGNETIC CIRCUIT THEORY ... ..	229
(i) Fundamental magnetic relationships ... ..	229
(ii) The magnetic circuit ... ..	231
(iii) Magnetic units and conversion factors ... ..	232
5. POWER TRANSFORMERS... ..	233
(i) General ... ..	233
(ii) Core material and size ... ..	234
(iii) Primary and secondary turns ... ..	235
(iv) Currents in windings ... ..	236
(v) Temperature rise ... ..	236
(vi) Typical design ... ..	237
(vii) Specifications for power transformers ... ..	241
6. IRON-CORED INDUCTORS ... ..	242
(i) General ... ..	242
(ii) Calculations—general ... ..	242
(iii) Effective permeability ... ..	243
(iv) Design with no d.c. flux ... ..	243
(v) Design of high Q inductors ... ..	245
(vi) Design with d.c. flux ... ..	247
(vii) Design by Hanna's method ... ..	248
(viii) Design of inductors for choke-input filters ... ..	249
(ix) Measurements ... ..	250
(x) Iron-cored inductors in resonant circuits ... ..	251
7. REFERENCES ... ..	252



## CHAPTER 6. MATHEMATICS

1. ARITHMETIC AND THE SLIDE RULE ... .. .	255
(i) Figures ... .. .	255
(ii) Powers and roots ... .. .	255
(iii) Logarithms ... .. .	255
(iv) The slide rule ... .. .	257
(v) Short cuts in arithmetic ... .. .	258
2. ALGEBRA ... .. .	259
(i) Addition ... .. .	260
(ii) Subtraction ... .. .	260
(iii) Multiplication ... .. .	260
(iv) Division ... .. .	260
(v) Powers ... .. .	260
(vi) Roots ... .. .	261
(vii) Brackets and simple manipulations ... .. .	261
(viii) Factoring ... .. .	262
(ix) Proportion ... .. .	262
(x) Variation ... .. .	262
(xi) Inequalities ... .. .	262
(xii) Functions ... .. .	263
(xiii) Equations ... .. .	263
(xiv) Formulae and laws ... .. .	265
(xv) Continuity and limits ... .. .	265
(xvi) Progressions, sequences and series ... .. .	266
(xvii) Logarithmic and exponential functions ... .. .	267
(xviii) Infinite series ... .. .	268
(xix) Hyperbolic functions ... .. .	269
(xx) General approximations ... .. .	271
3. GEOMETRY AND TRIGONOMETRY ... .. .	272
(i) Plane figures ... .. .	272
(ii) Surfaces and volumes of solids ... .. .	275
(iii) Trigonometrical relationships ... .. .	275
4. PERIODIC PHENOMENA ... .. .	278
5. GRAPHICAL REPRESENTATION AND $j$ NOTATION ... .. .	279
(i) Graphs ... .. .	279
(ii) Finding the equation to a curve ... .. .	281
(iii) Three variables ... .. .	281
(iv) Vectors and $j$ notation ... .. .	282
6. COMPLEX ALGEBRA AND DE MOIVRE'S THEOREM ... .. .	285
(i) Complex algebra with regular coordinates ... .. .	285
(ii) Complex algebra with polar coordinates ... .. .	286
(iii) De Moivre's Theorem ... .. .	287
7. DIFFERENTIAL AND INTEGRAL CALCULUS ... .. .	289
(i) Slope and rate of change ... .. .	289
(ii) Differentiation ... .. .	291
(iii) Integration ... .. .	294
(iv) Taylor's Series ... .. .	298
(v) Maclaurin's Series ... .. .	299
8. FOURIER SERIES AND HARMONICS ... .. .	299
(i) Periodic waves and the Fourier Series ... .. .	299
(ii) Other applications of the Fourier Series ... .. .	302
(iii) Graphical Harmonic Analysis ... .. .	302
9. REFERENCES ... .. .	304

# CONTENTS

SECTION

PAGE

## CHAPTER 7. NEGATIVE FEEDBACK

1.	FUNDAMENTAL TYPES OF FEEDBACK ... ..	306
	(i) Feedback positive and negative ... ..	306
	(ii) Negative voltage feedback at the mid-frequency ... ..	307
	(iii) Negative current feedback at the mid-frequency ... ..	312
	(iv) Bridge negative feedback at the mid-frequency ... ..	313
	(v) Combined positive and negative at the mid-frequency ... ..	314
	(vi) Comparison between different fundamental types at the mid-frequency ... ..	315
2.	PRACTICAL FEEDBACK CIRCUITS ... ..	316
	(i) The cathode follower ... ..	316
	(ii) The cathode degenerative amplifier and phase splitter ... ..	327
	(iii) Voltage feedback from secondary of output transformer ... ..	330
	(iv) Voltage feedback from plate—transformer input ... ..	332
	(v) Voltage feedback from plate—r.c.c. input ... ..	332
	(vi) Voltage feedback over two stages ... ..	334
	(vii) Voltage feedback over three stages ... ..	344
	(viii) Cathode coupled phase inverters and amplifiers ... ..	347
	(ix) Hum ... ..	348
	(x) Some special features of feedback amplifiers ... ..	352
	(xi) Combined positive and negative feedback ... ..	352
	(xii) Choke-coupled phase inverter ... ..	355
3.	STABILITY, PHASE SHIFT AND FREQUENCY RESPONSE ... ..	356
	(i) Stability and instability... ..	356
	(ii) Conditions for stability... ..	356
	(iii) Relationship between phase shift and attenuation ... ..	359
	(iv) Design of 1 and 2 stage amplifiers ... ..	364
	(v) Design of multistage amplifiers ... ..	365
	(vi) Effect of feedback on frequency response ... ..	378
	(vii) Design of amplifiers with flat frequency response ... ..	379
	(viii) Constancy of characteristics with feedback ... ..	388
	(ix) Effect of feedback on phase shift ... ..	389
4.	SPECIAL APPLICATIONS OF FEEDBACK ... ..	389
5.	VALVE CHARACTERISTICS AND FEEDBACK ... ..	390
	(i) Triode cathode follower ... ..	390
	(ii) Pentode cathode follower ... ..	393
	(iii) Triode with voltage feedback ... ..	394
	(iv) Pentode with voltage feedback, transformer coupled ... ..	395
	(v) Cathode degenerative triode ... ..	397
	(vi) Cathode degenerative pentode ... ..	399
	(vii) Cathode-coupled triodes ... ..	399
	(viii) Feedback over two stages ... ..	399
6.	REFERENCES TO FEEDBACK ... ..	399
7.	OVERLOADING OF FEEDBACK AMPLIFIERS ON TRANSIENTS ... ..	1475

## CHAPTER 8. WAVE MOTION AND THE THEORY OF MODULATION

1.	INTRODUCTION TO ELECTROMAGNETIC WAVES ... ..	403
	(i) Wave motion ... ..	403
	(ii) Electromagnetic spectrum ... ..	404
	(iii) Wave propagation ... ..	404
2.	TRANSMISSION OF INTELLIGENCE ... ..	405
	(i) Introduction ... ..	405
	(ii) Radio telegraphy... ..	405
	(iii) Radio telephony ... ..	405
3.	REFERENCES ... ..	406

## CONTENTS

SECTION

PAGE

### CHAPTER 9. TUNED CIRCUITS

1.	INTRODUCTION ... ..	407
2.	DAMPED OSCILLATIONS ... ..	408
3.	SERIES RESONANCE ... ..	409
4.	PARALLEL RESONANCE ... ..	410
5.	GENERAL CASE OF SERIES RESONANCE ... ..	412
6.	SELECTIVITY AND GAIN ... ..	412
	(i) Single tuned circuit ... ..	412
	(ii) Coupled circuits—tuned secondary ... ..	413
	(iii) Coupled circuits—tuned primary, tuned secondary... ..	414
	(iv) Coupled circuits of equal Q ... ..	415
	(v) Coupled circuits of unequal Q ... ..	416
7.	SELECTIVITY—GRAPHICAL METHODS ... ..	416
	(i) Single tuned circuit ... ..	416
	(ii) Two identical coupled tuned circuits... ..	417
8.	COUPLING OF CIRCUITS ... ..	418
	(i) Mutual inductive coupling ... ..	418
	(ii) Miscellaneous methods of coupling ... ..	418
	(iii) Complex coupling ... ..	420
9.	RESPONSE OF IDENTICAL AMPLIFIER STAGES IN CASCADE ... ..	421
10.	UNIVERSAL SELECTIVITY CURVES ... ..	421
11.	SUMMARY OF FORMULAE FOR TUNED CIRCUITS ... ..	423
12.	REFERENCES ... ..	427

### CHAPTER 10. CALCULATION OF INDUCTANCE

1.	SINGLE LAYER COILS OR SOLENOIDS ... ..	429
	(i) Current-sheet inductance ... ..	429
	(ii) Solenoids wound with spaced round wires ... ..	430
	(iii) Approximate formulae ... ..	432
	(iv) Design of single layer solenoid ... ..	433
	(v) Magnitude of the differences between $L_s$ and $L_o$ ... ..	435
	(vi) Curves for the determination of the "current-sheet" inductance ... ..	437
	(vii) Effect of concentric, non-magnetic screen ... ..	438
2.	MULTILAYER SOLENOIDS ... ..	441
	(i) Formula for current sheet inductance ... ..	441
	(ii) Correction for insulation thickness ... ..	442
	(iii) Approximate formulae ... ..	442
	(iv) Design of multilayer coils ... ..	443
	(v) Effect of a concentric screen ... ..	444
3.	TOROIDAL COILS ... ..	445
	(i) Toroidal coil of circular section with single layer winding ... ..	445
	(ii) Toroidal coil of rectangular section with single layer winding ... ..	445
	(iii) Toroidal coil of rectangular section with multilayer winding ... ..	445
4.	FLAT SPIRALS ... ..	445
	(i) Accurate formulae ... ..	445
	(ii) Approximate formulae ... ..	446
5.	MUTUAL INDUCTANCE ... ..	446
	(i) Accurate methods ... ..	446
	(ii) Approximate methods ... ..	448
6.	LIST OF SYMBOLS ... ..	448
7.	REFERENCES ... ..	448

## CONTENTS

SECTION	PAGE
<b>CHAPTER 11. DESIGN OF RADIO FREQUENCY INDUCTORS</b>	
1. INTRODUCTION ... ..	450
2. SELF-CAPACITANCE OF COILS ... ..	451
(i) Effects of self-capacitance ... ..	451
(ii) Calculation of self-capacitance of single-layer solenoids ... ..	451
(iii) Measurement of self-capacitance ... ..	453
3. INTERMEDIATE-FREQUENCY WINDINGS ... ..	453
(i) Air-cored coils ... ..	453
(ii) Iron-cored coils ... ..	454
(iii) Expanding selectivity i-f transformers ... ..	455
(iv) Calculation of gear ratios for universal coils ... ..	456
(v) Miscellaneous considerations ... ..	458
4. MEDIUM WAVE-BAND COILS ... ..	459
(i) Air-cored coils ... ..	459
(ii) Iron-cored coils ... ..	460
(iii) Permeability tuning ... ..	461
(iv) Matching ... ..	462
5. SHORT-WAVE COILS ... ..	463
(i) Design ... ..	463
(ii) Miscellaneous features ... ..	468
6. RADIO-FREQUENCY CHOKES ... ..	474
(i) Pie-wound chokes ... ..	474
(ii) Other types ... ..	475
7. TROPIC PROOFING ... ..	476
(i) General considerations ... ..	476
(ii) Baking ... ..	476
(iii) Impregnation ... ..	477
(iv) Flash dipping ... ..	477
(v) Materials ... ..	477
8. REFERENCES ... ..	478

## PART 3: AUDIO FREQUENCIES

<b>CHAPTER 12. AUDIO FREQUENCY VOLTAGE AMPLIFIERS</b>	
1. INTRODUCTION ... ..	481
(i) Voltage amplifiers ... ..	481
2. RESISTANCE-CAPACITANCE COUPLED TRIODES ... ..	482
(i) Choice of operating conditions ... ..	482
(ii) Coupling condenser ... ..	483
(iii) Cathode bias ... ..	484
(iv) Fixed bias ... ..	487
(v) Grid leak bias ... ..	489
(vi) Plate voltage and current ... ..	489
(vii) Gain and distortion at the mid-frequency ... ..	490
(viii) Dynamic characteristics ... ..	491
(ix) Maximum voltage output and distortion ... ..	491
(x) Conversion factors with r.c.c. triodes ... ..	493
(xi) Input impedance and Miller effect ... ..	493
(xii) Equivalent circuit of r.c.c. triode ... ..	494
(xiii) Voltage gain and phase shift ... ..	494
(xiv) Comments on tabulated characteristics of resistance-coupled triodes ... ..	495

## CONTENTS

SECTION	PAGE
3. RESISTANCE-CAPACITANCE COUPLED PENTODES ... .. .	496
(i) Choice of operating conditions ... .. .	496
(ii) Coupling condenser ... .. .	496
(iii) Screen by-pass ... .. .	496
(iv) Cathode bias ... .. .	499
(v) Fixed bias ... .. .	501
(vi) Dynamic characteristics of pentodes ... .. .	504
(vii) Gain at the mid-frequency ... .. .	506
(viii) Dynamic characteristics of pentodes and comparison with triodes ... .. .	508
(ix) Maximum voltage output and distortion ... .. .	510
(x) Conversion factors with r.c.c. pentodes ... .. .	511
(xi) Equivalent circuit of r.c.c. pentode ... .. .	512
(xii) Voltage gain and phase shift ... .. .	512
(xiii) Screen loadlines ... .. .	513
(xiv) Combined screen and cathode loadlines and the effect of tolerances ... .. .	515
(xv) Remote cut-off pentodes as r.c.c. amplifiers ... .. .	516
(xvi) Multigrid valves as r.c.c. amplifiers ... .. .	516
(xvii) Special applications ... .. .	516
(xviii) Comments on tabulated characteristics of resistance-coupled pentodes ... .. .	517
4. TRANSFORMER-COUPLED VOLTAGE AMPLIFIERS ... .. .	517
(i) Introduction ... .. .	517
(ii) Gain at the mid-frequency ... .. .	517
(iii) Gain at low frequencies ... .. .	517
(iv) Desirable valve characteristics ... .. .	517
(v) Equivalent circuits ... .. .	518
(vi) Gain and phase shift at all frequencies ... .. .	518
(vii) Transformer characteristics ... .. .	518
(viii) Fidelity ... .. .	518
(ix) Valve loadlines ... .. .	518
(x) Maximum peak output voltage ... .. .	518
(xi) Transformer loading ... .. .	518
(xii) Parallel feed ... .. .	518
(xiii) Auto-transformer coupling ... .. .	520
(xiv) Applications ... .. .	520
(xv) Special applications ... .. .	520
5. CHOKE-COUPLED AMPLIFIERS ... .. .	521
(i) Performance ... .. .	521
(ii) Application ... .. .	521
6. METHODS OF EXCITING PUSH-PULL AMPLIFIERS ... .. .	521
(i) Methods involving iron-cored inductors ... .. .	521
(ii) Phase splitter ... .. .	522
(iii) Phase inverter ... .. .	524
(iv) Self-balancing phase inverter ... .. .	524
(v) Self-balancing paraphase inverter ... .. .	524
(vi) Common cathode impedance self-balancing inverters ... .. .	526
(vii) Balanced output amplifiers with highly accurate balance ... .. .	527
(viii) Cross coupled phase inverter ... .. .	527
7. PUSH-PULL VOLTAGE AMPLIFIERS ... .. .	527
(i) Introduction ... .. .	527
(ii) Cathode resistors ... .. .	527
(iii) Output circuit ... .. .	527
(iv) Push-pull impedance-coupled amplifiers—mathematical treatment ... .. .	528
(v) Phase compressor ... .. .	528

## CONTENTS

SECTION	PAGE
8. IN-PHASE AMPLIFIERS ... ..	529
(i) Cathode-coupled amplifiers ... ..	529
(ii) Grounded-grid amplifiers ... ..	529
(iii) Inverted input amplifiers ... ..	529
(iv) Other forms of in-phase amplifiers ... ..	529
9. DIRECT-COUPLED AMPLIFIERS... ..	529
(i) Elementary d-c amplifiers ... ..	529
(ii) Bridge circuit ... ..	530
(iii) Cathode-coupled ... ..	531
(iv) Cathode follower ... ..	531
(v) Phase inverter ... ..	532
(vi) Screen coupled ... ..	532
(vii) Gas tube coupled ... ..	532
(viii) Modulation systems ... ..	532
(ix) Compensated d.c. amplifiers ... ..	533
(x) Bridge-balanced direct current amplifiers ... ..	533
(xi) Cascode amplifiers ... ..	533
10. STABILITY, DECOUPLING AND HUM ... ..	535
(i) Effect of common impedance in power supply ... ..	535
(ii) Plate supply by-passing ... ..	535
(iii) Plate circuit decoupling ... ..	535
(iv) Screen circuit decoupling ... ..	537
(v) Grid circuit decoupling ... ..	538
(vi) Hum in voltage amplifiers ... ..	538
11. TRANSIENTS AND PULSES IN AUDIO FREQUENCY AMPLIFIERS ... ..	540
(i) Transient distortion ... ..	540
(ii) Rectangular pulses ... ..	540
12. MULTISTAGE VOLTAGE AMPLIFIERS ... ..	541
(i) Single-channel amplifiers ... ..	541
(ii) Multi-channel amplifiers ... ..	541
13. REFERENCES ... ..	542

## CHAPTER 13. AUDIO FREQUENCY POWER AMPLIFIERS

1. INTRODUCTION ... ..	544
(i) Types of a-f power amplifiers ... ..	544
(ii) Class of operation ... ..	545
(iii) Some characteristics of power amplifiers ... ..	545
(iv) Effect of power supply on power amplifiers ... ..	547
2. CLASS A SINGLE TRIODES ... ..	548
(i) Simplified graphical conditions, power output and distortion ... ..	548
(ii) General graphical case, power output and distortion ... ..	550
(iii) Optimum operating conditions... ..	555
(iv) Loudspeaker load ... ..	558
(v) Plate circuit efficiency and power dissipation ... ..	559
(vi) Power sensitivity ... ..	559
(vii) Choke-coupled amplifier ... ..	559
(viii) Effect of a.c. filament supply ... ..	560
(ix) Overloading ... ..	560
(x) Regulation and by-passing of power supply... ..	560

# CONTENTS

SECTION	PAGE
3. CLASS A MULTI-GRID VALVES ... ..	560
(i) Introduction ... ..	560
(ii) Ideal pentodes ... ..	561
(iii) Practical pentodes—operating conditions ... ..	561
(iv) Graphical analysis—power output and distortion ... ..	563
(v) Rectification effects ... ..	565
(vi) Cathode bias ... ..	565
(vii) Resistance and inductance of transformer primary ... ..	566
(viii) Loudspeaker load ... ..	566
(ix) Effects of plate and screen regulation ... ..	568
(x) Beam power valves ... ..	569
(xi) Space charge tetrodes ... ..	569
(xii) Partial triode (“ ultra-linear ”) operation of pentodes ... ..	570
4. PARALLEL CLASS A AMPLIFIERS ... ..	570
5. PUSH-PULL TRIODES CLASS A, AB <sub>1</sub> ... ..	571
(i) Introduction ... ..	571
(ii) Theory of push-pull amplification ... ..	573
(iii) Power output and distortion ... ..	577
(iv) Average plate current ... ..	579
(v) Matching and the effects of mismatching ... ..	580
(vi) Cathode bias ... ..	582
(vii) Parasitics ... ..	582
6. PUSH-PULL PENTODES AND BEAM POWER AMPLIFIERS, CLASS A, AB <sub>1</sub> ... ..	583
(i) Introduction ... ..	583
(ii) Power output and distortion ... ..	583
(iii) The effect of power supply regulation ... ..	584
(iv) Matching and the effects of mismatching ... ..	584
(v) Average plate and screen currents ... ..	584
(vi) Cathode bias ... ..	585
(vii) Parasitics ... ..	585
(viii) Phase inversion in the power stage ... ..	585
(ix) Extended Class A ... ..	587
(x) Partial triode (“ ultra-linear ”) operation ... ..	587
7. CLASS B AMPLIFIERS AND DRIVERS ... ..	587
(i) Introduction ... ..	587
(ii) Power output and distortion—ideal conditions—Class B <sub>2</sub> ... ..	588
(iii) Power output and distortion—practical conditions—Class B <sub>2</sub> ... ..	588
(iv) Grid driving conditions... ..	590
(v) Design procedure for Class B <sub>2</sub> amplifiers ... ..	592
(vi) Earthed-grid cathode coupled amplifiers ... ..	592
(vii) Class B <sub>1</sub> amplifiers—quiescent push-pull ... ..	592
8. CLASS AB <sub>2</sub> AMPLIFIERS ... ..	593
(i) Introduction ... ..	593
(ii) Bias and screen stabilized Class AB <sub>2</sub> amplifier ... ..	593
(iii) McIntosh amplifier ... ..	594
9. CATHODE-FOLLOWER POWER AMPLIFIERS ... ..	596
10. SPECIAL FEATURES ... ..	596
(i) Grid circuit resistance ... ..	596
(ii) Grid bias sources ... ..	597
(iii) Miller Effect ... ..	598
(iv) 26 volt operation ... ..	598
(v) Hum from plate and screen supplies... ..	599
11. COMPLETE AMPLIFIERS ... ..	599
(i) Introduction ... ..	599
(ii) Design procedure and examples ... ..	599
(iii) Loudspeaker load ... ..	600
12. REFERENCES ... ..	601

CONTENTS

SECTION

PAGE

CHAPTER 14. FIDELITY AND DISTORTION

1. INTRODUCTION ... ..	603
(i) Fidelity ... ..	603
(ii) Types of distortion ... ..	604
(iii) Imagery for describing reproduced sound ... ..	604
2. NON-LINEAR DISTORTION AND HARMONICS... ..	605
(i) Non-linearity ... ..	605
(ii) Harmonics... ..	606
(iii) Permissible harmonic distortion ... ..	607
(iv) Total harmonic distortion ... ..	609
(v) Weighted distortion factor ... ..	610
(vi) The search for a true criterion of non-linearity ... ..	610
3. INTERMODULATION DISTORTION ... ..	611
(i) Introduction ... ..	611
(ii) Modulation method of measurement—r.m.s. sum ... ..	612
(iii) Difference frequency intermodulation method ... ..	613
(iv) Individual side-band method ... ..	613
(v) Modulation method of measurement—peak sum ... ..	614
(vi) Le Bel's oscillographic method ... ..	614
(vii) Comparison between different methods ... ..	616
(viii) Synthetic bass ... ..	616
4. FREQUENCY DISTORTION ... ..	617
(i) Frequency range ... ..	617
(ii) Tonal balance ... ..	617
(iii) Minimum audible change in frequency range ... ..	617
(iv) Sharp peaks ... ..	618
5. PHASE DISTORTION ... ..	618
6. TRANSIENT DISTORTION ... ..	619
(i) General survey ... ..	619
(ii) Testing for transient response ... ..	619
7. DYNAMIC RANGE AND ITS LIMITATIONS ... ..	620
(i) Volume range and hearing ... ..	620
(ii) Effect of volume level on frequency range ... ..	621
(iii) Acoustical power and preferred listening levels ... ..	623
(iv) Volume range in musical reproduction ... ..	623
(v) The effect of noise ... ..	624
8. SCALE DISTORTION ... ..	625
9. OTHER FORMS OF DISTORTION ... ..	626
(i) Frequency-modulation distortion ... ..	626
(ii) Variation of frequency response with output level ... ..	626
(iii) Listener fatigue ... ..	626
10. FREQUENCY RANGE PREFERENCES ... ..	627
(i) Tests by Chinn and Eisenberg ... ..	627
(ii) Tests by Olson ... ..	627
(iii) Single channel versus dual-channel tests ... ..	627
(iv) Summing up ... ..	628
11. SPEECH REPRODUCTION ... ..	628
(i) The characteristics of speech ... ..	628
(ii) Articulation ... ..	628
(iii) Masking of speech by noise ... ..	629
(iv) Distortion in speech reproduction ... ..	629
(v) Frequency ranges for speech ... ..	630



## CONTENTS

SECTION	PAGE
12. HIGH FIDELITY REPRODUCTION ... ..	630
(i) The target of high fidelity ... ..	630
(ii) Practicable high fidelity... ..	630
(iii) The ear as a judge of fidelity... ..	632
13. REFERENCES ... ..	632

## CHAPTER 15. TONE COMPENSATION AND TONE CONTROL

1. INTRODUCTION ... ..	635
(i) The purpose of tone compensation ... ..	635
(ii) Tone control ... ..	636
(iii) General considerations ... ..	636
(iv) Distortion due to tone control ... ..	636
(v) Calculations involving decibels per octave ... ..	637
(vi) Attenuation expressed as a time constant ... ..	638
(vii) The elements of tone control filters ... ..	639
(viii) Fundamental circuit incorporating R and C ... ..	639
(ix) Damping of tuned circuits ... ..	639
(x) Tolerances of elements ... ..	639
2. BASS BOOSTING ... ..	640
(i) General remarks ... ..	640
(ii) Circuits not involving resonance or negative feedback ... ..	640
(iiii) Methods incorporating resonant circuits ... ..	644
(iv) Circuits involving feedback ... ..	645
(v) Regeneration due to negative resistance characteristic ... ..	648
3. BASS ATTENUATION ... ..	649
(i) General remarks ... ..	649
(ii) Bass attenuation by grid coupling condensers ... ..	649
(iiii) Bass attenuation by cathode resistor by-passing ... ..	649
(iv) Bass attenuation by screen by-passing ... ..	650
(v) Bass attenuation by reactance shunting ... ..	650
(vi) Bass attenuation by negative feedback ... ..	651
(vii) Bass attenuation by Parallel-T network ... ..	651
(viii) Bass attenuation using Constant k filters ... ..	652
(ix) Bass attenuation using M-derived filters ... ..	652
4. COMBINED BASS TONE CONTROLS ... ..	653
(i) Stepped controls ... ..	653
(ii) Continuously variable controls ... ..	653
5. TREBLE BOOSTING ... ..	653
(i) General remarks ... ..	653
(ii) Circuits not involving resonance or negative feedback ... ..	653
(iiii) Methods incorporating resonant circuits ... ..	654
(iv) Circuits involving feedback ... ..	655
6. TREBLE ATTENUATION ... ..	655
(i) General remarks ... ..	655
(ii) Attenuation by shunt capacitance ... ..	655
(iiii) Treble attenuation by filter networks ... ..	657
(iv) Treble attenuation in negative feedback amplifiers ... ..	657
7. COMBINED TREBLE TONE CONTROLS ... ..	658
8. COMBINED BASS AND TREBLE TONE CONTROLS ... ..	658
(i) Stepped controls—general ... ..	658
(ii) Quality switch ... ..	659
(iiii) Universal step-type tone control not using inductors ... ..	660
(iv) Universal step-type tone control using inductors ... ..	661
(v) Fixed bass and treble boosting ... ..	662

## CONTENTS

SECTION	PAGE
(vi) Step-type tone control using negative feedback ... ..	662
(vii) Continuously-variable controls—general ... ..	662
(viii) Single control continuously-variable tone controls ... ..	662
(ix) Ganged continuously-variable tone controls ... ..	664
(x) Dual control continuously-variable tone controls ... ..	664
9. FEEDBACK TO PROVIDE TONE CONTROL ... ..	669
(i) Introduction ... ..	669
(ii) Amplifiers with feedback providing tone control ... ..	669
(iii) Whistle filters using feedback ... ..	672
10. AUTOMATIC FREQUENCY-COMPENSATED TONE CONTROL ... ..	672
(i) Introduction ... ..	672
(ii) Methods incorporating a tapped potentiometer ... ..	672
(iii) Methods incorporating step-type controls ... ..	673
(iv) Method incorporating inverse volume expansion with multi-channel amplifier ... ..	673
11. WHISTLE FILTERS ... ..	673
(i) Resonant circuit filters ... ..	673
(ii) Narrow band rejection filter ... ..	675
(iii) Crystal filters ... ..	675
(iv) Parallel-T network ... ..	675
(v) Filters incorporating L and C ... ..	676
12. OTHER METHODS OF TONE CONTROL ... ..	676
(i) Multiple-channel amplifiers ... ..	676
(ii) Synthetic bass ... ..	676
13. THE LISTENER AND TONE CONTROL ... ..	677
14. EQUALIZER NETWORKS ... ..	677
15. REFERENCES ... ..	677

## CHAPTER 16. VOLUME EXPANSION, COMPRESSION AND LIMITING

1. GENERAL PRINCIPLES ... ..	679
(i) Introduction ... ..	679
(ii) An ideal system ... ..	680
(iii) Practical problems in volume expansion ... ..	680
(iv) Distortion ... ..	681
(v) General comments ... ..	681
2. VOLUME COMPRESSION ... ..	681
(i) Introduction ... ..	681
(ii) Peak limiters ... ..	682
(iii) Volume limiters ... ..	683
(iv) Distortion caused by peak limiters or volume limiters ... ..	683
(v) Volume compression ... ..	683
(vi) Volume compression plus limiting ... ..	684
(vii) Compression of commercial speech ... ..	684
3. GAIN CONTROL DEVICES ... ..	684
(i) Remote cut-off pentodes ... ..	684
(ii) Pentagrids and triode-hexodes ... ..	685
(iii) Plate resistance control ... ..	685
(iv) Negative feedback ... ..	685
(v) Lamps ... ..	685
(vi) Suppressor-grid control ... ..	686

## CONTENTS

SECTION	PAGE
4. VOLUME EXPANSION ... .. .	686
(i) Introduction ... .. .	686
(ii) Expanders incorporating lamps ... .. .	687
(iiii) Expanders utilizing feedback ... .. .	688
(iv) Expanders incorporating remote cut-off pentodes ... .. .	688
(v) Expanders incorporating remote cut-off triodes ... .. .	689
(vi) Expanders incorporating suppressor-grid controlled pentodes ... .. .	689
(vii) Expanders incorporating valves with five grids ... .. .	691
(viii) Expanders incorporating plate resistance control ... .. .	692
5. PUBLIC ADDRESS A.V.C. ... .. .	693
6. SPEECH CLIPPERS ... .. .	693
7. NOISE PEAK AND OUTPUT LIMITERS ... .. .	694
(i) Introduction ... .. .	694
(ii) Instantaneous noise peak limiters ... .. .	694
(iiii) Output limiters ... .. .	698
(iv) General remarks ... .. .	699
8. REFERENCES ... .. .	699

## CHAPTER 17. REPRODUCTION FROM RECORDS

1. INTRODUCTION TO DISC RECORDING ... .. .	701
(i) Methods used in sound recording ... .. .	701
(ii) Principles of lateral recording ... .. .	702
(iiii) Frequency range ... .. .	704
(iv) Surface noise and dynamic range ... .. .	704
(v) Processing... .. .	705
(vi) Turntables and driving mechanism ... .. .	705
(vii) Automatic record changers ... .. .	705
2. DISCS AND STYLI ... .. .	706
(i) General information on discs ... .. .	706
(ii) Dimensions of records and grooves ... .. .	706
(iiii) Styli ... .. .	709
(iv) Pinch effect ... .. .	711
(v) Radius compensation ... .. .	711
(vi) Record and stylus wear ... .. .	712
3. PICKUPS ... .. .	714
(i) General survey ... .. .	714
(ii) Electro-magnetic (moving iron) pickups ... .. .	717
(iiii) Dynamic (moving coil) pickups ... .. .	719
(iv) Piezo-electric (crystal) pickups... .. .	720
(v) Magnetostriction pickups ... .. .	721
(vi) Strain-sensitive pickups ... .. .	721
(vii) Ribbon pickups ... .. .	722
(viii) Capacitance pickups ... .. .	722
(ix) Eddy-current pickups ... .. .	723
4. TRACKING ... .. .	723
(i) General survey of the problem ... .. .	723
(ii) How to design for minimum distortion ... .. .	725
(iiii) The influence of stylus friction ... .. .	726
5. RECORDING CHARACTERISTICS, EQUALIZERS AND AMPLIFIERS ... .. .	727
(i) Recording characteristics ... .. .	727
(ii) Pre-amplifiers for use with pickups ... .. .	732
(iiii) Introduction to equalizers ... .. .	732
(iv) High-frequency attenuation (scratch filter) ... .. .	737
(v) Equalizers for electro-magnetic pickups ... .. .	738

SECTION	CONTENTS	PAGE
	(vi) Equalizers for crystal pickups ... ..	741
	(vii) Equalizers applying negative feedback to the pickup ... ..	743
	(viii) Miscellaneous details regarding equalizing amplifiers ... ..	743
	(ix) Complete amplifiers ... ..	744
	(x) Pickups for connection to radio receivers ... ..	751
	(xi) Frequency test records ... ..	752
6.	DISTORTION AND UNDESIRABLE EFFECTS ... ..	757
	(i) Tracing distortion and pinch effect ... ..	757
	(ii) Playback loss ... ..	760
	(iii) Wow, and the effects of record warping ... ..	760
	(iv) Distortion due to stylus wear ... ..	761
	(v) Noise modulation ... ..	761
	(vi) Pickup distortion ... ..	762
	(vii) Acoustical radiation ... ..	762
	(viii) Distortion in recording ... ..	762
7.	NOISE REDUCTION ... ..	763
	(i) Analysis of noise ... ..	763
	(ii) High-frequency attenuation ... ..	763
	(iii) High-frequency pre-emphasis and de-emphasis ... ..	763
	(iv) Volume expansion ... ..	763
	(v) Olson noise suppressor ... ..	763
	(vi) Scott dynamic noise suppressor ... ..	764
	(vii) Price balanced clipper noise suppressor ... ..	765
8.	LACQUER DISC HOME RECORDING (DIRECT PLAYBACK) ... ..	766
	(i) General description ... ..	766
	(ii) Recording characteristic ... ..	766
	(iii) Cutting stylus ... ..	767
	(iv) Cutter head ... ..	767
	(v) Equalization of cutter ... ..	767
	(vi) Motor and turntable ... ..	767
	(vii) Amplifier ... ..	767
	(viii) Pickups for use on lacquer discs ... ..	768
	(ix) Recording with embossed groove ... ..	768
9.	REPRODUCTION FROM TRANSCRIPTION DISCS ... ..	769
	(i) Introduction ... ..	769
	(ii) Characteristics of record material, wear and noise ... ..	769
	(iii) Sound track ... ..	770
	(iv) Recording characteristics and equalization ... ..	770
	(v) Translation loss and radius compensation ... ..	770
10.	REFERENCES TO LATERAL DISC RECORDING ... ..	771

## CHAPTER 18. MICROPHONES, PRE-AMPLIFIERS, ATTENUATORS AND MIXERS

1.	MICROPHONES ... ..	775
	(i) General survey ... ..	775
	(ii) Carbon microphones ... ..	777
	(iii) Condenser microphones ... ..	778
	(iv) Crystal and ceramic microphones ... ..	778
	(v) Moving coil (dynamic) microphones ... ..	779
	(vi) Pressure ribbon microphones ... ..	779
	(vii) Velocity ribbon microphones ... ..	779
	(viii) Throat microphones ... ..	780
	(ix) Lapel microphones ... ..	780
	(x) Lip microphones ... ..	780

## CONTENTS

SECTION	PAGE
(xi) The directional characteristics of microphones ... ..	780
(xii) The equalization of microphones ... ..	781
(xiii) Microphone transformers ... ..	781
(xiv) Standards for microphones ... ..	781
<b>2. PRE-AMPLIFIERS</b> ... ..	<b>782</b>
(i) Introduction ... ..	782
(ii) Noise ... ..	782
(iii) Hum ... ..	784
(iv) Microphony ... ..	786
(v) Valves for use in pre-amplifiers ... ..	786
(vi) Microphone pre-amplifiers ... ..	788
(vii) Pickup pre-amplifiers ... ..	793
(viii) Gain-controlled pre-amplifiers ... ..	793
(ix) Standard pre-amplifiers for broadcasting ... ..	793
(x) Standard pre-amplifiers for sound equipment ... ..	793
<b>3. ATTENUATORS AND MIXERS</b> ... ..	<b>794</b>
(i) Potentiometer type attenuators (volume controls) ... ..	794
(ii) Single section attenuators—constant impedance ... ..	795
(iii) Single section attenuators—constant impedance in one direction only ... ..	795
(iv) Multiple section attenuators ... ..	796
(v) Electronic attenuators ... ..	797
(vi) Mixers and faders—general ... ..	798
(vii) Non-constant impedance mixers and faders ... ..	798
(viii) Constant impedance mixers and faders ... ..	801
<b>4. REFERENCES</b> ... ..	<b>804</b>

## CHAPTER 19. UNITS FOR THE MEASUREMENT OF GAIN AND NOISE

<b>1. BELS AND DECIBELS</b> ... ..	<b>806</b>
(i) Power relationships expressed in bels and decibels ... ..	806
(ii) Voltage and current relationships expressed in decibels ... ..	807
(iii) Absolute power and voltage expressed in decibels ... ..	807
(iv) Microphone output expressed in decibels ... ..	808
(v) Pickup output expressed in decibels ... ..	810
(vi) Amplifier gain expressed in decibels ... ..	810
(vii) Combined microphone and amplifier gain expressed in decibels ... ..	811
(viii) Loudspeaker output expressed in decibels ... ..	812
(ix) Sound system rating ... ..	812
(x) Tables and charts of decibel relationships ... ..	813
(xi) Nomogram for adding decibel-expressed quantities ... ..	821
(xii) Decibels, slide rules and mental arithmetic ... ..	822
<b>2. VOLUME INDICATORS AND VOLUME UNITS</b> ... ..	<b>823</b>
(i) Volume indicators ... ..	823
(ii) Volume units ... ..	824
<b>3. INDICATING INSTRUMENTS</b> ... ..	<b>825</b>
(i) Decibel meters ... ..	825
(ii) Power output meters ... ..	825
(iii) Volume indicators ... ..	825
(iv) Acoustical instruments ... ..	825
<b>4. NEPERS AND TRANSMISSION UNITS</b> ... ..	<b>825</b>
(i) Nepers ... ..	825
(ii) Transmission units ... ..	826



SECTION	CONTENTS	PAGE
	(iii) The overlap region ... ..	861
	(iv) Compromise arrangements ... ..	861
6.	LOUDSPEAKERS IN OPERATION ... ..	861
	(i) Loudness ... ..	861
	(ii) Power required ... ..	861
	(iii) Acoustics of rooms ... ..	864
	(iv) Loudspeaker placement ... ..	865
	(v) Stereophonic reproduction ... ..	865
	(vi) Sound reinforcing systems ... ..	866
	(vii) Open air Public Address ... ..	867
	(viii) Inter-communicating systems ... ..	867
	(ix) Background music in factories ... ..	867
7.	DISTORTION IN LOUDSPEAKERS ... ..	868
	(i) Non-linearity ... ..	868
	(ii) Frequency-modulation distortion in loudspeakers ... ..	869
	(iii) Transient distortion ... ..	869
	(iv) Sub-harmonics and sub-frequencies ... ..	871
	(v) Intermodulation distortion ... ..	871
8.	SUMMARY OF ACOUSTICAL DATA ... ..	871
	(i) Definitions in acoustics ... ..	871
	(ii) Electrical, mechanical and acoustical equivalents ... ..	872
	(iii) Velocity and wavelength of sound ... ..	872
	(iv) Musical scales ... ..	873
9.	STANDARDS FOR LOUDSPEAKERS ... ..	874
	(i) Voice coil impedance for radio receivers ... ..	874
	(ii) Loudspeaker standard ratings for sound equipment ... ..	874
10.	REFERENCES TO LOUDSPEAKERS ... ..	876

## CHAPTER 21. THE NETWORK BETWEEN THE POWER VALVE AND THE LOUDSPEAKER

1.	LOUDSPEAKER "MATCHING" ... ..	880
	(i) Loudspeaker characteristics and matching ... ..	880
	(ii) Optimum plate resistance ... ..	880
	(iii) Procedure for "matching" loudspeakers to various types of amplifiers ... ..	881
2.	MULTIPLE AND EXTENSION LOUDSPEAKERS ... ..	882
	(i) Multiple loudspeakers—general ... ..	882
	(ii) Sound systems ... ..	883
	(iii) Extension loudspeakers ... ..	883
	(iv) Operation of loudspeakers at long distances from amplifier ... ..	886
3.	LOUDSPEAKER DIVIDER NETWORKS ... ..	887
4.	REFERENCES ... ..	889

## PART 4: RADIO FREQUENCIES

### CHAPTER 22. AERIALS AND TRANSMISSION LINES

1.	INTRODUCTION ... ..	890
2.	THE TRANSMISSION LINE ... ..	890
	(i) Introduction ... ..	890
	(ii) The correct termination for a transmission line ... ..	890
	(iii) Impedance-transforming action of a transmission line ... ..	891

## CONTENTS

SECTION	PAGE
3. AERIALS AND POWER TRANSFER ... ..	892
(i) Introduction ... ..	892
(ii) Power transfer ... ..	892
4. CHARACTERISTICS OF AERIALS ... ..	893
(i) Effective area of a receiving aerial ... ..	893
(ii) The power gain of an aerial ... ..	894
(iii) The beam-width of an aerial ... ..	894
5. EFFECTS OF THE EARTH ON THE PERFORMANCE OF AN AERIAL ... ..	894
(i) Introduction ... ..	894
(ii) A perfectly-conducting earth ... ..	894
(iii) An imperfectly conducting earth ... ..	896
(iv) The attenuation of radio waves in the presence of an imper- fectly-reflecting earth ... ..	896
6. THE EFFECT OF THE IONOSPHERE ON THE RECEPTION OF RADIO SIGNALS ...	901
7. THE IMPEDANCE OF AN AERIAL ... ..	901
(i) Introduction ... ..	901
(ii) Resistive component of impedance ... ..	902
(iii) Reactive component of impedance ... ..	903
(iv) Characteristic impedance of aerial ... ..	903
(v) Examples of calculations ... ..	903
(vi) Dipoles ... ..	904
(vii) Loop aerials ... ..	905
8. DUMMY AERIALS ... ..	906
9. TYPES OF AERIAL USED FOR BROADCAST RECEPTION ... ..	907
(i) Introduction ... ..	907
(ii) Medium-frequency receiving aerials ... ..	907
(iii) Short-wave receiving aerials ... ..	908
(iv) V-H-F aerials ... ..	909
10. REFERENCES ... ..	911

## CHAPTER 23. RADIO FREQUENCY AMPLIFIERS

1. INTRODUCTION ... ..	912
(i) Aerial coupling ... ..	912
(ii) Tuning methods ... ..	913
(iii) R-F amplifiers ... ..	913
(iv) Design considerations ... ..	914
2. AERIAL STAGES ... ..	915
(i) Difficulties involved ... ..	915
(ii) Generalized coupling networks ... ..	915
(iii) Mutual inductance coupling ... ..	916
(iv) Tapped inductance ... ..	920
(v) Capacitance coupling ... ..	921
(vi) General summary ... ..	921
3. R-F AMPLIFIERS ... ..	922
(i) Reasons for using r-f stage ... ..	922
(ii) Mutual-inductance-coupled stage ... ..	922
(iii) Parallel tuned circuit ... ..	923
(iv) Choke-capacitance coupling ... ..	924
(v) Untuned and pre-tuned stages ... ..	924
(vi) Grounded grid stages ... ..	925
4. IMAGE REJECTION ... ..	925
(i) Meaning of image rejection ... ..	925
(ii) Image rejection due to aerial stage ... ..	926
(iii) Other considerations ... ..	926



## CONTENTS

SECTION	PAGE
5. EFFECTS OF VALVE INPUT ADMITTANCE ... ..	927
(i) Important general considerations ... ..	927
(ii) Input loading of receiving valves at radio frequencies ... ..	928
(A) Input conductance ... ..	929
(B) Cold input conductance ... ..	929
(C) Hot input conductance ... ..	930
(D) Change in input capacitance ... ..	932
(E) Reduction of detuning effect ... ..	933
6. VALVE AND CIRCUIT NOISE ... ..	935
(i) Thermal agitation noise ... ..	935
(ii) Shot noise ... ..	936
(iii) Induced grid noise ... ..	939
(iv) Total noise calculations ... ..	940
(v) Sample circuit calculations ... ..	941
(vi) Conclusions ... ..	942
7. INSTABILITY IN R-F AMPLIFIERS ... ..	942
(i) Causes of instability ... ..	942
(ii) Inter-electrode capacitance coupling ... ..	943
(iii) Summary ... ..	944
8. DISTORTION ... ..	944
(i) Modulation envelope distortion ... ..	945
(ii) Cross modulation distortion ... ..	945
9. BIBLIOGRAPHY ... ..	945

## CHAPTER 24. OSCILLATORS

1. INTRODUCTION ... ..	947
2. TYPES OF OSCILLATOR CIRCUITS ... ..	949
(i) Tuned plate oscillator ... ..	949
(ii) Tuned grid oscillator ... ..	950
(iii) Hartley oscillator ... ..	951
(iv) Colpitts oscillator ... ..	952
(v) Electron-coupled oscillator ... ..	953
(vi) Negative transconductance oscillators ... ..	953
3. CLASS A <sub>1</sub> , B AND C OSCILLATORS ... ..	954
4. CAUSES OF OSCILLATOR FREQUENCY VARIATION ... ..	955
(i) General ... ..	955
(ii) Changes due to supply voltage ... ..	955
(iii) Temperature and humidity changes ... ..	955
(iv) Oscillator harmonics ... ..	956
5. METHODS OF FREQUENCY STABILIZATION ... ..	957
6. UNSTABLE OSCILLATION ... ..	958
7. PARASITIC OSCILLATION ... ..	959
8. METHODS USED IN PRACTICAL DESIGN ... ..	959
9. BEAT FREQUENCY OSCILLATORS ... ..	960
10. BIBLIOGRAPHY ... ..	961

## CHAPTER 25. FREQUENCY CONVERSION AND TRACKING

1. THE OPERATION OF FREQUENCY CONVERTERS AND MIXERS ... ..	962
(i) Introduction ... ..	962
(ii) General analysis of operation common to all types ... ..	964
(iii) The oscillator section of converter tubes ... ..	968
(iv) The detailed operation of the modulator or mixer section of the converter stage ... ..	968

		CONTENTS	PAGE
SECTION	(v)	Conclusion ... ..	984
	(vi)	Appendix ... ..	985
2.	CONVERTER APPLICATIONS	... ..	987
	(i)	Broadcast frequencies ... ..	987
	(ii)	Short waves ... ..	990
	(iii)	Types of converters ... ..	996
3.	SUPERHETERODYNE TRACKING...	... ..	1002
	(i)	General ... ..	1002
	(ii)	(A) Formulae and charts for superheterodyne oscillator design ... ..	1005
		(B) Worked examples ... ..	1011
	(iii)	(A) Padded signal circuits ... ..	1013
		(B) Worked example ... ..	1015
4.	REFERENCES	... ..	1017
<b>CHAPTER 26. INTERMEDIATE FREQUENCY AMPLIFIERS</b>			
1.	CHOICE OF FREQUENCY	... ..	1020
	(i)	Reasons for selection of different frequencies ... ..	1020
	(ii)	Commonly accepted intermediate frequencies ... ..	1021
2.	NUMBER OF STAGES	... ..	1021
3.	COMMONLY USED CIRCUITS	... ..	1022
	(i)	Mutual inductance coupling ... ..	1023
	(ii)	Shunt capacitance coupling ... ..	1023
	(iii)	Composite i-f transformers ... ..	1024
4.	DESIGN METHODS	... ..	1025
	(i)	General ... ..	1025
	(ii)	Critically-coupled transformers ... ..	1026
		(A) Design equations and table ... ..	1026
		(B) Example ... ..	1028
		(C) Design extension ... ..	1029
		(D) Conclusions ... ..	1030
		(E) k measurement ... ..	1030
	(iii)	Over-coupled transformers ... ..	1031
		(A) Design equations and table ... ..	1031
		(B) Example ... ..	1033
		(C) k measurement (when k is high) ... ..	1033
	(iv)	Under-coupled transformers and single tuned circuits ... ..	1034
		(A) Single tuned circuit equations ... ..	1034
		(B) Example ... ..	1035
		(C) Under-coupled transformer equations ... ..	1035
		(D) Example ... ..	1036
	(v)	F-M i-f transformers ... ..	1037
	(vi)	I-F transformer construction ... ..	1041
	(vii)	Appendix: Calculation of coupling co-efficients ... ..	1043
5.	VARIABLE SELECTIVITY...	... ..	1048
	(i)	General considerations ... ..	1048
	(ii)	Automatic variable selectivity ... ..	1049
6.	VARIABLE BANDWIDTH CRYSTAL FILTERS	... ..	1050
	(i)	Behaviour of equivalent circuit ... ..	1050
	(ii)	Variable bandwidth crystal filters ... ..	1052
	(iii)	Design of variable bandwidth i-f crystal filter circuits ... ..	1053
		(A) Simplifying assumptions ... ..	1053
		(B) Gain ... ..	1053
		(C) Gain variation with bandwidth change ... ..	1054
		(D) Selectivity ... ..	1055

	(E) Crystal constants	...	...	...	...	1056
	(F) Position of filter in circuit	...	...	...	...	1057
	(G) Other types of crystal filters	...	...	...	...	1057
	(iv) Design example	...	...	...	...	1057
7.	DETUNING DUE TO A.V.C.	...	...	...	...	1061
	(i) Causes of detuning	...	...	...	...	1061
	(ii) Reduction of detuning effects	...	...	...	...	1062
8.	STABILITY	...	...	...	...	1065
	(i) Design data	...	...	...	...	1065
	(ii) Neutralizing circuits	...	...	...	...	1065
9.	DISTORTION	...	...	...	...	1067
	(i) Amplitude modulation i-f stages	...	...	...	...	1067
	(ii) Frequency modulation i-f stages	...	...	...	...	1068
10.	REFERENCES	...	...	...	...	1069

## CHAPTER 27. DETECTION AND AUTOMATIC VOLUME CONTROL

1.	A-M DETECTORS	...	...	...	...	1072
	(i) Diodes	...	...	...	...	1072
	(A) General	...	...	...	...	1072
	(B) Diode curves	...	...	...	...	1075
	(C) Quantitative design data	...	...	...	...	1075
	(D) Miscellaneous data	...	...	...	...	1081
	(ii) Other forms of detectors	...	...	...	...	1082
	(A) Grid detection	...	...	...	...	1082
	(B) Power grid detection	...	...	...	...	1084
	(C) Plate detection	...	...	...	...	1084
	(D) Reflex detection	...	...	...	...	1085
	(E) Regenerative detectors	...	...	...	...	1086
	(F) Superregenerative detectors	...	...	...	...	1087
2.	F-M DETECTORS	...	...	...	...	1088
	(i) Types of detectors in general use	...	...	...	...	1088
	(ii) General principles	...	...	...	...	1088
	(iii) Phase discriminators	...	...	...	...	1088
	(A) General	...	...	...	...	1088
	(B) Design data	...	...	...	...	1090
	(C) Design example	...	...	...	...	1091
	(iv) Ratio detectors	...	...	...	...	1095
	(A) General	...	...	...	...	1095
	(B) Operation	...	...	...	...	1097
	(C) Types of circuit	...	...	...	...	1098
	(D) Design considerations	...	...	...	...	1099
	(E) Practical circuits	...	...	...	...	1101
	(F) Measurement on ratio detectors	...	...	...	...	1102
3.	AUTOMATIC VOLUME CONTROL	...	...	...	...	1105
	(i) Introduction	...	...	...	...	1105
	(ii) Simple a.v.c.	...	...	...	...	1105
	(iii) Delayed a.v.c.	...	...	...	...	1106
	(iv) Methods of feed	...	...	...	...	1109
	(v) Typical circuits	...	...	...	...	1111
	(vi) A.V.C. application	...	...	...	...	1111
	(vii) Amplified a.v.c.	...	...	...	...	1112
	(viii) Audio a.v.c.	...	...	...	...	1113
	(ix) Modulation rise	...	...	...	...	1114

## CONTENTS

SECTION		PAGE
	(x) A.V.C. with battery valves ... ..	1114
	(xi) Special case with simple a.v.c. ... ..	1115
	(xii) The a.v.c. filter and its time constants ... ..	1115
	(xiii) A.V.C. characteristics ... ..	1117
	(xiv) An improved form of a.v.c. characteristic ... ..	1118
	(xv) Design methods ... ..	1120
4.	MUTING (Q.A.V.C.) ... ..	1125
	(i) General operation ... ..	1125
	(ii) Typical circuits ... ..	1125
	(iii) Circuits used with F-M receivers ... ..	1128
5.	NOISE LIMITING ... ..	1130
6.	TUNING INDICATORS ... ..	1132
	(i) Miscellaneous ... ..	1132
	(ii) Electron Ray tuning indicators ... ..	1133
	(iii) Null point indicator using Electron Ray tube ... ..	1134
	(iv) Indicators for F-M receivers ... ..	1135
7.	CRYSTAL DETECTORS ... ..	1136
	(i) Old type crystal detectors ... ..	1136
	(ii) Fixed germanium crystal detectors ... ..	1136
	(iii) Fixed silicon crystal detectors ... ..	1137
	(iv) Theory of crystal rectification ... ..	1138
	(v) Transistors ... ..	1138
8.	REFERENCES ... ..	1138

### CHAPTER 28. REFLEX AMPLIFIERS

1.	GENERAL DESCRIPTION ... ..	1140
	(i) Description ... ..	1140
	(ii) Advantages and disadvantages of reflex receivers ... ..	1140
2.	SOME CHARACTERISTICS OF REFLEX SUPERHET. RECEIVERS ... ..	1142
	(i) Playthrough (residual volume effect) ... ..	1142
	(ii) Over-loading ... ..	1142
	(iii) Automatic volume control ... ..	1142
	(iv) Reduction in percentage modulation ... ..	1143
	(v) Negative feedback ... ..	1143
	(vi) Operating conditions of reflex stage ... ..	1143
3.	DESIGN OF PLATE REFLEX SUPERHET. RECEIVERS ... ..	1143
	(i) General considerations ... ..	1143
	(ii) Full a.v.c. applied to both stages ... ..	1143
	(iii) Fractional a.v.c. applied to both stages ... ..	1143
	(iv) Full a.v.c. on converter, fractional a.v.c. on reflex stage ... ..	1144
4.	DESIGN OF SCREEN REFLEX SUPERHET. RECEIVERS ... ..	1145
	(i) Screen reflex receivers ... ..	1145
	(ii) Comparison between plate and screen reflexing ... ..	1146
5.	DESIGN OF T.R.F. REFLEX RECEIVERS ... ..	1146
6.	REFERENCES TO REFLEX AMPLIFIERS AND REFLEX RECEIVERS ... ..	1146

### CHAPTER 29. LIMITERS AND AUTOMATIC FREQUENCY CONTROL

1.	LIMITERS ... ..	1147
	(i) General ... ..	1147
	(ii) Typical circuits for F-M receivers ... ..	1149
2.	AUTOMATIC FREQUENCY CONTROL ... ..	1150
	(i) General principles ... ..	1150
	(ii) Discriminators for a.f.c. ... ..	1152
	(iii) Electronic reactances ... ..	1156
3.	REFERENCES ... ..	1160

## PART 5: RECTIFICATION, REGULATION, FILTERING AND HUM

## CHAPTER 30. RECTIFICATION

1. INTRODUCTION TO RECTIFICATION	...	...	...	...	1161
(i) Principles of rectification	...	...	...	...	1161
(ii) Rectifier valves and types of service	...	...	...	...	1164
(iii) The use of published curves	...	...	...	...	1165
(iv) Selenium and copper oxide rectifiers	.....	...	...	...	1169
2. RECTIFICATION WITH CONDENSER INPUT FILTER	...	...	...	...	1170
(i) Symbols and definitions	...	...	...	...	1170
(ii) Rectification with condenser input filter	...	...	...	...	1170
(iii) To determine peak and average diode currents	...	...	...	...	1174
(iv) To determine ripple percentage	...	...	...	...	1177
(v) To determine the transformer secondary r.m.s. current	...	...	...	...	1177
(vi) Procedure when complete published data are not available	...	...	...	...	1177
(vii) Approximations when the capacitance is large	...	...	...	...	1180
(viii) Peak hot-switching transient plate current	...	...	...	...	1180
(ix) The effect of ripple	...	...	...	...	1181
3. RECTIFICATION WITH CHOKE INPUT FILTER	...	...	...	...	1182
(i) Rectification with choke input filter	...	...	...	...	1182
(ii) Initial transient current	...	...	...	...	1185
4. TRANSFORMER HEATING	...	...	...	...	1185
5. VOLTAGE MULTIPLYING RECTIFIERS	...	...	...	...	1186
(i) General	...	...	...	...	1186
(ii) Voltage doublers	...	...	...	...	1186
(iii) Voltage triplers	...	...	...	...	1187
(iv) Voltage quadruplers	...	...	...	...	1187
6. SHUNT DIODE BIAS SUPPLIES	...	...	...	...	1188

## CHAPTER 31. FILTERING AND HUM

1. INDUCTANCE-CAPACITANCE FILTERS	...	...	...	...	1192
2. RESISTANCE-CAPACITANCE FILTERS	...	...	...	...	1194
3. PARALLEL-T FILTER NETWORKS	...	...	...	...	1194
4. HUM—GENERAL	...	...	...	...	1196
(i) Hum due to conditions within the valves	...	...	...	...	1196
(ii) Hum due to circuit design and layout	...	...	...	...	1198
(iii) Hum levels in receivers and amplifiers	...	...	...	...	1199
5. HUM NEUTRALIZING	...	...	...	...	1200
6. REFERENCES	...	...	...	...	1201

## CHAPTER 32. VIBRATOR POWER SUPPLIES

1. VIBRATORS—GENERAL PRINCIPLES	...	...	...	...	1202
(i) Operation	...	...	...	...	1202
(ii) Vibrator types	...	...	...	...	1202
(iii) Choice of vibrator	...	...	...	...	1203
(iv) Coil energizing	...	...	...	...	1204
(v) Waveform and time efficiency	...	...	...	...	1205
(vi) Standards for vibrators for auto-radio	...	...	...	...	1205

## CONTENTS

SECTION	PAGE
2. VIBRATOR TRANSFORMER DESIGN ... ..	1205
(i) General considerations ... ..	1205
(ii) Transformer calculations ... ..	1206
(iii) Standards for vibrator power transformers ... ..	1207
3. TIMING CAPACITANCE ... ..	1207
(i) The use of the timing capacitance ... ..	1207
(ii) Calculation of timing capacitance value ... ..	1207
(iii) Percentage closure ... ..	1208
(iv) Effect of flux density on timing capacitance value ... ..	1208
4. ELIMINATION OF VIBRATOR INTERFERENCE ... ..	1210
5. 12, 24 AND 32 VOLT VIBRATOR SUPPLIES ... ..	1211

### CHAPTER 33. CURRENT AND VOLTAGE REGULATORS

1. CURRENT REGULATORS ... ..	1213
(i) Barretters ... ..	1213
(ii) Negative temperature coefficient resistors (Thermistors) ... ..	1214
2. VOLTAGE REGULATORS ... ..	1214
(i) Gaseous tube voltage regulators ... ..	1214
(ii) Valve voltage regulators ... ..	1215
3. REFERENCES ... ..	1222

## PART 6: COMPLETE RECEIVERS

### CHAPTER 34. TYPES OF A-M RECEIVERS

1. INTRODUCTION AND SIMPLE RECEIVERS ... ..	1223
(i) Types of receivers ... ..	1223
(ii) Crystal sets ... ..	1223
(iii) Regenerative receivers ... ..	1223
(iv) Superheterodyne receivers ... ..	1224
(v) Tuned radio-frequency receivers ... ..	1224
2. THE SUPERHETERODYNE ... ..	1225
3. THE SYNCHRODYNE ... ..	1226
4. REFERENCES ... ..	1227

### CHAPTER 35. DESIGN OF SUPERHETERODYNE A-M RECEIVERS

1. INTRODUCTION ... ..	1228
2. SPECIFICATIONS AND REQUIREMENTS ... ..	1229
3. GENERAL DESIGN ... ..	1229
(i) A.V.C. and noise ... ..	1229
(ii) Audio-frequency response ... ..	1234
(iii) Hum ... ..	1239
(iv) Microphony ... ..	1241
(v) Instability ... ..	1243
(vi) The local oscillator ... ..	1244
(vii) Cabinet design ... ..	1248
(viii) Ratings ... ..	1249
(ix) Field testing ... ..	1250
4. FREQUENCY RANGES ... ..	1250
(i) Medium frequency receivers ... ..	1250
(ii) Dual wave receivers ... ..	1251
(iii) Multiband receivers ... ..	1252
(iv) Bandsread receivers ... ..	1253

## CONTENTS

SECTION	PAGE
5. A.C. OPERATED RECEIVERS ... ..	1256
(i) Four valve receivers ... ..	1256
(ii) Five valve receivers ... ..	1259
(iii) Larger receivers ... ..	1260
(iv) Communication receivers ... ..	1260
6. A.C./D.C. RECEIVERS ... ..	1264
(i) Series-resistor operation... ..	1264
(ii) Barretter operation ... ..	1266
(iii) Dial lamps ... ..	1266
(iv) Miscellaneous features ... ..	1267
7. BATTERY OPERATED RECEIVERS ... ..	1268
(i) General features ... ..	1268
(ii) Vibrator-operated receivers ... ..	1270
(iii) Characteristics of dry batteries ... ..	1272
8. CAR RADIO ... ..	1275
(i) Interference suppression ... ..	1275
(ii) Circuit considerations ... ..	1276
(iii) Valve operating conditions ... ..	1277
9. MISCELLANEOUS FEATURES ... ..	1278
(i) Spurious responses ... ..	1278
(ii) Reduction of interference ... ..	1279
(iii) Contact potential biasing ... ..	1280
(iv) Fuses ... ..	1281
(v) Tropic proofing ... ..	1282
(vi) Parasitic oscillations ... ..	1283
(vii) Printed circuits ... ..	1283
(viii) Other miscellaneous features ... ..	1285
10. REFERENCES ... ..	1285

### CHAPTER 36. DESIGN OF F-M RECEIVERS

1. F-M RECEIVERS ... ..	1287
(i) Comparison with A-M ... ..	1287
(ii) Aerial and r-f design ... ..	1287
(iii) Local oscillator design ... ..	1289
(iv) I-F amplifier ... ..	1290
(v) F-M detection and A-M rejection ... ..	1292
2. F-M/A-M RECEIVERS ... ..	1294
(i) R-F section ... ..	1294
(ii) I-F amplifier ... ..	1294
(iii) General considerations ... ..	1295
3. REFERENCES ... ..	1296

### CHAPTER 37. RECEIVER AND AMPLIFIER TESTS AND MEASUREMENTS

1. A-M RECEIVERS ... ..	1297
(i) Introduction ... ..	1297
(ii) Definitions ... ..	1297
(iii) Equipment required ... ..	1298
(iv) Measurements and operating conditions ... ..	1300
(v) Measurements ... ..	1301
(vi) Tests ... ..	1302
2. F-M RECEIVERS ... ..	1314
(i) Definitions ... ..	1314
(ii) Testing apparatus ... ..	1315

# CONTENTS

SECTION	PAGE
(iii) Test procedures and operating conditions ... ..	1315
(iv) Receiver adjustments ... ..	1316
(v) Performance tests ... ..	1317
<b>3. AUDIO FREQUENCY AMPLIFIERS</b> ... ..	<b>1321</b>
(i) Equipment and measurements ... ..	1321
(ii) Tests ... ..	1321
<b>4. MEASUREMENTS ON COILS</b> ... ..	<b>1325</b>
(i) Measurement of coefficient of coupling ... ..	1325
(ii) Measurement of primary resonant frequencies of aerial and r-f coils ... ..	1325
(iii) Measurement of distributed capacitance across coils ... ..	1325
<b>5. REFERENCES</b> ... ..	<b>1327</b>

## PART 7: SUNDRY DATA

### CHAPTER 38. TABLES, CHARTS AND SUNDRY DATA

<b>1. UNITS</b> ... ..	<b>1329</b>
(i) General physical units ... ..	1329
(ii) Electrical and magnetic units ... ..	1331
(iii) Photometric units ... ..	1334
(iv) Temperature ... ..	1334
<b>2. COLOUR CODES</b> ... ..	<b>1335</b>
(i) Colour code for fixed composition resistors ... ..	1335
(ii) Colour code for fixed wire wound resistors ... ..	1336
(iii) Table of R.M.A. colour code markings for resistors ... ..	1337
(iv) Colour code for moulded mica capacitors ... ..	1340
(v) Colour code for ceramic dielectric capacitors ... ..	1341
(vi) Colour code for i-f transformers ... ..	1342
(vii) Colour code for a-f transformers and output transformers ... ..	1342
(viii) Colour code for power transformers ... ..	1342
(ix) Colour code for loudspeakers ... ..	1343
(x) Colour code for chassis wiring ... ..	1343
(xi) Colour code for battery cables ... ..	1344
(xii) Colour code for metallized paper capacitors ... ..	1344
<b>3. STANDARD RESISTORS AND CAPACITORS</b> ... ..	<b>1344</b>
(i) Standard fixed composition resistors ... ..	1344
(ii) Standard fixed wire wound resistors ... ..	1346
(iii) Fixed paper dielectric capacitors in tubular non-metallic cases ... ..	1347
(iv) Metal encased fixed paper dielectric capacitors for d.c. application ... ..	1349
(v) Standard fixed mica dielectric capacitors ... ..	1351
(vi) Standard ceramic dielectric capacitors ... ..	1352
(vii) Standard variable capacitors ... ..	1354
(viii) Standard variable composition resistors ... ..	1356
(ix) Standard metallized paper dielectric capacitors ... ..	1357
(x) Standard electrolytic capacitors ... ..	1357
(xi) References to standard resistors and capacitors ... ..	1358
<b>4. STANDARD FREQUENCIES</b> ... ..	<b>1361</b>
(i) Standard frequency ranges ... ..	1361
(ii) Frequency bands for broadcasting ... ..	1361
(iii) Standard intermediate frequencies ... ..	1361
<b>5. WAVELENGTHS AND FREQUENCIES</b> ... ..	<b>1362</b>
(i) Wavelength-frequency conversion tables ... ..	1362
(ii) Wavelengths of electromagnetic radiations ... ..	1363
<b>6. STANDARD SYMBOLS AND ABBREVIATIONS</b> ... ..	<b>1363</b>
(i) Introduction ... ..	1363
(ii) Multipliers ... ..	1363



## CONTENTS

SECTION	PAGE
(iii) Some units and multipliers ... ..	1363
(iv) Magnitude letter symbols ... ..	1364
(v) Subscripts for magnitude letter symbols ... ..	1364
(vi) Magnitude letter symbols with subscripts ... ..	1365
(vii) Mathematical signs ... ..	1366
(viii) Abbreviations ... ..	1366
(ix) Abbreviations of titles of periodicals ... ..	1367
(x) References to periodicals ... ..	1369
(xi) References to standard symbols and abbreviations ... ..	1369
7. STANDARD GRAPHICAL SYMBOLS ... ..	1370
8. PROPERTIES OF MATERIALS AND CHEMICAL AND PHYSICAL CONSTANTS ... ..	1372
(i) Properties of insulating materials ... ..	1372
(ii) Properties of conducting materials ... ..	1374
(iii) Composition of some common plastics ... ..	1375
(iv) Weights of common materials... ..	1375
(v) Resistance of a conductor at any temperature ... ..	1376
(vi) References to properties of materials... ..	1376
(vii) Chemical and physical constants ... ..	1376
9. REACTANCE, IMPEDANCE AND RESONANCE ... ..	1377
(i) Inductive reactances ... ..	1377
(ii) Capacitive reactances ... ..	1378
(iii) Impedance of reactance and resistance in parallel ... ..	1380
(iv) Impedance of reactance and resistance in series ... ..	1382
(v) Resonance... ..	1386
(vi) Approximations in the calculation of impedance for reactance and resistance in series and parallel ... ..	1386
(vii) Reactance chart ... ..	1387
10. SCREW THREADS, TWIST DRILLS AND SHEET GAUGES ... ..	1388
(i) Standard American screws used in radio manufacture ... ..	1388
(ii) B.A. screw threads ... ..	1389
(iii) Whitworth screw threads ... ..	1389
(iv) Unified screw threads ... ..	1390
(v) Drill sizes for self-tapping screws ... ..	1391
(vi) Wood screws ... ..	1391
(vii) Twist drill sizes ... ..	1392
(viii) Sheet steel gauges ... ..	1393
11. TEMPERATURE RISE AND RATINGS ... ..	1394
12. FUSES ... ..	1395
13. CHARACTERISTICS OF LIGHT ; PANEL LAMPS ... ..	1396
(i) Visibility curves of the human eye and relative spectral energy curves of sunlight and tungsten lamp ... ..	1396
(ii) Velocity of light ... ..	1396
(iii) American panel lamp characteristics ... ..	1397
14. GREEK ALPHABET ... ..	1397
15. DEFINITIONS ... ..	1398
16. DECIMAL EQUIVALENTS OF FRACTIONS ... ..	1404
17. MULTIPLES AND SUB-MULTIPLES ... ..	1405
18. (i) Numerical values... ..	1406
(ii) Factorials ... ..	1407
19. WIRE TABLES ... ..	1408
20. LOGARITHM TABLES ... ..	1418
21. TRIGONOMETRICAL TABLES ... ..	1420
Hyperbolic sines, cosines and tangents ... ..	1421
22. LOG SCALES AND LOG SCALE INTERPOLATOR ... ..	1422

621359  
L278  
4. ed.  
#

# RADIOTRON DESIGNER'S HANDBOOK

Edited By  
**F. LANGFORD-SMITH**  
*B.Sc., B.E. (1st class honours)*  
*Senior Member I.R.E. (U.S.A.)*  
*A.M.I.E. (Aust.)*

FOURTH EDITION

Published by the Wireless Press  
for  
AMALGAMATED WIRELESS VALVE COMPANY PTY. LTD.  
47 YORK STREET, SYDNEY, AUSTRALIA  
1953

Reproduced and Distributed  
by  
Electron Tube Division  
RADIO CORPORATION OF AMERICA  
HARRISON, N. J.



Instituto Nacional  
de Tecnología Industrial  
Extensión y Desarrollo  
División Biblioteca

INTI  
132351

# CHAPTER HEADINGS

## PART 1: THE RADIO VALVE

CHAPTER	PAGE
1 INTRODUCTION TO THE RADIO VALVE ... ..	1
2 VALVE CHARACTERISTICS ... ..	13
3 THE TESTING OF OXIDE-COATED CATHODE HIGH-VACUUM RECEIVING VALVES	68

## PART 2: GENERAL THEORY AND COMPONENTS

4 THEORY OF NETWORKS ... ..	128
5 TRANSFORMERS AND IRON-CORED INDUCTORS ... ..	199
6 MATHEMATICS ... ..	254
7 NEGATIVE FEEDBACK ... ..	306
8 WAVE MOTION AND THE THEORY OF MODULATION ... ..	403
9 TUNED CIRCUITS ... ..	407
10 CALCULATION OF INDUCTANCE ... ..	429
11 DESIGN OF RADIO FREQUENCY INDUCTORS ... ..	450

## PART 3: AUDIO FREQUENCIES

12 AUDIO FREQUENCY VOLTAGE AMPLIFIERS ... ..	481
13 AUDIO FREQUENCY POWER AMPLIFIERS ... ..	544
14 FIDELITY AND DISTORTION ... ..	603
15 TONE COMPENSATION AND TONE CONTROL ... ..	635
16 VOLUME EXPANSION, COMPRESSION AND LIMITING ... ..	679
17 REPRODUCTION FROM RECORDS... ..	701
18 MICROPHONES, PRE-AMPLIFIERS, ATTENUATORS AND MIXERS... ..	775
19 UNITS FOR THE MEASUREMENT OF GAIN AND NOISE ... ..	806
20 LOUDSPEAKERS ... ..	831
21 THE NETWORK BETWEEN THE POWER OUTPUT STAGE AND THE LOUDSPEAKER	880

## PART 4: RADIO FREQUENCIES

22 AERIALS AND TRANSMISSION LINES ... ..	890
23 RADIO FREQUENCY AMPLIFIERS ... ..	912
24 OSCILLATORS ... ..	947
25 FREQUENCY CONVERSION AND TRACKING ... ..	962
26 INTERMEDIATE FREQUENCY AMPLIFIERS ... ..	1020
27 DETECTION AND AUTOMATIC VOLUME CONTROL ... ..	1072
28 REFLEX AMPLIFIERS ... ..	1140
29 LIMITERS AND AUTOMATIC FREQUENCY CONTROL ... ..	1147

## PART 5: RECTIFICATION, REGULATION, FILTERING AND HUM

30 RECTIFICATION ... ..	1161
31 FILTERING AND HUM ... ..	1192
32 VIBRATOR POWER SUPPLIES ... ..	1202
33 CURRENT AND VOLTAGE REGULATORS ... ..	1213

## PART 6: COMPLETE RECEIVERS

34 TYPES OF A-M RECEIVERS ... ..	1223
35 DESIGN OF SUPERHETERODYNE A-M RECEIVERS ... ..	1228
36 DESIGN OF F-M RECEIVERS ... ..	1287
37 RECEIVER AND AMPLIFIER TESTS AND MEASUREMENTS ... ..	1297

## PART 7: SUNDRY DATA

38 TABLES, CHARTS AND SUNDRY DATA ... ..	1328
--	------

See next page for detailed List of Contents.

SUPPLEMENT ... ..	1475
-------------------	------

# CONTENTS

## PART 1: THE RADIO VALVE

### CHAPTER 1. INTRODUCTION TO THE RADIO VALVE

SECTION	PAGE
1. ELECTRICITY AND EMISSION ... ..	1
2. THE COMPONENT PARTS OF RADIO VALVES ... ..	4
(i) Filaments, cathodes and heaters ... ..	4
(ii) Grids ... ..	5
(iii) Plates ... ..	5
(iv) Bulbs ... ..	5
(v) Voltages with valve operation ... ..	5
3. TYPES OF RADIO VALVES ... ..	6
(i) Diodes ... ..	6
(ii) Triodes ... ..	7
(iii) Tetrodes ... ..	7
(iv) Pentodes ... ..	7
(v) Pentode power amplifiers ... ..	8
(vi) Combined valves ... ..	8
(vii) Pentagrid converters ... ..	8
4. MAXIMUM RATINGS AND TOLERANCES ... ..	9
(i) Maximum ratings and their interpretation ... ..	9
(ii) Tolerances ... ..	9
5. FILAMENT AND HEATER VOLTAGE/CURRENT CHARACTERISTICS ... ..	10
6. VALVE NUMBERING SYSTEMS ... ..	10
7. REFERENCES ... ..	12

### CHAPTER 2. VALVE CHARACTERISTICS

1. VALVE COEFFICIENTS ... ..	13
2. CHARACTERISTIC CURVES ... ..	15
(i) Plate characteristics ... ..	15
(ii) Mutual characteristics ... ..	17
(iii) Grid current characteristics ... ..	18
(iv) Suppressor characteristics ... ..	21
(v) Constant current curves ... ..	22
(vi) "G" curves ... ..	23
(vii) Drift of characteristics during life ... ..	23
(viii) Effect of heater-voltage variation ... ..	24
3. RESISTANCE-LOADED AMPLIFIERS ... ..	24
(i) Triodes ... ..	24
(ii) Pentodes ... ..	26
4. TRANSFORMER-COUPLED AMPLIFIERS ... ..	27
(i) With resistive load ... ..	27
(ii) Effect of primary resistance ... ..	28
(iii) With i-f voltage amplifiers ... ..	28
(iv) R-F amplifiers with sliding screen ... ..	28

## CONTENTS

SECTION	PAGE
(v) Cathode loadlines ... ..	29
(vi) With reactive loads ... ..	30
5. TRIODE OPERATION OF PENTODES ... ..	34
(i) Triode operation of pentodes ... ..	34
(ii) Examples of transconductance calculation ... ..	34
(iii) Triode amplification factor ... ..	35
(iv) Plate resistance ... ..	36
(v) Connection of suppressor grid ... ..	36
6. CONVERSION FACTORS, AND THE CALCULATION OF CHARACTERISTICS OTHER THAN THOSE PUBLISHED ... ..	36
(i) The basis of valve conversion factors ... ..	36
(ii) The use of valve conversion factors ... ..	37
(iii) The calculation of valve characteristics other than those published ... ..	40
(iv) The effect of changes in operating conditions ... ..	42
7. VALVE EQUIVALENT CIRCUITS AND VECTORS ... ..	45
(i) Constant voltage equivalent circuit ... ..	45
(ii) Constant current equivalent circuit ... ..	46
(iii) Valve vectors ... ..	47
8. VALVE ADMITTANCES ... ..	49
(i) Grid input impedance and admittance ... ..	49
(ii) Admittance coefficients ... ..	50
(iii) The components of grid admittance—input resistance—input capacitance—grid input admittance ... ..	51
(iv) Typical values of short-circuit input conductance ... ..	55
(v) Change of short-circuit-input capacitance with transconductance ... ..	55
(vi) Grid-cathode capacitance ... ..	56
(vii) Input capacitances of pentodes (published values) ... ..	56
(viii) Grid-plate capacitance ... ..	57
9. MATHEMATICAL RELATIONSHIPS ... ..	57
(i) General ... ..	57
(ii) Resistance load ... ..	58
(iii) Power and efficiency ... ..	59
(iv) Series expansion; resistance load ... ..	61
(v) Series expansion; general case ... ..	63
(vi) The equivalent plate circuit theorem ... ..	63
(vii) Dynamic load line—general case ... ..	64
(viii) Valve networks—general case ... ..	64
(ix) Valve coefficients as partial differentials ... ..	64
(x) Valve characteristics at low plate currents ... ..	65
10. REFERENCES ... ..	66
<b>CHAPTER 3. THE TESTING OF OXIDE-COATED CATHODE HIGH-VACUUM RECEIVING VALVES</b>	
1. BASIS OF TESTING PRACTICE ... ..	68
(i) Fundamental physical properties ... ..	69
(ii) Basic functional characteristics ... ..	70
(iii) Fundamental characteristic tests ... ..	73
(iv) Valve ratings and their limiting effect on operation ... ..	75
(A) Limiting ratings ... ..	75
(B) Characteristics usually rated ... ..	75
(C) Rating systems ... ..	77
(D) Interpretation of maximum ratings ... ..	77
(E) Operating conditions ... ..	80
(v) Recommended practice and operation ... ..	80
(a) Mounting ... ..	80
(b) Ventilation ... ..	81

	(c) Heater-cathode insulation ... ..	81
	(d) Control grid circuit resistance ... ..	82
	(e) Operation at low screen voltages ... ..	84
	(f) Microphony ... ..	84
	(g) Hum ... ..	84
	(h) Stand-by operation ... ..	84
2.	CONTROL OF CHARACTERISTICS DURING MANUFACTURE ... ..	85
	(i) Importance of control over characteristics ... ..	85
	(ii) Basic manufacturing test specification ... ..	85
	(iii) Systematic testing ... ..	86
	(iv) Tolerances on characteristics ... ..	88
3.	METHODS OF TESTING CHARACTERISTICS ... ..	89
	(i) General conventions ... ..	90
	(ii) General characteristics ... ..	91
	(a) Physical dimensions ... ..	91
	(b) Shorts and continuity ... ..	91
	(c) Heater (or filament) current ... ..	93
	(d) Heater to cathode leakage ... ..	94
	(e) Inter-electrode insulation ... ..	94
	(f) Emission ... ..	94
	(g) Direct inter-electrode capacitances ... ..	95
	(iii) Specific diode characteristics ... ..	99
	(a) Rectification test ... ..	99
	(b) Sputter and arcing ... ..	100
	(c) Back emission ... ..	100
	(d) Zero signal or standing diode current ... ..	101
	(iv) Specific triode, pentode and beam tetrode characteristics... ..	101
	(A) Reverse grid current ... ..	101
	(B) Grid current commencement voltage ... ..	102
	(C) Positive grid current ... ..	102
	(D) Positive voltage electrode currents ... ..	103
	(E) Transconductance or mutual conductance... ..	103
	(F) Amplification factor ... ..	104
	(G) Plate resistance ... ..	104
	(H) A.C. amplification ... ..	105
	(I) Power output ... ..	105
	(J) Distortion ... ..	106
	(K) Microphony ... ..	107
	(L) Audio frequency noise ... ..	107
	(M) Radio frequency noise ... ..	107
	(N) Blocking ... ..	107
	(O) Stage gain testing ... ..	108
	(P) Electrode dissipation ... ..	108
	(v) Specific converter characteristics ... ..	108
	(A) Methods of operation including oscillator excitation ... ..	108
	(1) Oscillator self-excited ... ..	108
	(2) Oscillator driven ... ..	109
	(3) Static operation ... ..	109
	(B) Specific characteristics ... ..	109
	(a) Reverse signal grid current ... ..	109
	(b) Signal-grid current commencement ... ..	109
	(c) Mixer positive voltage electrode currents ... ..	109
	(d) Mixer conversion transconductance ... ..	109
	(e) Mixer plate resistance ... ..	111
	(f) Mixer transconductance ... ..	111
	(g) Oscillator grid current ... ..	111

	PAGE
	113
	113
	113
	113
	113
	113
	113
(vi) Tests for special characteristics ... ..	113
(A) Short-circuit input admittance ... ..	113
(B) Short-circuit feedback admittance ... ..	117
(C) Short-circuit output admittance ... ..	117
(D) Short-circuit forward admittance ... ..	117
(E) Perveance ... ..	117
(vii) Characteristics by pulse methods—point by point ... ..	118
(viii) Characteristics by curve tracer methods ... ..	119
4. ACCEPTANCE TESTING ... ..	120
(i) Relevant characteristics ... ..	120
(ii) Valve specifications ... ..	120
(iii) Testing procedure ... ..	120
5. SERVICE TESTING AND SERVICE TESTER PRACTICE ... ..	121
(i) Purpose and scope of service testing and discussion of as- sociated problems ... ..	121
(ii) Fundamental characteristics which should be tested ... ..	122
(iii) Types of commercial testers ... ..	122
(iv) Methods of testing characteristics in commercial service testers	123
(a) Shorts testing ... ..	123
(b) Continuity testing ... ..	123
(c) Heater to cathode leakage ... ..	123
(d) Emission testing ... ..	123
(e) Mutual conductance testing ... ..	123
(f) Plate conductance testing ... ..	124
(g) Reverse grid current testing ... ..	124
(h) Power output testing ... ..	124
(i) Conversion conductance testing ... ..	124
(j) Oscillator mutual conductance testing ... ..	124
(k) Noise testing ... ..	124
(l) A.C. amplification testing ... ..	124
(v) A.C. versus d.c. electrode voltages in testers ... ..	124
(vi) Pre-heating ... ..	125
(vii) Testing procedure ... ..	125
6. REFERENCES ... ..	125

## PART 2: GENERAL THEORY AND COMPONENTS

## CHAPTER 4. THEORY OF NETWORKS

1. CURRENT AND VOLTAGE ... ..	128
(i) Direct current ... ..	128
(ii) Alternating current ... ..	129
(iii) Indications of polarity and current flow ... ..	130
2. RESISTANCE ... ..	130
(i) Ohm's Law for d.c. ... ..	130
(ii) Ohm's Law for a.c. ... ..	131
(iii) Resistances in series ... ..	131
(iv) Resistances in parallel ... ..	132
(v) Conductance in resistive circuits ... ..	133

# CONTENTS

SECTION	PAGE
3. POWER ... ..	133
(i) Power in d.c. circuits ... ..	133
(ii) Power in resistive a.c. circuits... ..	133
4. CAPACITANCE ... ..	134
(i) Introduction to capacitance ... ..	134
(ii) Condensers in parallel and series ... ..	135
(iii) Calculation of capacitance ... ..	135
(iv) Condensers in d.c. circuits ... ..	136
(v) Condensers in a.c. circuits ... ..	137
5. INDUCTANCE ... ..	140
(i) Introduction to inductance ... ..	140
(ii) Inductances in d.c. circuits ... ..	141
(iii) Inductances in series and parallel ... ..	141
(iv) Mutual inductance ... ..	142
(v) Inductances in a.c. circuits ... ..	142
(vi) Power in inductive circuits ... ..	143
6. IMPEDANCE AND ADMITTANCE ... ..	144
(i) Impedance, a complex quantity ... ..	144
(ii) Series circuits with L, C and R ... ..	144
(iii) Parallel combinations of L, C and R ... ..	147
(iv) Series-parallel combinations of L, C and R... ..	149
(v) Conductance, susceptance and admittance ... ..	153
(vi) Conversion from series to parallel impedance ... ..	157
7. NETWORKS ... ..	158
(i) Introduction to networks ... ..	158
(ii) Kirchoff's Laws ... ..	160
(iii) Potential dividers ... ..	161
(iv) Thevenin's Theorem ... ..	164
(v) Norton's Theorem ... ..	165
(vi) Maximum Power Transfer Theorem ... ..	165
(vii) Reciprocity Theorem ... ..	165
(viii) Superposition Theorem... ..	165
(ix) Compensation Theorem... ..	166
(x) Four-terminal networks... ..	166
(xi) Multi-mesh networks ... ..	167
(xii) Non-linear components in networks ... ..	170
(xiii) Phase shift networks ... ..	170
(xiv) Transients in networks ... ..	171
(xv) References to networks ... ..	171
8. FILTERS ... ..	172
(i) Introduction to filters ... ..	172
(ii) Resistance-capacitance filters, high-pass and low-pass ... ..	172
(iii) Special types of resistance-capacitance filters ... ..	176
(iv) Iterative impedances of four terminal networks ... ..	176
(v) Image impedances and image transfer constant of four terminal networks ... ..	177
(vi) Symmetrical networks ... ..	179
(vii) "Constant k" filters ... ..	179
(viii) M-derived filters ... ..	182
(ix) Practical filters ... ..	184
(x) Frequency dividing networks ... ..	184
(xi) References to filters ... ..	185



## CONTENTS

SECTION	PAGE
9. PRACTICAL RESISTORS, CONDENSERS AND INDUCTORS ... ..	186
(i) Practical resistors ... ..	186
(ii) Practical condensers ... ..	191
(iii) Combination units ... ..	197
(iv) Practical inductors ... ..	197
(v) References to practical resistors and condensers ... ..	198
<b>CHAPTER 5. TRANSFORMERS AND IRON-CORED INDUCTORS</b>	
1. IDEAL TRANSFORMERS ... ..	199
(i) Definitions ... ..	199
(ii) Impedance calculations—single load ... ..	200
(iii) Impedance calculations—multiple loads ... ..	201
2. PRACTICAL TRANSFORMERS ... ..	204
(i) General considerations ... ..	204
(ii) Effects of losses ... ..	205
3. AUDIO-FREQUENCY TRANSFORMERS ... ..	206
(i) General considerations ... ..	206
(ii) Core materials ... ..	207
(iii) Frequency response and distortion	
(a) Interstage transformers ... ..	209
(b) Low level transformers ... ..	210
(c) Output transformers ... ..	211
(iv) Designing for low leakage inductance ... ..	217
(v) Winding capacitance ... ..	219
(vi) Tests on output transformers ... ..	227
(vii) Specifications for a-f transformers ... ..	228
4. MAGNETIC CIRCUIT THEORY ... ..	229
(i) Fundamental magnetic relationships ... ..	229
(ii) The magnetic circuit ... ..	231
(iii) Magnetic units and conversion factors ... ..	232
5. POWER TRANSFORMERS... ..	233
(i) General ... ..	233
(ii) Core material and size ... ..	234
(iii) Primary and secondary turns ... ..	235
(iv) Currents in windings ... ..	236
(v) Temperature rise ... ..	236
(vi) Typical design ... ..	237
(vii) Specifications for power transformers ... ..	241
6. IRON-CORED INDUCTORS ... ..	242
(i) General ... ..	242
(ii) Calculations—general ... ..	242
(iii) Effective permeability ... ..	243
(iv) Design with no d.c. flux ... ..	243
(v) Design of high Q inductors ... ..	245
(vi) Design with d.c. flux ... ..	247
(vii) Design by Hanna's method ... ..	248
(viii) Design of inductors for choke-input filters ... ..	249
(ix) Measurements ... ..	250
(x) Iron-cored inductors in resonant circuits ... ..	251
7. REFERENCES ... ..	252

# CONTENTS

SECTION

PAGE

## CHAPTER 6. MATHEMATICS

1.	ARITHMETIC AND THE SLIDE RULE ... ..	255
	(i) Figures ... ..	255
	(ii) Powers and roots ... ..	255
	(iii) Logarithms ... ..	255
	(iv) The slide rule ... ..	257
	(v) Short cuts in arithmetic ... ..	258
2.	ALGEBRA ... ..	259
	(i) Addition ... ..	260
	(ii) Subtraction ... ..	260
	(iii) Multiplication ... ..	260
	(iv) Division ... ..	260
	(v) Powers ... ..	260
	(vi) Roots ... ..	261
	(vii) Brackets and simple manipulations ... ..	261
	(viii) Factoring ... ..	262
	(ix) Proportion ... ..	262
	(x) Variation ... ..	262
	(xi) Inequalities ... ..	262
	(xii) Functions ... ..	263
	(xiii) Equations ... ..	263
	(xiv) Formulae and laws ... ..	265
	(xv) Continuity and limits ... ..	265
	(xvi) Progressions, sequences and series ... ..	266
	(xvii) Logarithmic and exponential functions ... ..	267
	(xviii) Infinite series ... ..	268
	(xix) Hyperbolic functions ... ..	269
	(xx) General approximations ... ..	271
3.	GEOMETRY AND TRIGONOMETRY ... ..	272
	(i) Plane figures ... ..	272
	(ii) Surfaces and volumes of solids ... ..	275
	(iii) Trigonometrical relationships ... ..	275
4.	PERIODIC PHENOMENA ... ..	278
5.	GRAPHICAL REPRESENTATION AND j NOTATION ... ..	279
	(i) Graphs ... ..	279
	(ii) Finding the equation to a curve ... ..	281
	(iii) Three variables ... ..	281
	(iv) Vectors and j notation ... ..	282
6.	COMPLEX ALGEBRA AND DE MOIVRE'S THEOREM ... ..	285
	(i) Complex algebra with regular coordinates ... ..	285
	(ii) Complex algebra with polar coordinates ... ..	286
	(iii) De Moivre's Theorem ... ..	287
7.	DIFFERENTIAL AND INTEGRAL CALCULUS ... ..	289
	(i) Slope and rate of change ... ..	289
	(ii) Differentiation ... ..	291
	(iii) Integration ... ..	294
	(iv) Taylor's Series ... ..	298
	(v) Maclaurin's Series ... ..	299
8.	FOURIER SERIES AND HARMONICS ... ..	299
	(i) Periodic waves and the Fourier Series ... ..	299
	(ii) Other applications of the Fourier Series ... ..	302
	(iii) Graphical Harmonic Analysis ... ..	302
9.	REFERENCES ... ..	304

## CHAPTER 7. NEGATIVE FEEDBACK

1. FUNDAMENTAL TYPES OF FEEDBACK ... ..	306
(i) Feedback positive and negative ... ..	306
(ii) Negative voltage feedback at the mid-frequency ... ..	307
(iii) Negative current feedback at the mid-frequency ... ..	312
(iv) Bridge negative feedback at the mid-frequency ... ..	313
(v) Combined positive and negative at the mid-frequency ... ..	314
(vi) Comparison between different fundamental types at the mid-frequency ... ..	315
2. PRACTICAL FEEDBACK CIRCUITS ... ..	316
(i) The cathode follower ... ..	316
(ii) The cathode degenerative amplifier and phase splitter ... ..	327
(iii) Voltage feedback from secondary of output transformer ... ..	330
(iv) Voltage feedback from plate—transformer input ... ..	332
(v) Voltage feedback from plate—r.c.c. input ... ..	332
(vi) Voltage feedback over two stages ... ..	334
(vii) Voltage feedback over three stages ... ..	344
(viii) Cathode coupled phase inverters and amplifiers ... ..	347
(ix) Hum ... ..	348
(x) Some special features of feedback amplifiers ... ..	352
(xi) Combined positive and negative feedback ... ..	352
(xii) Choke-coupled phase inverter ... ..	355
3. STABILITY, PHASE SHIFT AND FREQUENCY RESPONSE ... ..	356
(i) Stability and instability... ..	356
(ii) Conditions for stability... ..	356
(iii) Relationship between phase shift and attenuation ... ..	359
(iv) Design of 1 and 2 stage amplifiers ... ..	364
(v) Design of multistage amplifiers ... ..	365
(vi) Effect of feedback on frequency response ... ..	378
(vii) Design of amplifiers with flat frequency response ... ..	379
(viii) Constancy of characteristics with feedback ... ..	388
(ix) Effect of feedback on phase shift ... ..	389
4. SPECIAL APPLICATIONS OF FEEDBACK ... ..	389
5. VALVE CHARACTERISTICS AND FEEDBACK ... ..	390
(i) Triode cathode follower ... ..	390
(ii) Pentode cathode follower ... ..	393
(iii) Triode with voltage feedback ... ..	394
(iv) Pentode with voltage feedback, transformer coupled ... ..	395
(v) Cathode degenerative triode ... ..	397
(vi) Cathode degenerative pentode ... ..	399
(vii) Cathode-coupled triodes ... ..	399
(viii) Feedback over two stages ... ..	399
6. REFERENCES TO FEEDBACK ... ..	399
7. OVERLOADING OF FEEDBACK AMPLIFIERS ON TRANSIENTS ... ..	1477

## CHAPTER 8. WAVE MOTION AND THE THEORY OF MODULATION

1. INTRODUCTION TO ELECTROMAGNETIC WAVES ... ..	403
(i) Wave motion ... ..	403
(ii) Electromagnetic spectrum ... ..	404
(iii) Wave propagation ... ..	404
2. TRANSMISSION OF INTELLIGENCE ... ..	405
(i) Introduction ... ..	405
(ii) Radio telegraphy... ..	405
(iii) Radio telephony ... ..	405
3. REFERENCES ... ..	406

## CHAPTER 9. TUNED CIRCUITS

1. INTRODUCTION ... ..	407
2. DAMPED OSCILLATIONS ... ..	408
3. SERIES RESONANCE ... ..	409
4. PARALLEL RESONANCE ... ..	410
5. GENERAL CASE OF SERIES RESONANCE ... ..	412
6. SELECTIVITY AND GAIN ... ..	412
(i) Single tuned circuit ... ..	412
(ii) Coupled circuits—tuned secondary ... ..	413
(iii) Coupled circuits—tuned primary, tuned secondary... ..	414
(iv) Coupled circuits of equal Q ... ..	415
(v) Coupled circuits of unequal Q ... ..	416
7. SELECTIVITY—GRAPHICAL METHODS ... ..	416
(i) Single tuned circuit ... ..	416
(ii) Two identical coupled tuned circuits... ..	417
8. COUPLING OF CIRCUITS ... ..	418
(i) Mutual inductive coupling ... ..	418
(ii) Miscellaneous methods of coupling ... ..	418
(iii) Complex coupling ... ..	420
9. RESPONSE OF IDENTICAL AMPLIFIER STAGES IN CASCADE ... ..	421
10. UNIVERSAL SELECTIVITY CURVES ... ..	421
11. SUMMARY OF FORMULAE FOR TUNED CIRCUITS ... ..	423
12. REFERENCES ... ..	427

## CHAPTER 10. CALCULATION OF INDUCTANCE

1. SINGLE LAYER COILS OR SOLENOIDS ... ..	429
(i) Current-sheet inductance ... ..	429
(ii) Solenoids wound with spaced round wires ... ..	430
(iii) Approximate formulae ... ..	432
(iv) Design of single layer solenoid ... ..	433
(v) Magnitude of the differences between $L_s$ and $L_o$ ... ..	435
(vi) Curves for the determination of the "current-sheet" inductance ... ..	437
(vii) Effect of concentric, non-magnetic screen ... ..	438
2. MULTILAYER SOLENOIDS ... ..	441
(i) Formula for current sheet inductance ... ..	441
(ii) Correction for insulation thickness ... ..	442
(iii) Approximate formulae ... ..	442
(iv) Design of multilayer coils ... ..	443
(v) Effect of a concentric screen ... ..	444
3. TOROIDAL COILS ... ..	445
(i) Toroidal coil of circular section with single layer winding ... ..	445
(ii) Toroidal coil of rectangular section with single layer winding ... ..	445
(iii) Toroidal coil of rectangular section with multilayer winding ... ..	445
4. FLAT SPIRALS ... ..	445
(i) Accurate formulae ... ..	445
(ii) Approximate formulae ... ..	446
5. MUTUAL INDUCTANCE ... ..	446
(i) Accurate methods ... ..	446
(ii) Approximate methods ... ..	448
6. LIST OF SYMBOLS ... ..	448
7. REFERENCES ... ..	448

## CHAPTER 11. DESIGN OF RADIO FREQUENCY INDUCTORS

1. INTRODUCTION ... ..	450
2. SELF-CAPACITANCE OF COILS ... ..	451
(i) Effects of self-capacitance ... ..	451
(ii) Calculation of self-capacitance of single-layer solenoids ... ..	451
(iii) Measurement of self-capacitance ... ..	453
3. INTERMEDIATE-FREQUENCY WINDINGS ... ..	453
(i) Air-cored coils ... ..	453
(ii) Iron-cored coils ... ..	454
(iii) Expanding selectivity i-f transformers ... ..	455
(iv) Calculation of gear ratios for universal coils ... ..	456
(v) Miscellaneous considerations ... ..	458
4. MEDIUM WAVE-BAND COILS ... ..	459
(i) Air-cored coils ... ..	459
(ii) Iron-cored coils ... ..	460
(iii) Permeability tuning ... ..	461
(iv) Matching ... ..	462
5. SHORT-WAVE COILS ... ..	463
(i) Design ... ..	463
(ii) Miscellaneous features ... ..	468
6. RADIO-FREQUENCY CHOKES ... ..	474
(i) Pie-wound chokes ... ..	474
(ii) Other types ... ..	475
7. TROPIC PROOFING ... ..	476
(i) General considerations ... ..	476
(ii) Baking ... ..	476
(iii) Impregnation ... ..	477
(iv) Flash dipping ... ..	477
(v) Materials ... ..	477
8. REFERENCES ... ..	478

## PART 3: AUDIO FREQUENCIES

## CHAPTER 12. AUDIO FREQUENCY VOLTAGE AMPLIFIERS

1. INTRODUCTION ... ..	481
(i) Voltage amplifiers ... ..	481
2. RESISTANCE-CAPACITANCE COUPLED TRIODES ... ..	482
(i) Choice of operating conditions ... ..	482
(ii) Coupling condenser ... ..	483
(iii) Cathode bias ... ..	484
(iv) Fixed bias ... ..	487
(v) Grid leak bias ... ..	489
(vi) Plate voltage and current ... ..	489
(vii) Gain and distortion at the mid-frequency ... ..	490
(viii) Dynamic characteristics ... ..	491
(ix) Maximum voltage output and distortion ... ..	491
(x) Conversion factors with r.c.c. triodes ... ..	493
(xi) Input impedance and Miller effect ... ..	493
(xii) Equivalent circuit of r.c.c. triode ... ..	494
(xiii) Voltage gain and phase shift ... ..	494
(xiv) Comments on tabulated characteristics of resistance-coupled triodes ... ..	495

# CONTENTS

SECTION	PAGE
<b>3. RESISTANCE-CAPACITANCE COUPLED PENTODES</b> ... ..	496
(i) Choice of operating conditions ... ..	496
(ii) Coupling condenser ... ..	496
(iii) Screen by-pass ... ..	496
(iv) Cathode bias ... ..	499
(v) Fixed bias ... ..	501
(vi) Dynamic characteristics of pentodes ... ..	504
(vii) Gain at the mid-frequency ... ..	506
(viii) Dynamic characteristics of pentodes and comparison with triodes ... ..	508
(ix) Maximum voltage output and distortion ... ..	510
(x) Conversion factors with r.c.c. pentodes ... ..	511
(xi) Equivalent circuit of r.c.c. pentode ... ..	512
(xii) Voltage gain and phase shift ... ..	512
(xiii) Screen loadlines ... ..	513
(xiv) Combined screen and cathode loadlines and the effect of tolerances ... ..	515
(xv) Remote cut-off pentodes as r.c.c. amplifiers ... ..	516
(xvi) Multigrid valves as r.c.c. amplifiers ... ..	516
(xvii) Special applications ... ..	516
(xviii) Comments on tabulated characteristics of resistance-coupled pentodes ... ..	517
<b>4. TRANSFORMER-COUPLED VOLTAGE AMPLIFIERS</b> ... ..	517
(i) Introduction ... ..	517
(ii) Gain at the mid-frequency ... ..	517
(iii) Gain at low frequencies ... ..	517
(iv) Desirable valve characteristics ... ..	517
(v) Equivalent circuits ... ..	518
(vi) Gain and phase shift at all frequencies ... ..	518
(vii) Transformer characteristics ... ..	518
(viii) Fidelity ... ..	518
(ix) Valve loadlines ... ..	518
(x) Maximum peak output voltage ... ..	518
(xi) Transformer loading ... ..	518
(xii) Parallel feed ... ..	518
(xiii) Auto-transformer coupling ... ..	520
(xiv) Applications ... ..	520
(xv) Special applications ... ..	520
<b>5. CHOKE-COUPLED AMPLIFIERS</b> ... ..	521
(i) Performance ... ..	521
(ii) Application ... ..	521
<b>6. METHODS OF EXCITING PUSH-PULL AMPLIFIERS</b> ... ..	521
(i) Methods involving iron-cored inductors ... ..	521
(ii) Phase splitter ... ..	522
(iii) Phase inverter ... ..	524
(iv) Self-balancing phase inverter ... ..	524
(v) Self-balancing paraphase inverter ... ..	524
(vi) Common cathode impedance self-balancing inverters ... ..	526
(vii) Balanced output amplifiers with highly accurate balance ... ..	527
(viii) Cross coupled phase inverter ... ..	527
<b>7. PUSH-PULL VOLTAGE AMPLIFIERS</b> ... ..	527
(i) Introduction ... ..	527
(ii) Cathode resistors ... ..	527
(iii) Output circuit ... ..	527
(iv) Push-pull impedance-coupled amplifiers—mathematical treatment ... ..	528
(v) Phase compressor ... ..	528

## CONTENTS

SECTION	PAGE
8. IN-PHASE AMPLIFIERS ... ..	529
(i) Cathode-coupled amplifiers ... ..	529
(ii) Grounded-grid amplifiers ... ..	529
(iii) Inverted input amplifiers ... ..	529
(iv) Other forms of in-phase amplifiers ... ..	529
9. DIRECT-COUPLED AMPLIFIERS... ..	529
(i) Elementary d-c amplifiers ... ..	529
(ii) Bridge circuit ... ..	530
(iii) Cathode-coupled ... ..	531
(iv) Cathode follower ... ..	531
(v) Phase inverter ... ..	532
(vi) Screen coupled ... ..	532
(vii) Gas tube coupled ... ..	532
(viii) Modulation systems ... ..	532
(ix) Compensated d.c. amplifiers ... ..	533
(x) Bridge-balanced direct current amplifiers ... ..	533
(xi) Cascode amplifiers ... ..	533
10. STABILITY, DECOUPLING AND HUM ... ..	535
(i) Effect of common impedance in power supply ... ..	535
(ii) Plate supply by-passing ... ..	535
(iii) Plate circuit decoupling ... ..	535
(iv) Screen circuit decoupling ... ..	537
(v) Grid circuit decoupling ... ..	538
(vi) Hum in voltage amplifiers ... ..	538
11. TRANSIENTS AND PULSES IN AUDIO FREQUENCY AMPLIFIERS ... ..	540
(i) Transient distortion ... ..	540
(ii) Rectangular pulses ... ..	540
12. MULTISTAGE VOLTAGE AMPLIFIERS ... ..	541
(i) Single-channel amplifiers ... ..	541
(ii) Multi-channel amplifiers ... ..	541
13. REFERENCES ... ..	542

## CHAPTER 13. AUDIO FREQUENCY POWER AMPLIFIERS

1. INTRODUCTION ... ..	544
(i) Types of a-f power amplifiers ... ..	544
(ii) Class of operation ... ..	545
(iii) Some characteristics of power amplifiers ... ..	545
(iv) Effect of power supply on power amplifiers ... ..	547
2. CLASS A SINGLE TRIODES ... ..	548
(i) Simplified graphical conditions, power output and distortion ... ..	548
(ii) General graphical case, power output and distortion ... ..	550
(iii) Optimum operating conditions... ..	555
(iv) Loudspeaker load ... ..	558
(v) Plate circuit efficiency and power dissipation ... ..	559
(vi) Power sensitivity ... ..	559
(vii) Choke-coupled amplifier ... ..	559
(viii) Effect of a.c. filament supply ... ..	560
(ix) Overloading ... ..	560
(x) Regulation and by-passing of power supply... ..	560

# CONTENTS

SECTION	PAGE
3. CLASS A MULTI-GRID VALVES	560
(i) Introduction	560
(ii) Ideal pentodes	561
(iii) Practical pentodes—operating conditions	561
(iv) Graphical analysis—power output and distortion	563
(v) Rectification effects	565
(vi) Cathode bias	565
(vii) Resistance and inductance of transformer primary	566
(viii) Loudspeaker load	566
(ix) Effects of plate and screen regulation	568
(x) Beam power valves	569
(xi) Space charge tetrodes	569
(xii) Partial triode (“ultra-linear”) operation of pentodes	570
4. PARALLEL CLASS A AMPLIFIERS	570
5. PUSH-PULL TRIODES CLASS A, AB <sub>1</sub>	571
(i) Introduction	571
(ii) Theory of push-pull amplification	573
(iii) Power output and distortion	577
(iv) Average plate current	579
(v) Matching and the effects of mismatching	580
(vi) Cathode bias	582
(vii) Parasitics	582
6. PUSH-PULL PENTODES AND BEAM POWER AMPLIFIERS, CLASS A, AB <sub>1</sub>	583
(i) Introduction	583
(ii) Power output and distortion	583
(iii) The effect of power supply regulation	584
(iv) Matching and the effects of mismatching	584
(v) Average plate and screen currents	584
(vi) Cathode bias	585
(vii) Parasitics	585
(viii) Phase inversion in the power stage	585
(ix) Extended Class A	587
(x) Partial triode (“ultra-linear”) operation	587
7. CLASS B AMPLIFIERS AND DRIVERS	587
(i) Introduction	587
(ii) Power output and distortion—ideal conditions—Class B <sub>2</sub>	588
(iii) Power output and distortion—practical conditions—Class B <sub>2</sub>	588
(iv) Grid driving conditions...	590
(v) Design procedure for Class B <sub>2</sub> amplifiers	592
(vi) Earthed-grid cathode coupled amplifiers	592
(vii) Class B <sub>1</sub> amplifiers—quiescent push-pull	592
8. CLASS AB <sub>2</sub> AMPLIFIERS	593
(i) Introduction	593
(ii) Bias and screen stabilized Class AB <sub>2</sub> amplifier	593
(iii) McIntosh amplifier	594
9. CATHODE-FOLLOWER POWER AMPLIFIERS	596
10. SPECIAL FEATURES	596
(i) Grid circuit resistance	596
(ii) Grid bias sources	597
(iii) Miller Effect	598
(iv) 26 volt operation	598
(v) Hum from plate and screen supplies...	599
11. COMPLETE AMPLIFIERS	599
(i) Introduction	599
(ii) Design procedure and examples	599
(iii) Loudspeaker load	600
12. REFERENCES	601



# CONTENTS

SECTION

PAGE

## CHAPTER 14. FIDELITY AND DISTORTION

1.	INTRODUCTION ... ..	603
	(i) Fidelity ... ..	603
	(ii) Types of distortion ... ..	604
	(iii) Imagery for describing reproduced sound ... ..	604
2.	NON-LINEAR DISTORTION AND HARMONICS... ..	605
	(i) Non-linearity ... ..	605
	(ii) Harmonics... ..	606
	(iii) Permissible harmonic distortion ... ..	607
	(iv) Total harmonic distortion ... ..	609
	(v) Weighted distortion factor ... ..	610
	(vi) The search for a true criterion of non-linearity ... ..	610
3.	INTERMODULATION DISTORTION ... ..	611
	(i) Introduction ... ..	611
	(ii) Modulation method of measurement—r.m.s. sum ... ..	612
	(iii) Difference frequency intermodulation method ... ..	613
	(iv) Individual side-band method ... ..	613
	(v) Modulation method of measurement—peak sum ... ..	614
	(vi) Le Bel's oscillographic method ... ..	614
	(vii) Comparison between different methods ... ..	616
	(viii) Synthetic bass ... ..	616
4.	FREQUENCY DISTORTION ... ..	617
	(i) Frequency range ... ..	617
	(ii) Tonal balance ... ..	617
	(iii) Minimum audible change in frequency range ... ..	617
	(iv) Sharp peaks ... ..	618
5.	PHASE DISTORTION ... ..	618
6.	TRANSIENT DISTORTION ... ..	619
	(i) General survey ... ..	619
	(ii) Testing for transient response ... ..	619
7.	DYNAMIC RANGE AND ITS LIMITATIONS ... ..	620
	(i) Volume range and hearing ... ..	620
	(ii) Effect of volume level on frequency range ... ..	621
	(iii) Acoustical power and preferred listening levels ... ..	623
	(iv) Volume range in musical reproduction ... ..	623
	(v) The effect of noise ... ..	624
8.	SCALE DISTORTION ... ..	625
9.	OTHER FORMS OF DISTORTION ... ..	626
	(i) Frequency-modulation distortion ... ..	626
	(ii) Variation of frequency response with output level ... ..	626
	(iii) Listener fatigue ... ..	626
10.	FREQUENCY RANGE PREFERENCES ... ..	627
	(i) Tests by Chinn and Eisenberg ... ..	627
	(ii) Tests by Olson ... ..	627
	(iii) Single channel versus dual-channel tests ... ..	627
	(iv) Summing up ... ..	628
11.	SPEECH REPRODUCTION ... ..	628
	(i) The characteristics of speech ... ..	628
	(ii) Articulation ... ..	628
	(iii) Masking of speech by noise ... ..	629
	(iv) Distortion in speech reproduction ... ..	629
	(v) Frequency ranges for speech ... ..	630

## CONTENTS

SECTION	PAGE
12. HIGH FIDELITY REPRODUCTION ... ..	630
(i) The target of high fidelity ... ..	630
(ii) Practicable high fidelity... ..	630
(iii) The ear as a judge of fidelity... ..	632
13. REFERENCES ... ..	632

## CHAPTER 15. TONE COMPENSATION AND TONE CONTROL

1. INTRODUCTION ... ..	635
(i) The purpose of tone compensation ... ..	635
(ii) Tone control ... ..	636
(iii) General considerations ... ..	636
(iv) Distortion due to tone control ... ..	636
(v) Calculations involving decibels per octave ... ..	637
(vi) Attenuation expressed as a time constant ... ..	638
(vii) The elements of tone control filters ... ..	639
(viii) Fundamental circuit incorporating R and C ... ..	639
(ix) Damping of tuned circuits ... ..	639
(x) Tolerances of elements ... ..	639
2. BASS BOOSTING ... ..	640
(i) General remarks ... ..	640
(ii) Circuits not involving resonance or negative feedback ... ..	640
(iii) Methods incorporating resonant circuits ... ..	644
(iv) Circuits involving feedback ... ..	645
(v) Regeneration due to negative resistance characteristic ... ..	648
3. BASS ATTENUATION ... ..	649
(i) General remarks ... ..	649
(ii) Bass attenuation by grid coupling condensers ... ..	649
(iii) Bass attenuation by cathode resistor by-passing ... ..	649
(iv) Bass attenuation by screen by-passing ... ..	650
(v) Bass attenuation by reactance shunting ... ..	650
(vi) Bass attenuation by negative feedback ... ..	651
(vii) Bass attenuation by Parallel-T network ... ..	651
(viii) Bass attenuation using Constant k filters ... ..	652
(ix) Bass attenuation using M-derived filters ... ..	652
4. COMBINED BASS TONE CONTROLS ... ..	653
(i) Stepped controls ... ..	653
(ii) Continuously variable controls ... ..	653
5. TREBLE BOOSTING ... ..	653
(i) General remarks ... ..	653
(ii) Circuits not involving resonance or negative feedback ... ..	653
(iii) Methods incorporating resonant circuits ... ..	654
(iv) Circuits involving feedback ... ..	655
6. TREBLE ATTENUATION ... ..	655
(i) General remarks ... ..	655
(ii) Attenuation by shunt capacitance ... ..	655
(iii) Treble attenuation by filter networks ... ..	657
(iv) Treble attenuation in negative feedback amplifiers ... ..	657
7. COMBINED TREBLE TONE CONTROLS ... ..	658
8. COMBINED BASS AND TREBLE TONE CONTROLS ... ..	658
(i) Stepped controls—general ... ..	658
(ii) Quality switch ... ..	659
(iii) Universal step-type tone control not using inductors ... ..	660
(iv) Universal step-type tone control using inductors ... ..	661
(v) Fixed bass and treble boosting ... ..	662

## CONTENTS

SECTION	PAGE
(vi) Step-type tone control using negative feedback ... ..	662
(vii) Continuously-variable controls—general ... ..	662
(viii) Single control continuously-variable tone controls ... ..	662
(ix) Ganged continuously-variable tone controls ... ..	664
(x) Dual control continuously-variable tone controls ... ..	664
<b>9. FEEDBACK TO PROVIDE TONE CONTROL</b> ... ..	<b>669</b>
(i) Introduction ... ..	669
(ii) Amplifiers with feedback providing tone control ... ..	669
(iii) Whistle filters using feedback ... ..	672
<b>10. AUTOMATIC FREQUENCY-COMPENSATED VOLUME CONTROL</b> ... ..	<b>672</b>
(i) Introduction ... ..	672
(ii) Methods incorporating a tapped potentiometer ... ..	672
(iii) Methods incorporating step-type controls ... ..	673
(iv) Method incorporating inverse volume expansion with multi-channel amplifier ... ..	673
<b>11. WHISTLE FILTERS</b> ... ..	<b>673</b>
(i) Resonant circuit filters ... ..	673
(ii) Narrow band rejection filter ... ..	675
(iii) Crystal filters ... ..	675
(iv) Parallel-T network ... ..	675
(v) Filters incorporating L and C ... ..	676
<b>12. OTHER METHODS OF TONE CONTROL</b> ... ..	<b>676</b>
(i) Multiple-channel amplifiers ... ..	676
(ii) Synthetic bass ... ..	676
<b>13. THE LISTENER AND TONE CONTROL</b> ... ..	<b>677</b>
<b>14. EQUALIZER NETWORKS</b> ... ..	<b>677</b>
<b>15. REFERENCES</b> ... ..	<b>677</b>

## CHAPTER 16. VOLUME EXPANSION, COMPRESSION AND LIMITING

<b>1. GENERAL PRINCIPLES</b> ... ..	<b>679</b>
(i) Introduction ... ..	679
(ii) An ideal system ... ..	680
(iii) Practical problems in volume expansion ... ..	680
(iv) Distortion ... ..	681
(v) General comments ... ..	681
<b>2. VOLUME COMPRESSION</b> ... ..	<b>681</b>
(i) Introduction ... ..	681
(ii) Peak limiters ... ..	682
(iii) Volume limiters ... ..	683
(iv) Distortion caused by peak limiters or volume limiters ... ..	683
(v) Volume compression ... ..	683
(vi) Volume compression plus limiting ... ..	684
(vii) Compression of commercial speech ... ..	684
<b>3. GAIN CONTROL DEVICES</b> ... ..	<b>684</b>
(i) Remote cut-off pentodes ... ..	684
(ii) Pentagrids and triode-hexodes ... ..	685
(iii) Plate resistance control ... ..	685
(iv) Negative feedback ... ..	685
(v) Lamps ... ..	685
(vi) Suppressor-grid control ... ..	686

## CONTENTS

SECTION	PAGE
4. VOLUME EXPANSION ... ..	686
(i) Introduction ... ..	686
(ii) Expanders incorporating lamps ... ..	687
(iii) Expanders utilizing feedback ... ..	688
(iv) Expanders incorporating remote cut-off pentodes ... ..	688
(v) Expanders incorporating remote cut-off triodes ... ..	689
(vi) Expanders incorporating suppressor-grid controlled pentodes ... ..	689
(vii) Expanders incorporating valves with five grids ... ..	691
(viii) Expanders incorporating plate resistance control ... ..	692
5. PUBLIC ADDRESS A.V.C. ... ..	693
6. SPEECH CLIPPERS ... ..	693
7. NOISE PEAK AND OUTPUT LIMITERS ... ..	694
(i) Introduction ... ..	694
(ii) Instantaneous noise peak limiters ... ..	694
(iii) Output limiters ... ..	698
(iv) General remarks ... ..	699
8. REFERENCES ... ..	699
<b>CHAPTER 17. REPRODUCTION FROM RECORDS</b>	
1. INTRODUCTION TO DISC RECORDING ... ..	701
(i) Methods used in sound recording ... ..	701
(ii) Principles of lateral recording ... ..	702
(iii) Frequency range ... ..	704
(iv) Surface noise and dynamic range ... ..	704
(v) Processing... ..	705
(vi) Turntables and driving mechanism ... ..	705
(vii) Automatic record changers ... ..	705
2. DISCS AND STYLI ... ..	706
(i) General information on discs ... ..	706
(ii) Dimensions of records and grooves ... ..	706
(iii) Styli ... ..	709
(iv) Pinch effect ... ..	711
(v) Radius compensation ... ..	711
(vi) Record and stylus wear ... ..	712
3. PICKUPS ... ..	714
(i) General survey ... ..	714
(ii) Electro-magnetic (moving iron) pickups ... ..	717
(iii) Dynamic (moving coil) pickups ... ..	719
(iv) Piezo-electric (crystal) pickups... ..	720
(v) Magnetostriction pickups ... ..	721
(vi) Strain-sensitive pickups ... ..	721
(vii) Ribbon pickups ... ..	722
(viii) Capacitance pickups ... ..	722
(ix) Eddy-current pickups ... ..	723
4. TRACKING ... ..	723
(i) General survey of the problem ... ..	723
(ii) How to design for minimum distortion ... ..	725
(iii) The influence of stylus friction ... ..	726
5. RECORDING CHARACTERISTICS, EQUALIZERS AND AMPLIFIERS ... ..	727
(i) Recording characteristics ... ..	727
(ii) Pre-amplifiers for use with pickups ... ..	732
(iii) Introduction to equalizers ... ..	732
(iv) High-frequency attenuation (scratch filter) ... ..	737
(v) Equalizers for electro-magnetic pickups ... ..	738

## CONTENTS

SECTION	PAGE
(vi) Equalizers for crystal pickups ... ..	741
(vii) Equalizers applying negative feedback to the pickup ... ..	743
(viii) Miscellaneous details regarding equalizing amplifiers ... ..	743
(ix) Complete amplifiers ... ..	744
(x) Pickups for connection to radio receivers ... ..	751
(xi) Frequency test records ... ..	752
<b>6. DISTORTION AND UNDESIRABLE EFFECTS</b> ... ..	<b>757</b>
(i) Tracing distortion and pinch effect ... ..	757
(ii) Playback loss ... ..	760
(iii) Wow, and the effects of record warping ... ..	760
(iv) Distortion due to stylus wear ... ..	761
(v) Noise modulation ... ..	761
(vi) Pickup distortion ... ..	762
(vii) Acoustical radiation ... ..	762
(viii) Distortion in recording ... ..	762
<b>7. NOISE REDUCTION</b> ... ..	<b>763</b>
(i) Analysis of noise ... ..	763
(ii) High-frequency attenuation ... ..	763
(iii) High-frequency pre-emphasis and de-emphasis ... ..	763
(iv) Volume expansion ... ..	763
(v) Olson noise suppressor ... ..	763
(vi) Scott dynamic noise suppressor ... ..	764
(vii) Price balanced clipper noise suppressor ... ..	765
<b>8. LACQUER DISC HOME RECORDING (DIRECT PLAYBACK)</b> ... ..	<b>766</b>
(i) General description ... ..	766
(ii) Recording characteristic ... ..	766
(iii) Cutting stylus ... ..	767
(iv) Cutter head ... ..	767
(v) Equalization of cutter ... ..	767
(vi) Motor and turntable ... ..	767
(vii) Amplifier ... ..	767
(viii) Pickups for use on lacquer discs ... ..	768
(ix) Recording with embossed groove ... ..	768
<b>9. REPRODUCTION FROM TRANSCRIPTION DISCS</b> ... ..	<b>769</b>
(i) Introduction ... ..	769
(ii) Characteristics of record material, wear and noise ... ..	769
(iii) Sound track ... ..	770
(iv) Recording characteristics and equalization ... ..	770
(v) Translation loss and radius compensation ... ..	770
<b>10. REFERENCES TO LATERAL DISC RECORDING</b> ... ..	<b>771</b>

## CHAPTER 18. MICROPHONES, PRE-AMPLIFIERS, ATTENUATORS AND MIXERS

<b>1. MICROPHONES</b> ... ..	<b>775</b>
(i) General survey ... ..	775
(ii) Carbon microphones ... ..	777
(iii) Condenser microphones ... ..	778
(iv) Crystal and ceramic microphones ... ..	778
(v) Moving coil (dynamic) microphones ... ..	779
(vi) Pressure ribbon microphones ... ..	779
(vii) Velocity ribbon microphones ... ..	779
(viii) Throat microphones ... ..	780
(ix) Lapel microphones ... ..	780
(x) Lip microphones ... ..	780

## CONTENTS

SECTION	PAGE
(xi) The directional characteristics of microphones ... ..	780
(xii) The equalization of microphones ... ..	781
(xiii) Microphone transformers ... ..	781
(xiv) Standards for microphones ... ..	781
<b>2. PRE-AMPLIFIERS</b> ... ..	<b>782</b>
(i) Introduction ... ..	782
(ii) Noise ... ..	782
(iii) Hum ... ..	784
(iv) Microphony ... ..	786
(v) Valves for use in pre-amplifiers ... ..	786
(vi) Microphone pre-amplifiers ... ..	788
(vii) Pickup pre-amplifiers ... ..	793
(viii) Gain-controlled pre-amplifiers ... ..	793
(ix) Standard pre-amplifiers for broadcasting ... ..	793
(x) Standard pre-amplifiers for sound equipment ... ..	793
<b>3. ATTENUATORS AND MIXERS</b> ... ..	<b>794</b>
(i) Potentiometer type attenuators (volume controls) ... ..	794
(ii) Single section attenuators—constant impedance ... ..	795
(iii) Single section attenuators—constant impedance in one direction only ... ..	795
(iv) Multiple section attenuators ... ..	796
(v) Electronic attenuators ... ..	797
(vi) Mixers and faders—general ... ..	798
(vii) Non-constant impedance mixers and faders ... ..	798
(viii) Constant impedance mixers and faders ... ..	801
<b>4. REFERENCES</b> ... ..	<b>804</b>

## CHAPTER 19. UNITS FOR THE MEASUREMENT OF GAIN AND NOISE

<b>1. BELS AND DECIBELS</b> ... ..	<b>806</b>
(i) Power relationships expressed in bels and decibels ... ..	806
(ii) Voltage and current relationships expressed in decibels ... ..	807
(iii) Absolute power and voltage expressed in decibels ... ..	807
(iv) Microphone output expressed in decibels ... ..	808
(v) Pickup output expressed in decibels ... ..	810
(vi) Amplifier gain expressed in decibels ... ..	810
(vii) Combined microphone and amplifier gain expressed in decibels ... ..	811
(viii) Loudspeaker output expressed in decibels ... ..	812
(ix) Sound system rating ... ..	812
(x) Tables and charts of decibel relationships ... ..	813
(xi) Nomogram for adding decibel-expressed quantities ... ..	821
(xii) Decibels, slide rules and mental arithmetic ... ..	822
<b>2. VOLUME INDICATORS AND VOLUME UNITS</b> ... ..	<b>823</b>
(i) Volume indicators ... ..	823
(ii) Volume units ... ..	824
<b>3. INDICATING INSTRUMENTS</b> ... ..	<b>825</b>
(i) Decibel meters ... ..	825
(ii) Power output meters ... ..	825
(iii) Volume indicators ... ..	825
(iv) Acoustical instruments ... ..	825
<b>4. NEPERS AND TRANSMISSION UNITS</b> ... ..	<b>825</b>
(i) Nepers ... ..	825
(ii) Transmission units ... ..	826

## CONTENTS

SECTION	PAGE
5. LOUDNESS	826
(i) Introduction to loudness	826
(ii) The phon	826
(iii) Loudness units	827
6. THE MEASUREMENT OF SOUND LEVEL AND NOISE...	827
(i) Introduction	827
(ii) The sound level meter	826
(iii) The measurement of noise in amplifiers	829
(iv) The measurement of radio noise	829
7. REFERENCES	830

## CHAPTER 20. LOUDSPEAKERS

1. INTRODUCTION	831
(i) Types of loudspeakers	831
(ii) Direct radiator loudspeakers	831
(iii) Horn loudspeakers	832
(iv) Headphones	832
(v) Loudspeaker characteristics	833
(vi) Amplitude of cone movement	834
(vii) Good qualities of loudspeakers	834
(viii) Loudspeaker grilles	835
2. CHARACTERISTICS OF MOVING-COIL CONE LOUDSPEAKERS	835
(i) Rigid (piston) cone in an infinite flat baffle	835
(ii) Practical cones...	835
(iii) Special constructions for wide frequency range	836
(iv) Impedance and phase angle	837
(v) Frequency response	838
(vi) Efficiency	839
(vii) Directional characteristics	839
(viii) Field magnet	840
(ix) Hum bucking coil	840
(x) Damping	840
3. BAFFLES AND ENCLOSURES FOR DIRECT-RADIATOR LOUDSPEAKERS	842
(i) Flat baffles	842
(ii) Open back cabinets	842
(iii) Enclosed cabinet loudspeakers	843
(iv) Acoustical phase inverter ("vented baffle")	845
(v) Acoustical labyrinth loudspeakers	850
(vi) The R-J loudspeaker	850
(vii) Design of exterior of cabinet	850
4. HORN LOUDSPEAKERS	851
(i) Introduction	851
(ii) Conical horns	851
(iii) Exponential horns	851
(iv) Hyperbolic exponential horns	853
(v) Horn loudspeakers—general	854
(vi) Folded horn loudspeakers	856
(vii) High-frequency horns	858
(viii) Combination horn and phase inverter loudspeakers for personal radio receivers	859
(ix) Material for making horns	859
5. DUAL AND TRIPLE SYSTEM LOUDSPEAKERS	860
(i) Introduction	860
(ii) Choice of the cross-over frequency	860

## CONTENTS

SECTION		PAGE
	(iii) The overlap region ... ..	861
	(iv) Compromise arrangements ... ..	861
6.	LOUDSPEAKERS IN OPERATION ... ..	861
	(i) Loudness ... ..	861
	(ii) Power required ... ..	861
	(iii) Acoustics of rooms ... ..	864
	(iv) Loudspeaker placement ... ..	865
	(v) Stereophonic reproduction ... ..	865
	(vi) Sound reinforcing systems ... ..	866
	(vii) Open air Public Address ... ..	867
	(viii) Inter-communicating systems ... ..	867
	(ix) Background music in factories ... ..	867
7.	DISTORTION IN LOUDSPEAKERS ... ..	868
	(i) Non-linearity ... ..	868
	(ii) Frequency-modulation distortion in loudspeakers ... ..	869
	(iii) Transient distortion ... ..	869
	(iv) Sub-harmonics and sub-frequencies ... ..	871
	(v) Intermodulation distortion ... ..	871
8.	SUMMARY OF ACOUSTICAL DATA ... ..	871
	(i) Definitions in acoustics ... ..	871
	(ii) Electrical, mechanical and acoustical equivalents ... ..	872
	(iii) Velocity and wavelength of sound ... ..	872
	(iv) Musical scales ... ..	873
9.	STANDARDS FOR LOUDSPEAKERS ... ..	874
	(i) Voice coil impedance for radio receivers ... ..	874
	(ii) Loudspeaker standard ratings for sound equipment ... ..	874
10.	REFERENCES TO LOUDSPEAKERS ... ..	876

## CHAPTER 21. THE NETWORK BETWEEN THE POWER VALVE AND THE LOUDSPEAKER

1.	LOUDSPEAKER "MATCHING" ... ..	880
	(i) Loudspeaker characteristics and matching ... ..	880
	(ii) Optimum plate resistance ... ..	880
	(iii) Procedure for "matching" loudspeakers to various types of amplifiers ... ..	881
2.	MULTIPLE AND EXTENSION LOUDSPEAKERS ... ..	882
	(i) Multiple loudspeakers—general ... ..	882
	(ii) Sound systems ... ..	883
	(iii) Extension loudspeakers ... ..	883
	(iv) Operation of loudspeakers at long distances from amplifier ... ..	886
3.	LOUDSPEAKER DIVIDER NETWORKS ... ..	887
4.	REFERENCES ... ..	889

## PART 4: RADIO FREQUENCIES

### CHAPTER 22. AERIALS AND TRANSMISSION LINES

1.	INTRODUCTION ... ..	890
2.	THE TRANSMISSION LINE ... ..	890
	(i) Introduction ... ..	890
	(ii) The correct termination for a transmission line ... ..	890
	(iii) Impedance-transforming action of a transmission line ... ..	891



## CONTENTS

SECTION	PAGE
3. AERIALS AND POWER TRANSFER ... ..	892
(i) Introduction ... ..	892
(ii) Power transfer ... ..	892
4. CHARACTERISTICS OF AERIALS ... ..	893
(i) Effective area of a receiving aerial ... ..	893
(ii) The power gain of an aerial ... ..	894
(iii) The beam-width of an aerial ... ..	894
5. EFFECTS OF THE EARTH ON THE PERFORMANCE OF AN AERIAL ... ..	894
(i) Introduction ... ..	894
(ii) A perfectly-conducting earth ... ..	894
(iii) An imperfectly conducting earth ... ..	896
(iv) The attenuation of radio waves in the presence of an imper- fectly-reflecting earth ... ..	896
6. THE EFFECT OF THE IONOSPHERE ON THE RECEPTION OF RADIO SIGNALS ...	901
7. THE IMPEDANCE OF AN AERIAL ... ..	901
(i) Introduction ... ..	901
(ii) Resistive component of impedance ... ..	902
(iii) Reactive component of impedance ... ..	903
(iv) Characteristic impedance of aerial ... ..	903
(v) Examples of calculations ... ..	903
(vi) Dipoles ... ..	904
(vii) Loop aerials ... ..	905
8. DUMMY AERIALS ... ..	906
9. TYPES OF AERIAL USED FOR BROADCAST RECEPTION ... ..	907
(i) Introduction ... ..	907
(ii) Medium-frequency receiving aerials ... ..	907
(iii) Short-wave receiving aerials ... ..	908
(iv) V-H-F aerials ... ..	909
10. REFERENCES ... ..	911

## CHAPTER 23. RADIO FREQUENCY AMPLIFIERS

1. INTRODUCTION ... ..	912
(i) Aerial coupling ... ..	912
(ii) Tuning methods ... ..	913
(iii) R-F amplifiers ... ..	913
(iv) Design considerations ... ..	914
2. AERIAL STAGES ... ..	915
(i) Difficulties involved ... ..	915
(ii) Generalized coupling networks ... ..	915
(iii) Mutual inductance coupling ... ..	916
(iv) Tapped inductance ... ..	920
(v) Capacitance coupling ... ..	921
(vi) General summary ... ..	921
3. R-F AMPLIFIERS ... ..	922
(i) Reasons for using r-f stage ... ..	922
(ii) Mutual-inductance-coupled stage ... ..	922
(iii) Parallel tuned circuit ... ..	923
(iv) Choke-capacitance coupling ... ..	924
(v) Untuned and pre-tuned stages ... ..	924
(vi) Grounded grid stages ... ..	925
4. IMAGE REJECTION ... ..	925
(i) Meaning of image rejection ... ..	925
(ii) Image rejection due to aerial stage ... ..	926
(iii) Other considerations ... ..	926

## CONTENTS

SECTION	PAGE
5. EFFECTS OF VALVE INPUT ADMITTANCE ... .. .	927
(i) Important general considerations ... .. .	927
(ii) Input loading of receiving valves at radio frequencies ... .. .	928
(A) Input conductance ... .. .	929
(B) Cold input conductance ... .. .	929
(C) Hot input conductance ... .. .	930
(D) Change in input capacitance ... .. .	932
(E) Reduction of detuning effect ... .. .	933
6. VALVE AND CIRCUIT NOISE ... .. .	935
(i) Thermal agitation noise ... .. .	935
(ii) Shot noise ... .. .	936
(iii) Induced grid noise ... .. .	939
(iv) Total noise calculations ... .. .	940
(v) Sample circuit calculations ... .. .	941
(vi) Conclusions ... .. .	942
7. INSTABILITY IN R-F AMPLIFIERS ... .. .	942
(i) Causes of instability ... .. .	942
(ii) Inter-electrode capacitance coupling ... .. .	943
(iii) Summary ... .. .	944
8. DISTORTION ... .. .	944
(i) Modulation envelope distortion ... .. .	945
(ii) Cross modulation distortion ... .. .	945
9. BIBLIOGRAPHY ... .. .	945

## CHAPTER 24. OSCILLATORS

1. INTRODUCTION ... .. .	947
2. TYPES OF OSCILLATOR CIRCUITS ... .. .	949
(i) Tuned plate oscillator ... .. .	949
(ii) Tuned grid oscillator ... .. .	950
(iii) Hartley oscillator ... .. .	951
(iv) Colpitts oscillator ... .. .	952
(v) Electron-coupled oscillator ... .. .	953
(vi) Negative transconductance oscillators ... .. .	953
3. CLASS A <sub>1</sub> B AND C OSCILLATORS ... .. .	954
4. CAUSES OF OSCILLATOR FREQUENCY VARIATION ... .. .	955
(i) General ... .. .	955
(ii) Changes due to supply voltage ... .. .	955
(iii) Temperature and humidity changes ... .. .	955
(iv) Oscillator harmonics ... .. .	956
5. METHODS OF FREQUENCY STABILIZATION ... .. .	957
6. UNSTABLE OSCILLATION ... .. .	958
7. PARASITIC OSCILLATION ... .. .	959
8. METHODS USED IN PRACTICAL DESIGN ... .. .	959
9. BEAT FREQUENCY OSCILLATORS ... .. .	960
10. BIBLIOGRAPHY ... .. .	961

## CHAPTER 25. FREQUENCY CONVERSION AND TRACKING

1. THE OPERATION OF FREQUENCY CONVERTERS AND MIXERS ... .. .	962
(i) Introduction ... .. .	962
(ii) General analysis of operation common to all types ... .. .	964
(iii) The oscillator section of converter tubes ... .. .	968
(iv) The detailed operation of the modulator or mixer section of the converter stage ... .. .	968

## CONTENTS

SECTION		PAGE
	(v) Conclusion ... ..	984
	(vi) Appendix ... ..	985
2.	CONVERTER APPLICATIONS ... ..	987
	(i) Broadcast frequencies ... ..	987
	(ii) Short waves ... ..	990
	(iii) Types of converters ... ..	996
3.	SUPERHETERODYNE TRACKING... ..	1002
	(i) General ... ..	1002
	(ii) (A) Formulae and charts for superheterodyne oscillator design ... ..	1005
	(B) Worked examples ... ..	1011
	(iii) (A) Padded signal circuits ... ..	1013
	(B) Worked example ... ..	1015
4.	REFERENCES ... ..	1017

### CHAPTER 26. INTERMEDIATE FREQUENCY AMPLIFIERS

1.	CHOICE OF FREQUENCY ... ..	1020
	(i) Reasons for selection of different frequencies ... ..	1020
	(ii) Commonly accepted intermediate frequencies ... ..	1021
2.	NUMBER OF STAGES ... ..	1021
3.	COMMONLY USED CIRCUITS ... ..	1022
	(i) Mutual inductance coupling ... ..	1023
	(ii) Shunt capacitance coupling ... ..	1023
	(iii) Composite i-f transformers ... ..	1024
4.	DESIGN METHODS ... ..	1025
	(i) General ... ..	1025
	(ii) Critically-coupled transformers ... ..	1026
	(A) Design equations and table ... ..	1026
	(B) Example ... ..	1028
	(C) Design extension ... ..	1029
	(D) Conclusions ... ..	1030
	(E) k measurement ... ..	1030
	(iii) Over-coupled transformers ... ..	1031
	(A) Design equations and table ... ..	1031
	(B) Example ... ..	1033
	(C) k measurement (when k is high) ... ..	1033
	(iv) Under-coupled transformers and single tuned circuits ... ..	1034
	(A) Single tuned circuit equations ... ..	1034
	(B) Example ... ..	1035
	(C) Under-coupled transformer equations ... ..	1035
	(D) Example ... ..	1036
	(v) F-M i-f transformers ... ..	1037
	(vi) I-F transformer construction ... ..	1041
	(vii) Appendix : Calculation of coupling co-efficients ... ..	1043
5.	VARIABLE SELECTIVITY... ..	1048
	(i) General considerations ... ..	1048
	(ii) Automatic variable selectivity ... ..	1049
6.	VARIABLE BANDWIDTH CRYSTAL FILTERS ... ..	1050
	(i) Behaviour of equivalent circuit ... ..	1050
	(ii) Variable bandwidth crystal filters ... ..	1052
	(iii) Design of variable bandwidth i-f crystal filter circuits ... ..	1053
	(A) Simplifying assumptions ... ..	1053
	(B) Gain ... ..	1053
	(C) Gain variation with bandwidth change ... ..	1054
	(D) Selectivity ... ..	1055

# CONTENTS

SECTION	PAGE
(E) Crystal constants ... ..	1056
(F) Position of filter in circuit ... ..	1057
(G) Other types of crystal filters ... ..	1057
(iv) Design example ... ..	1057
7. DETUNING DUE TO A.V.C. ... ..	1061
(i) Causes of detuning ... ..	1061
(ii) Reduction of detuning effects ... ..	1062
8. STABILITY ... ..	1065
(i) Design data ... ..	1065
(ii) Neutralizing circuits ... ..	1065
9. DISTORTION ... ..	1067
(i) Amplitude modulation i-f stages ... ..	1067
(ii) Frequency modulation i-f stages ... ..	1068
10. REFERENCES ... ..	1069

## CHAPTER 27. DETECTION AND AUTOMATIC VOLUME CONTROL

1. A-M DETECTORS ... ..	1072
(i) Diodes ... ..	1072
(A) General ... ..	1072
(B) Diode curves ... ..	1075
(C) Quantitative design data ... ..	1075
(D) Miscellaneous data ... ..	1081
(ii) Other forms of detectors ... ..	1082
(A) Grid detection ... ..	1082
(B) Power grid detection ... ..	1084
(C) Plate detection ... ..	1084
(D) Reflex detection ... ..	1085
(E) Regenerative detectors ... ..	1086
(F) Superregenerative detectors ... ..	1087
2. F-M DETECTORS ... ..	1088
(i) Types of detectors in general use ... ..	1088
(ii) General principles ... ..	1088
(iii) Phase discriminators ... ..	1088
(A) General ... ..	1088
(B) Design data ... ..	1090
(C) Design example ... ..	1091
(iv) Ratio detectors ... ..	1095
(A) General ... ..	1095
(B) Operation ... ..	1097
(C) Types of circuit ... ..	1098
(D) Design considerations ... ..	1099
(E) Practical circuits ... ..	1101
(F) Measurement on ratio detectors ... ..	1102
3. AUTOMATIC VOLUME CONTROL ... ..	1105
(i) Introduction ... ..	1105
(ii) Simple a.v.c. ... ..	1105
(iii) Delayed a.v.c. ... ..	1106
(iv) Methods of feed ... ..	1109
(v) Typical circuits ... ..	1111
(vi) A.V.C. application ... ..	1111
(vii) Amplified a.v.c. ... ..	1112
(viii) Audio a.v.c. ... ..	1113
(ix) Modulation rise ... ..	1114

## CONTENTS

SECTION	PAGE
(x) A.V.C. with battery valves ... ..	1114
(xi) Special case with simple a.v.c. ... ..	1115
(xii) The a.v.c. filter and its time constants ... ..	1115
(xiii) A.V.C. characteristics ... ..	1117
(xiv) An improved form of a.v.c. characteristic ... ..	1118
(xv) Design methods ... ..	1120
4. MUTING (Q.A.V.C.) ... ..	1125
(i) General operation ... ..	1125
(ii) Typical circuits ... ..	1125
(iii) Circuits used with F-M receivers ... ..	1128
5. NOISE LIMITING ... ..	1130
6. TUNING INDICATORS ... ..	1132
(i) Miscellaneous ... ..	1132
(ii) Electron Ray tuning indicators ... ..	1133
(iii) Null point indicator using Electron Ray tube ... ..	1134
(iv) Indicators for F-M receivers ... ..	1135
7. CRYSTAL DETECTORS ... ..	1136
(i) Old type crystal detectors ... ..	1136
(ii) Fixed germanium crystal detectors ... ..	1136
(iii) Fixed silicon crystal detectors ... ..	1137
(iv) Theory of crystal rectification ... ..	1138
(v) Transistors ... ..	1138
8. REFERENCES ... ..	1138

### CHAPTER 28. REFLEX AMPLIFIERS

1. GENERAL DESCRIPTION ... ..	1140
(i) Description ... ..	1140
(ii) Advantages and disadvantages of reflex receivers ... ..	1140
2. SOME CHARACTERISTICS OF REFLEX SUPERHET. RECEIVERS ... ..	1142
(i) Playthrough (residual volume effect) ... ..	1142
(ii) Over-loading ... ..	1142
(iii) Automatic volume control ... ..	1142
(iv) Reduction in percentage modulation ... ..	1143
(v) Negative feedback ... ..	1143
(vi) Operating conditions of reflex stage ... ..	1143
3. DESIGN OF PLATE REFLEX SUPERHET. RECEIVERS ... ..	1143
(i) General considerations ... ..	1143
(ii) Full a.v.c. applied to both stages ... ..	1143
(iii) Fractional a.v.c. applied to both stages ... ..	1143
(iv) Full a.v.c. on converter, fractional a.v.c. on reflex stage ... ..	1144
4. DESIGN OF SCREEN REFLEX SUPERHET. RECEIVERS ... ..	1145
(i) Screen reflex receivers ... ..	1145
(ii) Comparison between plate and screen reflexing ... ..	1146
5. DESIGN OF T.R.F. REFLEX RECEIVERS ... ..	1146
6. REFERENCES TO REFLEX AMPLIFIERS AND REFLEX RECEIVERS ... ..	1146

### CHAPTER 29. LIMITERS AND AUTOMATIC FREQUENCY CONTROL

1. LIMITERS ... ..	1147
(i) General ... ..	1147
(ii) Typical circuits for F-M receivers ... ..	1149
2. AUTOMATIC FREQUENCY CONTROL ... ..	1150
(i) General principles ... ..	1150
(ii) Discriminators for a.f.c. ... ..	1152
(iii) Electronic reactances ... ..	1156
3. REFERENCES ... ..	1160

## PART 5: RECTIFICATION, REGULATION, FILTERING AND HUM

## CHAPTER 30. RECTIFICATION

1. INTRODUCTION TO RECTIFICATION	1161
(i) Principles of rectification	1161
(ii) Rectifier valves and types of service	1164
(iii) The use of published curves	1165
(iv) Selenium and copper oxide rectifiers	1169
2. RECTIFICATION WITH CONDENSER INPUT FILTER	1170
(i) Symbols and definitions	1170
(ii) Rectification with condenser input filter	1170
(iii) To determine peak and average diode currents	1174
(iv) To determine ripple percentage	1177
(v) To determine the transformer secondary r.m.s. current	1177
(vi) Procedure when complete published data are not available	1177
(vii) Approximations when the capacitance is large	1180
(viii) Peak hot-switching transient plate current	1180
(ix) The effect of ripple	1181
3. RECTIFICATION WITH CHOKE INPUT FILTER	1182
(i) Rectification with choke input filter	1182
(ii) Initial transient current	1185
4. TRANSFORMER HEATING	1185
5. VOLTAGE MULTIPLYING RECTIFIERS	1186
(i) General	1186
(ii) Voltage doublers	1186
(iii) Voltage triplers	1187
(iv) Voltage quadruplers	1187
6. SHUNT DIODE BIAS SUPPLIES	1188

## CHAPTER 31. FILTERING AND HUM

1. INDUCTANCE-CAPACITANCE FILTERS	1192
2. RESISTANCE-CAPACITANCE FILTERS	1194
3. PARALLEL-T FILTER NETWORKS	1194
4. HUM—GENERAL	1196
(i) Hum due to conditions within the valves	1196
(ii) Hum due to circuit design and layout	1198
(iii) Hum levels in receivers and amplifiers	1199
5. HUM NEUTRALIZING	1200
6. REFERENCES	1201

## CHAPTER 32. VIBRATOR POWER SUPPLIES

1. VIBRATORS—GENERAL PRINCIPLES	1202
(i) Operation	1202
(ii) Vibrator types	1202
(iii) Choice of vibrator	1203
(iv) Coil energizing	1204
(v) Waveform and time efficiency	1205
(vi) Standards for vibrators for auto-radio	1205

## CONTENTS

SECTION	PAGE
2. VIBRATOR TRANSFORMER DESIGN ... ..	1205
(i) General considerations ... ..	1205
(ii) Transformer calculations ... ..	1206
(iii) Standards for vibrator power transformers ... ..	1207
3. TIMING CAPACITANCE ... ..	1207
(i) The use of the timing capacitance ... ..	1207
(ii) Calculation of timing capacitance value ... ..	1207
(iii) Percentage closure ... ..	1208
(iv) Effect of flux density on timing capacitance value ... ..	1208
4. ELIMINATION OF VIBRATOR INTERFERENCE ... ..	1210
5. 12, 24 AND 32 VOLT VIBRATOR SUPPLIES ... ..	1211

### CHAPTER 33. CURRENT AND VOLTAGE REGULATORS

1. CURRENT REGULATORS ... ..	1213
(i) Barretters ... ..	1213
(ii) Negative temperature coefficient resistors (Thermistors) ... ..	1214
2. VOLTAGE REGULATORS ... ..	1214
(i) Gaseous tube voltage regulators ... ..	1214
(ii) Valve voltage regulators ... ..	1215
3. REFERENCES ... ..	1222

## PART 6 : COMPLETE RECEIVERS

### CHAPTER 34. TYPES OF A-M RECEIVERS

1. INTRODUCTION AND SIMPLE RECEIVERS ... ..	1223
(i) Types of receivers ... ..	1223
(ii) Crystal sets ... ..	1223
(iii) Regenerative receivers ... ..	1223
(iv) Superheterodyne receivers ... ..	1224
(v) Tuned radio-frequency receivers ... ..	1224
2. THE SUPERHETERODYNE ... ..	1225
3. THE SYNCHRODYNE ... ..	1226
4. REFERENCES ... ..	1227

### CHAPTER 35. DESIGN OF SUPERHETERODYNE A-M RECEIVERS

1. INTRODUCTION ... ..	1228
2. SPECIFICATIONS AND REQUIREMENTS ... ..	1229
3. GENERAL DESIGN ... ..	1229
(i) A.V.C. and noise ... ..	1229
(ii) Audio-frequency response ... ..	1234
(iii) Hum ... ..	1239
(iv) Microphony ... ..	1241
(v) Instability ... ..	1243
(vi) The local oscillator ... ..	1244
(vii) Cabinet design ... ..	1248
(viii) Ratings ... ..	1249
(ix) Field testing ... ..	1250
4. FREQUENCY RANGES ... ..	1250
(i) Medium frequency receivers ... ..	1250
(ii) Dual wave receivers ... ..	1251
(iii) Multiband receivers ... ..	1252
(iv) Bandsread receivers ... ..	1253

## CONTENTS

SECTION	PAGE
5. A.C. OPERATED RECEIVERS ... ..	1256
(i) Four valve receivers ... ..	1256
(ii) Five valve receivers ... ..	1259
(iii) Larger receivers ... ..	1260
(iv) Communication receivers ... ..	1260
6. A.C./D.C. RECEIVERS ... ..	1264
(i) Series-resistor operation... ..	1264
(ii) Barretter operation ... ..	1266
(iii) Dial lamps ... ..	1266
(iv) Miscellaneous features ... ..	1267
7. BATTERY OPERATED RECEIVERS ... ..	1268
(i) General features ... ..	1268
(ii) Vibrator-operated receivers ... ..	1270
(iii) Characteristics of dry batteries ... ..	1272
8. CAR RADIO ... ..	1275
(i) Interference suppression ... ..	1275
(ii) Circuit considerations ... ..	1276
(iii) Valve operating conditions ... ..	1277
9. MISCELLANEOUS FEATURES ... ..	1278
(i) Spurious responses ... ..	1278
(ii) Reduction of interference ... ..	1279
(iii) Contact potential biasing ... ..	1280
(iv) Fuses ... ..	1281
(v) Tropic proofing ... ..	1282
(vi) Parasitic oscillations ... ..	1283
(vii) Printed circuits ... ..	1283
(viii) Other miscellaneous features ... ..	1285
10. REFERENCES ... ..	1285

### CHAPTER 36. DESIGN OF F-M RECEIVERS

1. F-M RECEIVERS ... ..	1287
(i) Comparison with A-M ... ..	1287
(ii) Aerial and r-f design ... ..	1287
(iii) Local oscillator design ... ..	1289
(iv) I-F amplifier ... ..	1290
(v) F-M detection and A-M rejection ... ..	1292
2. F-M/A-M RECEIVERS ... ..	1294
(i) R-F section ... ..	1294
(ii) I-F amplifier ... ..	1294
(iii) General considerations ... ..	1295
3. REFERENCES ... ..	1296

### CHAPTER 37. RECEIVER AND AMPLIFIER TESTS AND MEASUREMENTS

1. A-M RECEIVERS ... ..	1297
(i) Introduction ... ..	1297
(ii) Definitions ... ..	1297
(iii) Equipment required ... ..	1298
(iv) Measurements and operating conditions ... ..	1300
(v) Measurements ... ..	1301
(vi) Tests ... ..	1302
2. F-M RECEIVERS ... ..	1314
(i) Definitions ... ..	1314
(ii) Testing apparatus ... ..	1315



## CONTENTS

SECTION	PAGE
(iii) Test procedures and operating conditions ... ..	1315
(iv) Receiver adjustments ... ..	1316
(v) Performance tests ... ..	1317
<b>3. AUDIO FREQUENCY AMPLIFIERS</b> ... ..	<b>1321</b>
(i) Equipment and measurements ... ..	1321
(ii) Tests ... ..	1321
<b>4. MEASUREMENTS ON COILS</b> ... ..	<b>1325</b>
(i) Measurement of coefficient of coupling ... ..	1325
(ii) Measurement of primary resonant frequencies of aerial and r-f coils ... ..	1325
(iii) Measurement of distributed capacitance across coils ... ..	1325
<b>5. REFERENCES</b> ... ..	<b>1327</b>

## PART 7: SUNDRY DATA

### CHAPTER 38. TABLES, CHARTS AND SUNDRY DATA

<b>1. UNITS</b> ... ..	<b>1329</b>
(i) General physical units ... ..	1329
(ii) Electrical and magnetic units ... ..	1331
(iii) Photometric units ... ..	1334
(iv) Temperature ... ..	1334
<b>2. COLOUR CODES</b> ... ..	<b>1335</b>
(i) Colour code for fixed composition resistors ... ..	1335
(ii) Colour code for fixed wire wound resistors ... ..	1336
(iii) Table of R.M.A. colour code markings for resistors ... ..	1337
(iv) Colour code for moulded mica capacitors ... ..	1340
(v) Colour code for ceramic dielectric capacitors ... ..	1341
(vi) Colour code for i-f transformers ... ..	1342
(vii) Colour code for a-f transformers and output transformers ... ..	1342
(viii) Colour code for power transformers ... ..	1342
(ix) Colour code for loudspeakers ... ..	1343
(x) Colour code for chassis wiring ... ..	1343
(xi) Colour code for battery cables ... ..	1344
(xii) Colour code for metallized paper capacitors ... ..	1344
<b>3. STANDARD RESISTORS AND CAPACITORS</b> ... ..	<b>1344</b>
(i) Standard fixed composition resistors ... ..	1344
(ii) Standard fixed wire wound resistors ... ..	1346
(iii) Fixed paper dielectric capacitors in tubular non-metallic cases ... ..	1347
(iv) Metal encased fixed paper dielectric capacitors for d.c. application ... ..	1349
(v) Standard fixed mica dielectric capacitors ... ..	1351
(vi) Standard ceramic dielectric capacitors ... ..	1352
(vii) Standard variable capacitors ... ..	1354
(viii) Standard variable composition resistors ... ..	1356
(ix) Standard metallized paper dielectric capacitors ... ..	1357
(x) Standard electrolytic capacitors ... ..	1357
(xi) References to standard resistors and capacitors ... ..	1358
<b>4. STANDARD FREQUENCIES</b> ... ..	<b>1361</b>
(i) Standard frequency ranges ... ..	1361
(ii) Frequency bands for broadcasting ... ..	1361
(iii) Standard intermediate frequencies ... ..	1361
<b>5. WAVELENGTHS AND FREQUENCIES</b> ... ..	<b>1362</b>
(i) Wavelength-frequency conversion tables ... ..	1362
(ii) Wavelengths of electromagnetic radiations ... ..	1363
<b>6. STANDARD SYMBOLS AND ABBREVIATIONS</b> ... ..	<b>1363</b>
(i) Introduction ... ..	1363
(ii) Multipliers ... ..	1363



Instituto Nacional  
de Tecnología Industrial ... 1363

Extensión y Desarrollo  
División Biblioteca

# CONTENTS

SECTION	PAGE
(iii) Some units and multipliers ... ..	1363
(iv) Magnitude letter symbols ... ..	1364
(v) Subscripts for magnitude letter symbols ... ..	1364
(vi) Magnitude letter symbols with subscripts ... ..	1365
(vii) Mathematical signs ... ..	1366
(viii) Abbreviations ... ..	1366
(ix) Abbreviations of titles of periodicals ... ..	1367
(x) References to periodicals ... ..	1369
(xi) References to standard symbols and abbreviations ... ..	1369
7. STANDARD GRAPHICAL SYMBOLS ... ..	1370
8. PROPERTIES OF MATERIALS AND CHEMICAL AND PHYSICAL CONSTANTS ... ..	1372
(i) Properties of insulating materials ... ..	1372
(ii) Properties of conducting materials ... ..	1374
(iii) Composition of some common plastics ... ..	1375
(iv) Weights of common materials... ..	1375
(v) Resistance of a conductor at any temperature ... ..	1376
(vi) References to properties of materials... ..	1376
(vii) Chemical and physical constants ... ..	1376
9. REACTANCE, IMPEDANCE AND RESONANCE ... ..	1377
(i) Inductive reactances ... ..	1377
(ii) Capacitive reactances ... ..	1378
(iii) Impedance of reactance and resistance in parallel ... ..	1380
(iv) Impedance of reactance and resistance in series ... ..	1382
(v) Resonance... ..	1386
(vi) Approximations in the calculation of impedance for reactance and resistance in series and parallel ... ..	1386
(vii) Reactance chart ... ..	1387
10. SCREW THREADS, TWIST DRILLS AND SHEET GAUGES ... ..	1388
(i) Standard American screws used in radio manufacture ... ..	1388
(ii) B.A. screw threads ... ..	1389
(iii) Whitworth screw threads ... ..	1389
(iv) Unified screw threads ... ..	1390
(v) Drill sizes for self-tapping screws ... ..	1391
(vi) Wood screws ... ..	1391
(vii) Twist drill sizes ... ..	1392
(viii) Sheet steel gauges ... ..	1393
11. TEMPERATURE RISE AND RATINGS ... ..	1394
12. FUSES ... ..	1395
13. CHARACTERISTICS OF LIGHT ; PANEL LAMPS ... ..	1396
(i) Visibility curves of the human eye and relative spectral energy curves of sunlight and tungsten lamp ... ..	1396
(ii) Velocity of light ... ..	1396
(iii) American panel lamp characteristics ... ..	1397
14. GREEK ALPHABET ... ..	1397
15. DEFINITIONS ... ..	1398
16. DECIMAL EQUIVALENTS OF FRACTIONS ... ..	1404
17. MULTIPLES AND SUB-MULTIPLES ... ..	1405
18. (i) Numerical values ... ..	1406
(ii) Factorials ... ..	1407
19. WIRE TABLES ... ..	1408
20. LOGARITHM TABLES ... ..	1418
21. TRIGONOMETRICAL TABLES ... ..	1420
Hyperbolic sines, cosines and tangents ... ..	1421
22. LOG SCALES AND LOG SCALE INTERPOLATOR ... ..	1422